

OPERATIONAL AMPLIFIERS

Design and Applications

JERALD G. GRAEME

Editor, Part 1

*Manager, Monolithic Engineering
Burr-Brown Research Corporation*

GENE E. TOBEY

Editor, Part 2

*Amplifier Product Marketing Engineer
Burr-Brown Research Corporation*

LAWRENCE P. HUELSMAN, Ph.D.

Consulting Editor

*Professor of Electrical Engineering
The University of Arizona*

McGRAW-HILL BOOK COMPANY

New York St. Louis San Francisco Düsseldorf Johannesburg
Kuala Lumpur London Mexico Montreal New Delhi Panama
Paris São Paulo Singapore Sydney Tokyo Toronto

CONT

OPERATIONAL AMPLIFIERS

Copyright © 1971 by Burr-Brown Research Corporation. All Rights Reserved. Printed in the United States of America. No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher. *Library of Congress Catalog Card Number 74-163297*

ISBN 07-064917-0

8 9 0 K P K P 7 9 8 7 6 5 4

The information conveyed in this book has been carefully reviewed and believed to be accurate and reliable; however, no responsibility is assumed for the operability of any circuit diagram or inaccuracies in calculations or statements. Further, nothing herein conveys to the purchaser a license under the patent rights of any individual or organization relating to the subject matter described herein.

*Contributor
Preface
Historical I*

Part :

1. DIFFEREI

- 1.1 Lov
- 1.2 Hig
- 1.3 Cor
- 1.4 Dif
- 1.5 Dif

2. INPUT E

- 2.1 Inp
- 2.2 Inp
- 2.3 Inp
- 2.4 Eq

APPLICATION

Rating of

circuit for
used to as a
have quite
r triangle
nt circuit
es should
de of the

res act as
l current
ge wave-
shown in
fig. 10.10

Waveform Generators

381

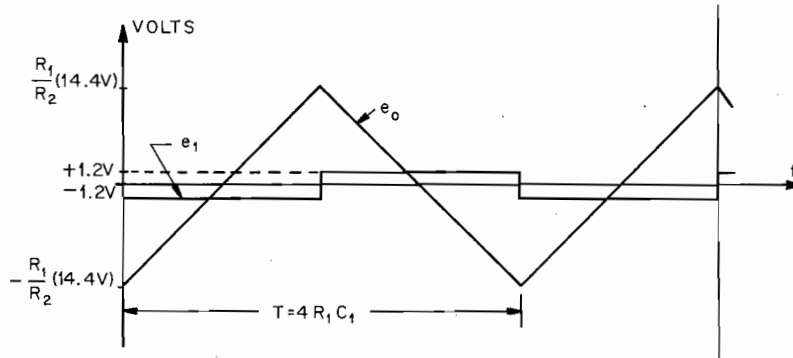


Fig. 10.11 Triangle generator waveforms.

would be $R_2 = 10 \text{ k}\Omega$, $R_1 = 5 \text{ k}\Omega$, $R_3 = 100 \text{ k}\Omega$, $C_1 = 0.1 \text{ }\mu\text{F}$. These values will provide a triangle wave of approximately $+7.2$ to -7.2 V swing at a frequency of 500 Hz .

10.3 Sine-wave Generators³⁻⁵

One of the most important waveforms that an engineer may be called upon to generate is the sinusoidal waveform. In this section we shall treat a variety of techniques which may be used to perform this task. Specifically we shall investigate the use of Wien-bridge oscillators, quadrature oscillators, and phase-shift oscillators. For the Wien-bridge and the quadrature oscillator case several different circuits are considered. These may be applied to different special requirements as indicated in the discussion of the circuits.

10.3.1 Wien-bridge oscillator—general description A Wien bridge may be combined with an operational amplifier to form an excellent sine-wave generator. Some sort of automatic gain control is generally used to stabilize the magnitude of the output sinusoid. A general schematic of a Wien-bridge oscillator is shown in Fig. 10.12. To see how this circuit operates let us assume that the output e_o is a sinusoid; then the feedback ratio of the bridge is given by

$$\frac{Z_2}{Z_1 + Z_2} = \frac{R_2}{R_1 + R_2(1 + C_2/C_1) + j(\omega R_1 R_2 C_2 - 1/\omega C_1)}$$

where $Z_1 = R_1 + 1/j\omega C_1$ and $Z_2 = R_2/(1 + j\omega R_2 C_2)$. The operational amplifier will maintain 0 V between its input terminals; thus,

$$\beta \hat{E}_o = \frac{Z_2}{Z_1 + Z_2} \hat{E}_o$$

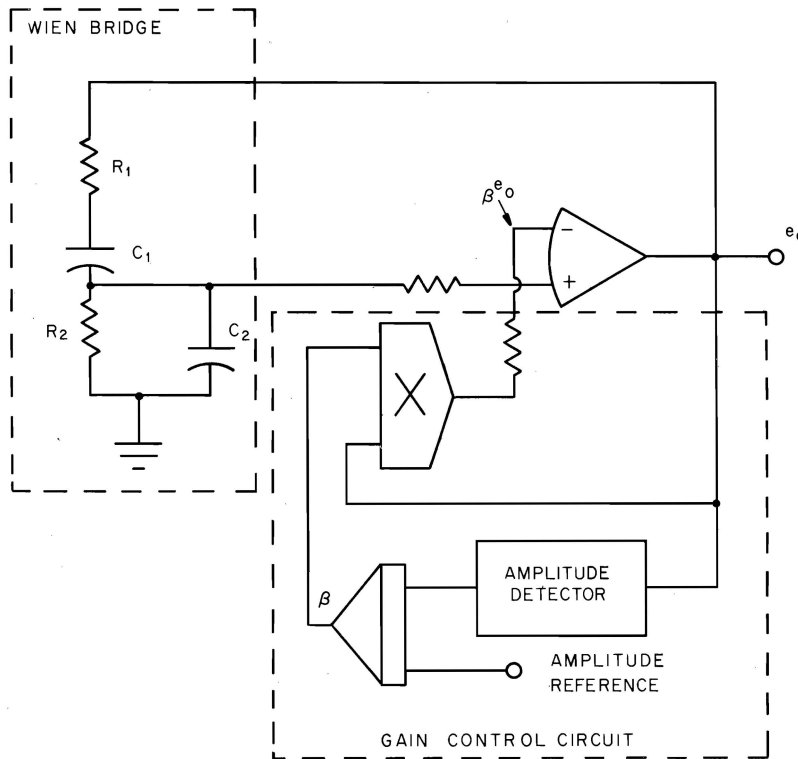


Fig. 10.12 Wien-bridge oscillator.

where \hat{E}_o is a phasor representing the voltage $e_o(t)$. The condition for oscillation is

$$\omega_o R_1 R_2 C_2 - \frac{1}{\omega_o C_1} = 0$$

$$\omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

If we make $R_1 = R_2$ and $C_1 = C_2$, then

$$\omega_o = \frac{1}{R_1 C_1} \quad \text{and} \quad \beta = \frac{1}{3}$$

If $\beta = \frac{1}{3}$ and the condition of $R_1 = R_2$ and $C_1 = C_2$ is met, then the output will be a sinusoid of frequency $1/2\pi RC$.

It should be noted that, so long as β is $\frac{1}{3}$, the circuit will oscillate at any amplitude. Also, if β is less than $\frac{1}{3}$, the oscillation will diverge and if β is more than $\frac{1}{3}$ the oscillation will converge. Thus it is common practice to provide some sort of automatic amplitude control. This is usually

done by va
Incandescce
multipliers

10.3.2 Pre
of the gen
sider the c
by R_1 , C_1
plified by A
 A_3 and A_4 .
only when
 A diode br
can be use
The int
tradeoff b
allow the c
any distu
minimize
ously, will

where R_1
10 kHz ar
and excell
operate at
must be c
Althoug
are used, s
In such p
used to m

10.3.3 Le
circuit pr
requiring
Wien-brid
given. T
are requi
cussed W
will be in
impedanc
diodes, w
be used v

done by varying the negative feedback gain (β) to stabilize the oscillator. Incandescent lamps, thermistors, FETs, diode bridges, or general-purpose multipliers can all be used for such gain control purposes.

10.3.2 Precise Wien-bridge oscillator^{4,5} As a typical implementation of the general Wien-bridge oscillator diagram shown in Fig. 10.12, consider the circuit shown in Fig. 10.13. The actual Wien bridge is formed by R_1 , C_1 , R_2 , and C_2 . The oscillatory output of amplifier A_1 is amplified by A_2 , and the output level is sensed by the absolute-value circuit of A_3 and A_4 . The amplifier A_4 acts as an error integrator and will stabilize only when the absolute value of the input equals the reference amplitude. A diode bridge is used for varying the negative feedback of A_1 . An FET can be used for gain control rather than the diode bridge if desired.

The integrator gain is set by capacitor C_3 . The choice of C_3 is a tradeoff between response time and distortion. Small values of C_3 will allow the circuit to reach its stable value very rapidly. Also, response to any disturbance is rapid. On the other hand, making C_3 large will minimize distortion. The frequency of oscillation, as discussed previously, will be

$$f_o = \frac{1}{2\pi R_1 C_1}$$

where $R_1 = R_2$ and $C_1 = C_2$. Frequencies in the range of 10 Hz to 10 kHz are practical for this circuit. Distortion of less than 0.1 percent and excellent frequency stability are readily achieved. The circuit will operate at frequencies above 10 kHz, but the type of operational amplifier must be carefully chosen and stray capacitances should be considered.

Although, in the circuit shown in Fig. 10.13, five operational amplifiers are used, similar circuits are available in miniature encapsulated packages. In such packages, integrated-circuit operational amplifiers are usually used to minimize the size.

10.3.3 Low-cost Wien-bridge oscillator The Wien-bridge oscillator circuit presented in the preceding paragraphs has the disadvantage of requiring five operational amplifiers. In Fig. 10.14 a circuit diagram for a Wien-bridge oscillator which requires only one operational amplifier is given. The primary virtue of this circuit is that very few components are required. Distortion will be greater than with the previously discussed Wien bridge. But, depending upon care of adjustment, distortion will be in the range of 1 to 5 percent. This circuit has high output impedance, and any loading at e_o will shift the operating point of the diodes, which will in turn change the amplitude. Thus this circuit *must* be used with either a fixed load at e_o or a buffer must be added. As with