



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

# AN-5841

## Applying SG5841 to Control a Flyback Power Supply

### Summary

This application note describes a detailed design strategy for a high-efficiency, compact flyback converter. Design considerations, mathematical equations, and guidelines for a printed circuit board layout are provided.

### Features

- Green-Mode PWM Controller
- Low Startup Current: 14 $\mu$ A
- Low Operating Current: 4mA
- Programmable PWM Frequency with Hopping
- Peak-Current-Mode Control
- Cycle-by-Cycle Current Limiting
- Synchronized Slope Compensation
- Leading-Edge Blanking (LEB)
- Constant Output Power Limit
- Totem-Pole Output with Soft Driving
- V<sub>DD</sub> Over-Voltage Clamping
- Programmable Over-Temperature Protection (OTP)
- Internal Open-Loop Protection
- V<sub>DD</sub> Under-Voltage Lockout (UVLO)
- GATE Output Maximum Voltage Clamp: 18V

### Description

The SG5841 is a highly integrated PWM controller IC. It provides features to satisfy the need for low standby power consumption. With low startup current and low operating current, high-efficiency power conversion is achieved. Typical startup current is only 14 $\mu$ A and operating current is around 4mA. In nominal loading conditions, the SG5841 operates at fixed PWM frequency. As the load decreases, its proprietary green-mode circuit gradually reduces the PWM frequency. This green-mode function dramatically cuts the power loss in no-load and light-load conditions, enabling the power supply to meet power conservation requirements.

Additionally, the controller incorporates many protection functions. Once the power supply is overloaded, the controller forces the power supply into “hiccup” mode to limit output power. The built-in line-voltage compensation circuit maintains constant maximum output power for a wide input line voltage range. An external negative-temperature-coefficient (NTC) thermistor can be connected to the RT pin for over-temperature protection.

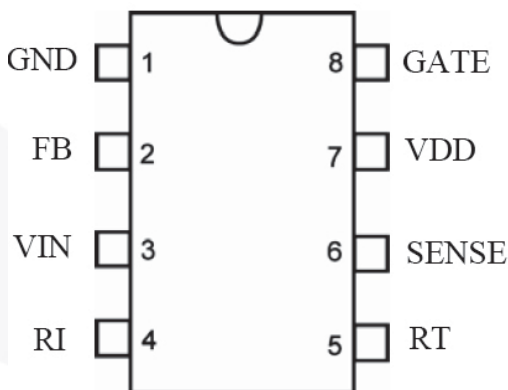


Figure 1. Pin Configuration

## Block Diagram

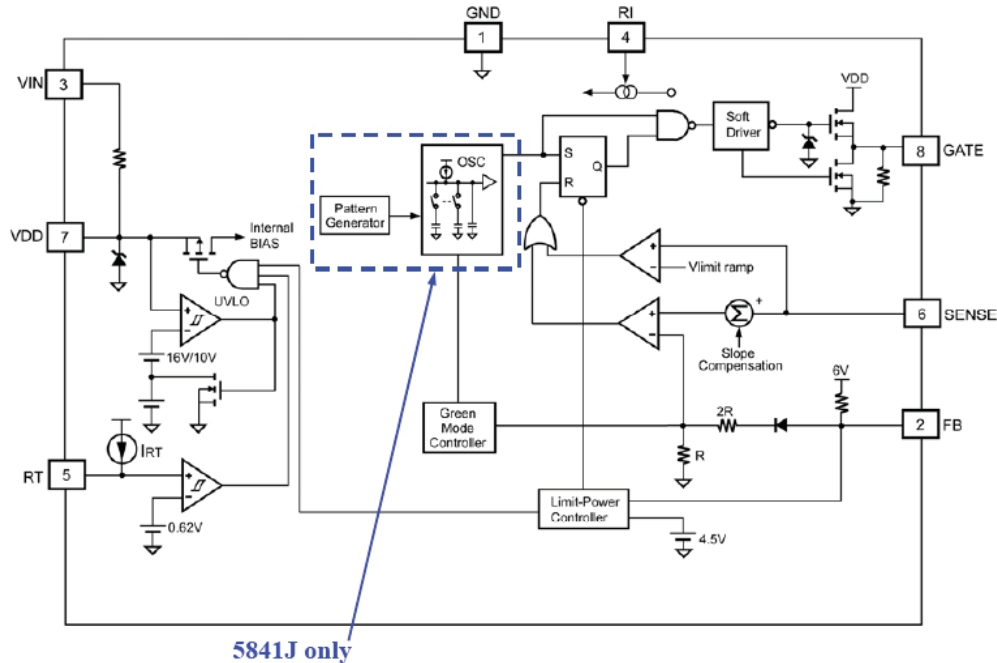


Figure 2. Block Diagram

## Startup Circuitry

When the power is turned on, the input rectified voltage  $V_{DC}$  charges the hold-up capacitor  $C1$  via a startup resistor  $R_{IN}$ .  $R_{IN}$  can be connected to the VIN or VDD pin directly. As the voltage of VDD pin reaches the start threshold voltage  $V_{DD-ON}$ , the SG5841 activates and drives the entire power supply to work.

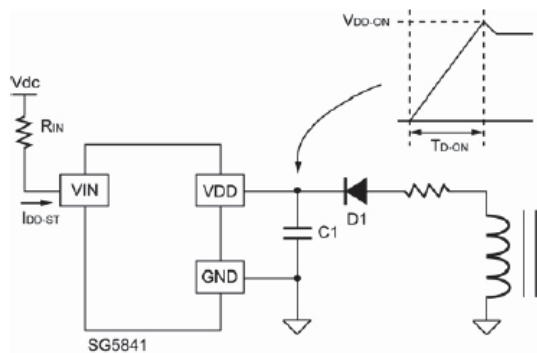


Figure 3. Single-Step Circuit Providing Power

The maximum power-on delay time is determined as:

$$V_{DD-ON} = (V_{DC} - I_{DD-ST} \cdot R_{IN}) \left[ 1 - e^{-\frac{t_{D-ON}}{R_{IN} \cdot C1}} \right] \quad (1)$$

where:

$I_{DD-ST}$  is the startup current of the SG5841;  
 $t_{D-ON}$  is the power-on delay of the power supply.

Due to the low startup current, a large  $R_{IN}$ , such as  $1.5M\Omega$ , can be used. With a hold-up capacitor of  $4.7\mu F$ , the power-on delay  $t_{D-ON}$  is less than 3.3s for  $90V_{AC}$  input.

If a shorter startup time is required, a two-step startup circuit, as shown in Figure 4, is recommended. In this circuit, a smaller  $C1$  capacitor can be used to reduce the startup time without using a smaller startup resistor  $R_{IN}$  and increasing the power dissipation on  $R_{IN}$ . The energy supporting the SG5841 after startup is mainly from a bigger capacitor  $C2$ .

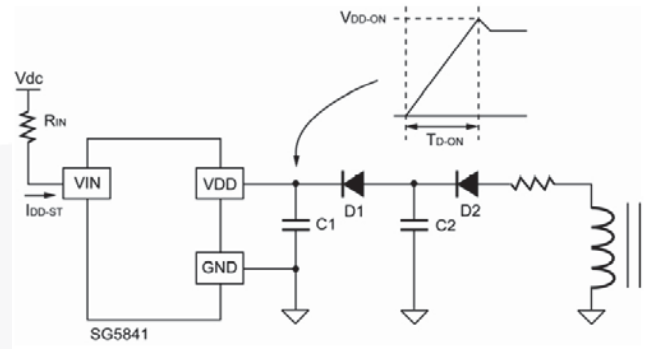


Figure 4. Two-Step Circuit Providing Power

The maximum power dissipation of  $R_{IN}$  is:

$$P_{RIN,max} = \frac{(V_{DC,max} - V_{DD})^2}{R_{IN}} \cong \frac{V_{DC,max}^2}{R_{IN}} \quad (2)$$

where  $V_{DC,max}$  is the maximum rectified input voltage.

Take a wide-range input ( $90V_{AC}$ - $264V_{AC}$ ) as an example:

$$V_{DC}=100V\sim 380V$$

$$P_{RIN,max} = \frac{380^2}{1.5 \times 10^6} \cong 96mW \quad (3)$$

In addition to the low startup current, SG5841 consumes less normal operating current than traditional UC384x.

To achieve a successful startup and keep a no-load input power low enough to meet the power-saving requirements; the voltage level of  $V_{DD}$  is recommended to be designed above 12V at no load.

If the voltage of  $V_{DD}$  falls below UVLO during “adaptive off-time modulation,” the unit enters “hiccup” operation.

### Oscillation and Green Mode

Resistor  $R_I$  programs the frequency of the internal oscillator. A  $26K\Omega$  resistor  $R_I$  generates PWM frequency as 65KHz:

$$f_{PWM} (KHz) = \frac{1690}{R_I(K\Omega)} \quad (4)$$

The range of the PWM frequency is recommended between 47KHz ~ 109KHz.

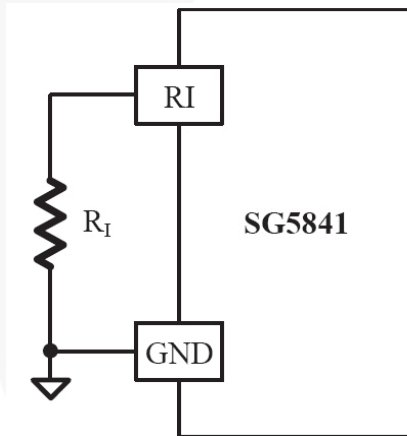


Figure 5. Setting PWM Frequency

The proprietary green mode provides off-time modulation to reduce the PWM frequency at light-load and no-load conditions. The feedback voltage of the FB pin is taken as a reference. When the feedback voltage is lower than  $\sim 2.1V$ , the PWM frequency decreases. Because most losses in a switching-mode power supply are proportional to the PWM frequency, off-time modulation reduces the power consumption of the power supply at light-load and no-load conditions. For a typical case of  $R_I = 26K\Omega$ , the PWM frequency is 65KHz at nominal load and decreases to 22KHz at light load, about one-third the nominal PWM frequency. The power supply enters “adaptive off-time modulation” in zero-load conditions.

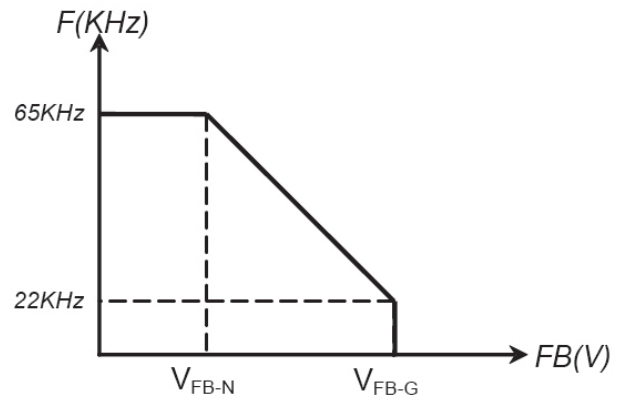


Figure 6. PWM Frequency vs. FB Voltage ( $R_I=26K\Omega$ )

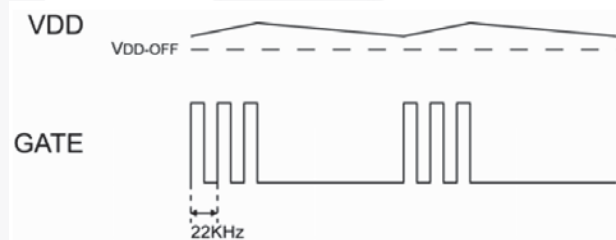


Figure 7. Adaptive Off-Time Modulation

A frequency hopping function improves the system level of EMI performance. The PWM switching frequency hops between 65KHz  $\pm$  4.2KHz, with a hopping period of around 4.4ms (5841J only).

### The FB Input

The SG5841 is designed for peak-current-mode control. A current-to-voltage conversion is done externally with a current-sense resistor  $R_S$ . Under normal operation, the peak inductor current is controlled by FB level:

$$I_{pk} = \frac{V_{FB} - 1.2}{3 \cdot R_S} \quad (5)$$

where  $V_{FB}$  is the voltage of the FB pin.

When  $V_{FB}$  is less than 1.2V, the SG5841 terminates the output pulses.

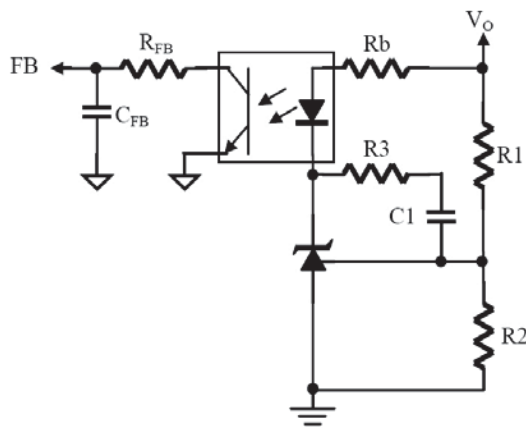


Figure 8. Feedback Circuit

Figure 8 is a typical feedback circuit consisting mainly of a shunt regulator and an opto-coupler.  $R_1$  and  $R_2$  form a voltage divider for the output voltage regulation.  $R_3$  and  $C_1$  are adjusted for control-loop compensation. A small-value RC filter (e.g.  $R_{FB}=47\Omega$ ,  $C_{FB}=1nF$ ) from FB to GND can increase stability. The maximum sourcing current of FB pin is 2mA. The phototransistor must be capable of sinking this current to pull FB level down at no load. The value of biasing resistor  $R_b$  is determined as:

$$\frac{V_O - V_D - V_Z}{R_b} \bullet K \geq 2mA \quad (6)$$

where:

$V_D$  is the drop voltage of photodiode, about 1.2V;  
 $V_Z$  is the minimum operation voltage, 2.5V of the shunt regulator; and  
 $K$  is the current transfer rate (CTR) of the opto coupler.

For an output voltage  $V_O=5V$  with  $CTR=100\%$ , the maximum value of  $R_b$  is 650 $\Omega$ .

### Built-in Slope Compensation

A flyback converter can be operated in discontinuous current mode (DCM) or continuous current mode (CCM). There are many advantages to operating the converter in CCM. With the same output power, a converter in CCM exhibits smaller peak inductor current than in DCM. Therefore, a small sized transformer and a low-rating MOSFET can be applied. On the secondary side of the transformer, the rms output current of DCM can be up to twice of CCM. Larger wire gauge and output capacitors with larger ripple current rating are required. DCM operation also results in higher output voltage spikes. A large LC filter has also to be added. Therefore, a flyback converter in CCM achieves better performance with lower component cost.

Despite the above advantages of CCM operation, there is one concern – stability. In CCM operation, the output power is proportional to the average inductor current, while the peak current is controlled. This causes the well-known sub-harmonic oscillation when the PWM duty cycle exceeds 50%. Adding slope compensation (reducing

the current-loop gain) is an effective way to prevent this oscillation. The SG5841 introduces a synchronized positive-going ramp ( $V_{SLOPE}$ ) in every switching cycle to stabilize the current loop. Therefore, the SG5841 allows design of cost-effective, highly efficient, compact flyback power supplies operating in CCM without adding any external components.

The positive ramp added is:

$$V_{SLOPE} = V_{SL} \bullet D \quad (7)$$

where:

$$V_{SL}=0.33V;$$

$$D=\text{Duty Cycle.}$$

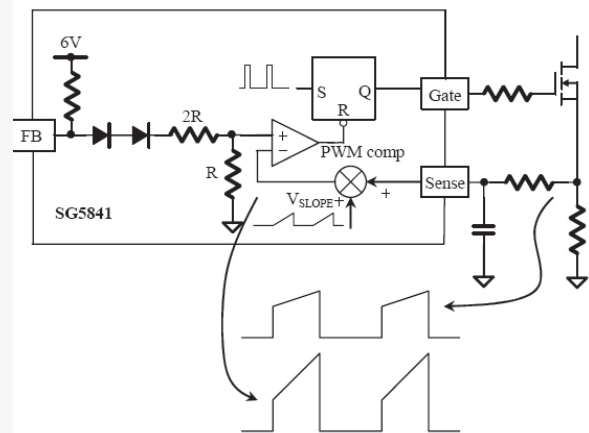


Figure 9. Synchronized Slope Compensation

### Leading Edge Blanking (LEB)

A voltage signal proportional to the MOSFET current develops on the current-sense resistor  $R_s$ . Each time the MOSFET is turned on, a spike induced by the diode reverse recovery and by the output capacitances of the MOSFET and diode, occurs on the sensed signal. A leading-edge blanking time of about 270ns is introduced to avoid premature termination of MOSFET. Therefore, only a small-value RC filter (e.g. 100 $\Omega$  + 470pF) is required between the SENSE pin and  $R_s$ . Still, a non-inductive resistor for the  $R_s$  is recommended.

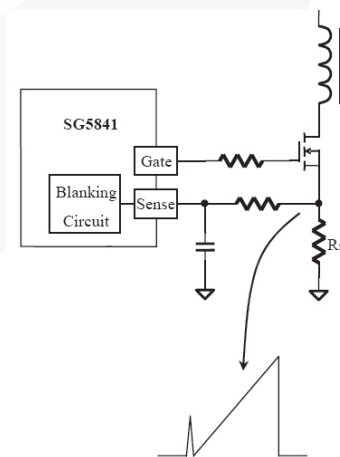


Figure 10. Turn-on Spike

# Explore Litigation Insights

Docket Alarm provides insights to develop a more informed litigation strategy and the peace of mind of knowing you're on top of things.

## Real-Time Litigation Alerts



Keep your litigation team up-to-date with **real-time alerts** and advanced team management tools built for the enterprise, all while greatly reducing PACER spend.

Our comprehensive service means we can handle Federal, State, and Administrative courts across the country.

## Advanced Docket Research



With over 230 million records, Docket Alarm's cloud-native docket research platform finds what other services can't. Coverage includes Federal, State, plus PTAB, TTAB, ITC and NLRB decisions, all in one place.

Identify arguments that have been successful in the past with full text, pinpoint searching. Link to case law cited within any court document via Fastcase.

## Analytics At Your Fingertips



Learn what happened the last time a particular judge, opposing counsel or company faced cases similar to yours.

Advanced out-of-the-box PTAB and TTAB analytics are always at your fingertips.

## API

Docket Alarm offers a powerful API (application programming interface) to developers that want to integrate case filings into their apps.

## LAW FIRMS

Build custom dashboards for your attorneys and clients with live data direct from the court.

Automate many repetitive legal tasks like conflict checks, document management, and marketing.

## FINANCIAL INSTITUTIONS

Litigation and bankruptcy checks for companies and debtors.

## E-DISCOVERY AND LEGAL VENDORS

Sync your system to PACER to automate legal marketing.