

ADVANCED
MICROELECTRONICS

Kiyoo Itoh

VLSI Memory Chip Design



Springer

RONICS

rovides systematic information on
manufacturing of microelectronic
rchers or engineers in their fields,
ch as wafer processing, materials,
VLSI implementation, and subsys-
i physics and engineering and the
as research scientists.

ss Communication

ooks/ssam/

Kiyoo Itoh

VLSI Memory Chip Design

With 416 Figures and 26 Tables



Springer

Dr. Kiyoo Itoh
Hitachi Ltd., Central Research Laboratory
1-280, Higashi-Koigakubo
Kokubunji-shi
Tokyo185-8601
Japan
e-mail: k-itoh@crl.hitachi.co.jp

Series Editors:

Dr. Kiyoo Itoh
Hitachi Ltd., Central Research Laboratory
1-280 Higashi-Koigakubo
Kokubunji-shi
Tokyo 185-8601
Japan

Professor Takayasu Sakurai
Center for Collaborative Research
University of Tokyo
7-22-1 Roppongi, Minato-ku,
Tokyo 106-8558
Japan

Library of Congress Cataloging-in-Publication Data

Itoh, Kiyoo, 1941-
VLSI memory chip design / Kiyoo Itoh.
p. cm. -- (Springer series in advanced microelectronics ; 5)
Includes bibliographical references and index.
ISBN 3540678204 (alk. paper)
1. Semiconductor storage devices--Design and construction. 2. Integrated
circuits--Very large scale integration--Design and construction. I. Title. II. Series.

TK7895.M4 I876 2001
621.39'732--dc21

00-068735

ISSN 1437-0387

ISBN 3-540-67820-4 Springer-Verlag Berlin Heidelberg New York

This work is subject to copyright. All rights are reserved, whether the whole or part of the material is concerned, specifically the rights of translation, reprinting, reuse of illustrations, recitation, broadcasting, reproduction on microfilm or in any other way, and storage in data banks. Duplication of this publication or parts thereof is permitted only under the provisions of the German Copyright Law of September 9, 1965, in its current version, and permission for use must always be obtained from Springer-Verlag. Violations are liable for prosecution under the German Copyright Law.

Springer-Verlag Berlin Heidelberg New York
a member of Springer Science+Business Media

<http://www.springer.de>

© Springer-Verlag Berlin Heidelberg 2001
Printed in Germany

The use of general descriptive names, registered names, trademarks, etc. in this publication does not imply, even in the absence of a specific statement, that such names are exempt from the relevant protective laws and regulations and therefore free for general use.

Typesetting by the author.

Data conversion and figure processing by LE-TeX Jelonek, Schmidt & Vöckler GbR, 04229 Leipzig.

Cover concept by eStudio Calmar Steinen using a background picture from Photo Studio "SONO". Courtesy of Mr. Yukio Sono, 3-18-4 Uchi-Kanda, Chiyoda-ku, Tokyo.
Cover design: *design & production* GmbH, Heidelberg

Printed on acid-free paper SPIN: 12187942 57/3180 - 5 4 3

ance, the basic technologies
 peripheral circuits are des-
 cy are explained. Chapter 4
 M which strongly influences
 , in the chip. The relation-
 ving/sensing is explained in
 on-chip voltage generators
 tors are essential for power-
 apter 6 discusses subsystem-
 mportant in providing wide
 S. Chapters 7 and 8 describe
 sizing the importance of the
 f lowering power-supply vol-
 old-current reduction which

leagues and the office admi-
 Ohta, at Hitachi Ltd. They
 to finalize my work. Special
 inuing support and patience

Kiyoo Itoh

Contents

1. An Introduction to Memory Chip Design	1
1.1 Introduction	1
1.2 The Internal Organization of Memory Chips	3
1.2.1 The Memory Cell Array	3
1.2.2 The Peripheral Circuit	5
1.2.3 The I/O Interface Circuit	6
1.3 Categories of Memory Chip	6
1.4 General Trends in DRAM Design and Technology	11
1.4.1 The History of Memory-Cell Development	11
1.4.2 The Basic Operation of The 1-T Cell	15
1.4.3 Advances in DRAM Design and Technology	19
1.5 General Trends in SRAM Design and Technology	24
1.5.1 The History of Memory-Cell Development	24
1.5.2 The Basic Operation of a SRAM Cell	26
1.5.3 Advances in SRAM Design and Technology	29
1.6 General Trends in Non-Volatile Memory Design and Technology	31
1.6.1 The History of Memory-Cell Development	31
1.6.2 The Basic Operation of Flash Memory Cells	34
1.6.3 Advances in Flash-Memory Design and Technology ...	46
2. The Basics of RAM Design and Technology	49
2.1 Introduction	49
2.2 Devices	49
2.2.1 MOSFETs	49
2.2.2 Capacitors	57
2.2.3 Resistors	60
2.2.4 Wiring and Wiring Materials	61
2.2.5 Silicon Substrates and CMOS Latch-Up	65
2.2.6 Other Devices	67
2.3 NMOS Static Circuits	67
2.3.1 The dc Characteristics of an Inverter	68
2.3.2 The ac Characteristics of an Inverter	70
2.3.3 The Improved NMOS Static Inverter	74

VIII Contents

2.4	NMOS Dynamic Circuits	76
2.4.1	The Dynamic Inverter	76
2.4.2	The Bootstrap Driver	77
2.5	CMOS Circuits	79
2.5.1	The dc Characteristics	80
2.5.2	The ac Characteristics	82
2.6	Basic Memory Circuits	83
2.6.1	The Inverter and the Basic Logic Gate	83
2.6.2	The Current Mirror	83
2.6.3	The Differential Amplifier	83
2.6.4	The Voltage Booster	87
2.6.5	The Level Shifter	88
2.6.6	The Ring Oscillator	88
2.6.7	The Counter	89
2.7	The Scaling Law	90
2.7.1	Constant Electric-Field Scaling	90
2.7.2	Constant Operation-Voltage Scaling	92
2.7.3	Combined Scaling	92
2.8	Lithography	93
2.9	Packaging	94
3.	DRAM Circuits	97
3.1	Introduction	97
3.1.1	High-Density Technology	98
3.1.2	High-Performance Circuits	100
3.2	The catalog Specifications of the Standard DRAM	102
3.2.1	Operational Conditions	102
3.2.2	Modes of Operation and Timing Specifications	105
3.3	The Basic Configuration and Operation of the DRAM Chip ..	110
3.3.1	Chip Configuration	110
3.3.2	Address Multiplexing	111
3.4	Fundamental Chip Technologies	113
3.4.1	A Larger Memory Capacity and Scaled-Down Devices ..	113
3.4.2	High S/N Ratio Circuits	116
3.4.3	Low Power Circuits	117
3.4.4	High-Speed Circuits	123
3.4.5	The Multidivision of a Memory Array	128
3.5	The Multidivided Data Line and Word Line	131
3.5.1	The Multidivided Data Line	132
3.5.2	The Multidivided Word Line	139
3.6	Read and Relevant Circuits	141
3.6.1	The Address Buffer	141
3.6.2	The Address Decoder	144
3.6.3	The Word Driver	147
3.6.4	The Sensing Circuit	157

..... 76
 76
 77
 79
 80
 82
 83
 Gate 83
 83
 87
 88
 88
 89
 90
 90
 ig 92
 92
 93
 94
 97
 97
 98
 100
 d DRAM 102
 102
 pecifications 105
 of the DRAM Chip .. 110
 110
 111
 113
 caled-Down Devices . 113
 116
 117
 123
 ray 128
 ine 131
 132
 139
 141
 141
 144
 147
 157

3.6.5 The Common I/O-Line Relevant Circuit 167
 3.6.6 The Data-Output Buffer 172
 3.7 Write and Relevant Circuits 174
 3.8 Refresh-Relevant Circuits 175
 3.8.1 Refresh Schemes 175
 3.8.2 The Extension of Data-Retention Time
 in Active Mode 176
 3.8.3 Current Reduction Circuits in Data-Retention Mode .. 176
 3.9 Redundancy Techniques 178
 3.9.1 Issues for Large-Memory-Capacity Chips 184
 3.9.2 Intra-Subarray Replacement Redundancy 185
 3.9.3 Inter-Subarray Replacement Redundancy 189
 3.9.4 The Repair of dc-Characteristics Faults 191
 3.10 On-Chip Testing Circuits 192

4. High Signal-to-Noise Ratio
DRAM Design and Technology 195
 4.1 Introduction 195
 4.2 Trends in High S/N Ratio Design 195
 4.2.1 The Signal Charge 197
 4.2.2 Leakage Charge 204
 4.2.3 The Soft-Error Critical Charge 208
 4.2.4 The Data-Line Noise Charge 210
 4.3 Data-Line Noise Reduction 210
 4.3.1 Noise Sources and Their Reduction 210
 4.3.2 Word-Line Drive Noise 213
 4.3.3 Data-Line and Sense-Amplifier Imbalances 217
 4.3.4 Word-Line to Data-Line Coupling Noise 230
 4.3.5 Data-Line Interference Noise 237
 4.3.6 Power-Supply Voltage Bounce 240
 4.3.7 Variation in the Reference Voltage 241
 4.3.8 Other Noises 244
 4.4 Summary 247

5. On-Chip Voltage Generators 249
 5.1 Introduction 249
 5.2 The Substrate-Bias Voltage (V_{BB}) Generator 251
 5.2.1 The Roles of the V_{BB} generator 251
 5.2.2 Basic Operation and Design Issues 256
 5.2.3 Power-On Characteristics 258
 5.2.4 Characteristics in the High- V_{DD} Region 264
 5.2.5 The V_{BB} Bump 266
 5.2.6 Substrate-Current Generation 269
 5.2.7 Triple-Well Structures 272
 5.2.8 Low-Power V_{BB} Generators 273

5.3	The Voltage Up-Converter	276
5.3.1	The Roles of the Voltage Up-Converter	276
5.3.2	Design Approaches and Issues	278
5.3.3	High Boost-Ratio Converters	283
5.3.4	Low-Power, High Supply Current Converters	285
5.4	The Voltage Down-Converter	290
5.4.1	The Roles of the Voltage Down-Converter	290
5.4.2	The Negative-Feedback Converter and Design Issues ..	293
5.4.3	Optimum Design	297
5.4.4	Phase Compensation	301
5.4.5	Reference-Voltage Generators	316
5.4.6	Burn-In Test Circuits	323
5.4.7	Voltage Trimming	327
5.4.8	Low-Power Circuits	329
5.5	The Half- V_{DD} Generator	332
5.6	Examples of Advanced On-Chip Voltage Generators	333
6.	High-Performance Subsystem Memories	339
6.1	Introduction	339
6.2	Hierarchical Memory Systems	341
6.2.1	Memory Hierarchy	341
6.2.2	Improvements in Memory-Subsystem Performance	344
6.2.3	Memory-Chip Performance	349
6.3	Memory-Subsystem Technologies	354
6.3.1	Wide-Bit I/O Chip Configurations	354
6.3.2	Parallel Operation of Multidivided Arrays	354
6.3.3	Multibank Interleaving	357
6.3.4	Synchronous Operation	358
6.3.5	Pipeline/Prefetch Operations	362
6.3.6	High-Speed Clocking Schemes	363
6.3.7	Terminated I/O Interfaces	363
6.3.8	High-Density Packaging	364
6.4	High-Performance Standard DRAMs	365
6.4.1	Trends in Chip Development	365
6.4.2	Synchronous DRAM	368
6.4.3	Rambus DRAM	380
6.5	Embedded Memories	383
7.	Low-Power Memory Circuits	389
7.1	Introduction	389
7.2	Sources and Reduction of Power Dissipation in a RAM Subsystem	392
7.2.1	Wide-Bit I/O Chip Configuration	393
7.2.2	Small Package	394
7.2.3	The Low-Voltage Data-Bus Interface	396

..... 276
 verter..... 276
 278
 283
 Converters..... 285
 290
 onverter 290
 r and Design Issues .. 293
 297
 301
 316
 323
 327
 329
 332
 e Generators 333


 s 339
 339
 341
 341
 stem Performance 344
 349
 354
 ns..... 354
 d Arrays 354
 357
 358
 362
 363
 363
 364
 365
 365
 368
 380
 383

 389
 389
 ation
 392
 n 393
 394
 rface..... 396


7.3 Sources of Power Dissipation in the RAM Chip..... 402
 7.3.1 Active Power Sources 402
 7.3.2 Data-Retention Power Sources 405
 7.4 Low-Power DRAM Circuits 406
 7.4.1 Active Power Reduction 406
 7.4.2 Data-Retention Power Reduction 412
 7.5 Low-Power SRAM Circuits 413
 7.5.1 Active Power Reduction 413
 7.5.2 Data-Retention Power Reduction 423

8. Ultra-Low-Voltage Memory Circuits 425
 8.1 Introduction 425
 8.2 Design Issues for Ultra-Low-Voltage RAM Circuits 426
 8.2.1 Reduction of the Subthreshold Current..... 426
 8.2.2 Stable Memory-Cell Operation 432
 8.2.3 Suppression of, or Compensation for,
 Design Parameter Variations 433
 8.2.4 Power-Supply Standardization 435
 8.3 Ultra-Low-Voltage DRAM Circuits 437
 8.3.1 Gate Boosting Circuit 439
 8.3.2 The Multi- V_T Circuit 440
 8.3.3 The Gate-Source Back-Biasing Circuit 442
 8.3.4 The Well Control Circuit 456
 8.3.5 The Source Control Circuit 461
 8.3.6 The Well and Source Control Circuit 462
 8.4 Ultra-Low-Voltage SRAM Circuits 463
 8.5 Ultra-Low-Voltage SOI Circuits 466

References 473
Index 489

 

 of data lines [3.3, 3.4]. A C_D of 200 fF



sense amplifiers in a DRAM chip [3.4]

width of a word line made of a resistive material with a large number of divisions has been determined to be a significant area penalty. In the 64 Kb generation, the word-line pitch was short and the speed requirement was high, as shown in Fig. 3.40a [3.9], poly-Si was replaced by a lower-

resistance polycide, in order to double or quadruple the number of memory cells to be driven. To further reduce the RC delay, a poly-Si or polycide word line strapped with a low-resistance aluminum line in each string of 64–128 cells [3.17], as shown in Fig. 3.40b, has been widely accepted in commercial chips since the 1 Mb generation. In the 64 Mb generation, even a hybrid division of the two types shown in Fig. 3.40 has been proposed. However, the aluminum-strapped word-line structure suffers from some drawbacks. It becomes difficult to achieve fine patterning of aluminum at a tight pitch of word lines on a hilly surface, while still connecting to the poly-Si line at the bottom, as the memory cell is miniaturized. In addition, even the word-line structure starts to create quite a large RC delay as many memory cells are connected to a word or subword line. A multidivided word-line scheme using a hierarchical word-line structure [3.18, 3.19], as shown in Fig. 3.25, solves these problems, and is discussed later in detail.

 


Fig. 3.40. Reductions in word-line delay [3.4, 3.9, 3.17]. (a) 64 Kb–256 Kb. 64 Kb: poly-Si ($30 \Omega/\square$), 64 data-line pairs per WL. 256 Kb: polycide ($1\text{--}5 \Omega/\square$), 256 data-line pairs per WL. (b) 1 Mb and beyond: poly-Si ($50 \Omega/\square$), Al ($0.1 \Omega/\square$)

3.6 Read and Relevant Circuits

3.6.1 The Address Buffer

In the NMOS era of the 16–256 Kb generations, a differential address buffer using an on-chip reference voltage [3.14] was widely used. Since the 1 Mb

 


Fig. 3.41. The $\overline{\text{RAS}}$ clock buffer [3.21]

generation, various simple CMOS address buffers have been proposed. In principle, the same circuit configuration is applicable to both the row and column address buffers. Recently, however, a high-speed column address buffer has been especially important to enhance the data throughput by shortening the column address access time t_{AA} , which is dominated by the address buffer (about 40% of t_{AA} [3.20]).

Figure 3.41 shows a typical $\overline{\text{RAS}}$ -clock buffer [3.21] to control the row address buffers. To discriminate between the TTL logic levels of over 2.4 V or below 0.8 V for an input $\overline{\text{RAS}}$ signal, the logical threshold voltage is adjusted to be about 1.6 V by tuning the channel-width ratios of the NMOS and the PMOS at the first input stage. A multistage CMOS circuit controls the row internal circuits, using pulses with differing polarities and delays.

Figure 3.42 shows an address buffer that features a cross-coupled differential amplifier [3.21]. It enables an almost constant speed due to a differential circuit configuration, independently of the power-supply noise. Address buffers consisting of inverters, similar to the above $\overline{\text{RAS}}$ buffer, have also been widely accepted. In general, however, the operation of inverter-type buffers is susceptible to power-supply noise [3.20]. For example, as soon as the input logic signals to many buffers are simultaneously switched to the other logic state so that the ground (V_{SS}) line voltage is instantaneously raised and maximized, the speed of each buffer is degraded, with a reduced NMOS gate-source voltage. For a 64 Mb design [3.20], a simultaneous switching of 13 address buffers caused a V_{SS} noise of 0.4 V and a speed difference of 2.3 μs between the inverter and cross-coupled types, although the difference depended on the quality of the V_{SS} layout. In the figure, the input voltage of address A_i is compared with a reference V_{REF} (1.6 V) to discriminate between a high logic level (H) and a low logic level. The resultant differential signal developed between N_1 and N_2 is quickly amplified to a full V_{DD} by the cross-coupled amplifier, as a result of the application of $\overline{\text{RAS}}_2$. After that, the complementary addresses a_i and \overline{a}_i are generated by the application of $\overline{\text{RAS}}_4$ to address latches (ALCs). Note that during standby periods (i.e. $\overline{\text{RAS}}$: H) both a_i and \overline{a}_i are kept low and there is no current path in the buffer.

 


Fig. 3.42

Figur
although
address c
pulses ge
ATD pul
as to cor
sition is
the I/O
the trans
without
can be c
amplifier

address
input

Fig. 3.
buffers

 
 


Fig. 3.42. The cross-coupled address buffer [3.21]

ffers have been proposed. In icable to both the row and co-1-speed column address buffer ata throughput by shortening minated by the address buffer

ffer [3.21] to control the row TL logic levels of over 2.4 V or l threshold voltage is adjusted ratios of the NMOS and the MOS circuit controls the row larities and delays.

tures a cross-coupled different- ant speed due to a differential ver-supply noise. Address buf- re RAS buffer, have also been ration of inverter-type buffers example, as soon as the input ly switched to the other logic is instantaneously raised and aded, with a reduced NMOS [0], a simultaneous switching 4 V and a speed difference of he figure, the input voltage of 1.6 V) to discriminate between e resultant differential signal ied to a full V_{DD} by the cross- on of \overline{RAS}_2 . After that, the ed by the application of \overline{RAS}_4 standby periods (i.e. \overline{RAS} : H) rent path in the buffer.

Figure 3.43 shows a typical address transition detector (ATD) [3.22], although the variations are shown in Fig. 7.18. Exclusive OR of a_0' and the address delayed by τ generates a short pulse every a_0' transition. All the short pulses generated from all the address input transitions are summed up to one ATD pulse, EQ. Thus, an ATD pulse is generated at any address transition so as to control internal circuits instead of external clocks. If any address transition is quickly detected by ATD and the resultant ATD signal precharges the I/O line in advance, a data line will be selected using addresses just after the transition, so that a data on the data line is outputted on the I/O line without waiting for the I/O precharging. Thus, a long I/O precharging time can be concealed. The ATD signal reduces the power dissipation of main amplifier by cutting the dc current during periods when it is not needed.

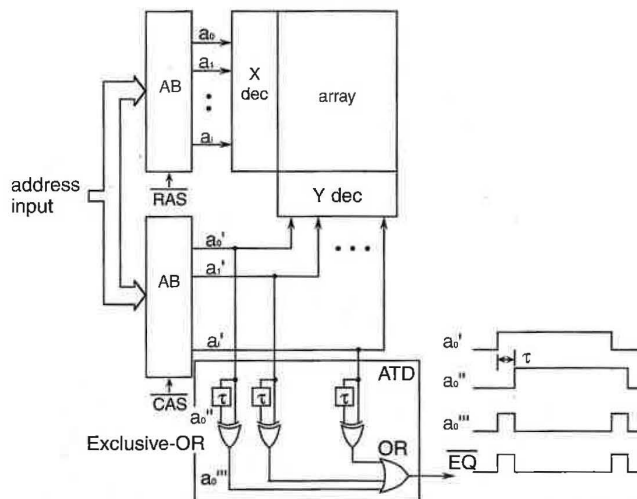


Fig. 3.43. The address transition detector (ATD) scheme [3.22]. AB, address buffers

3.6.2 The Address Decoder

Major concerns for the address-decoder block are power dissipation, speed, and area, because the block includes a huge number of circuits and occupies quite a large segment of the chip.

There are two kinds of decoder; row decoders and column decoders. In DRAM design, unlike SRAM designs, the circuit configurations of the two are totally different. Each row decoder must be a dynamic circuit, while each column decoder can be a static circuit, as explained previously. Note that to precharge all the row decoders without any dc current path, all of the complementary addresses are fixed at a low level during a precharge period, as shown in Fig. 3.42.

Figure 3.44 shows dynamic and static decoders, exemplified by two-bit address signals. There are two kinds of dynamic decoder in DRAM applications; NOR and NAND decoders. First, all of the output nodes (X_0 - X_3) are precharged to V_{DD} by transistors Q_P , while keeping all addresses low. Then, according to the succeeding valid address signals, the output nodes are discharged or kept high. Obviously, in NOR decoders all output nodes except for a selected one are discharged, while in NAND decoders all output nodes except for a selected one are kept high. Thus, NOR decoders suffer from a drawback of the large charging and discharging power. The power increases with memory capacity, because an increased number of the nodes - for example, a few thousands, for multimegabit DRAMs - is involved. On the other hand, in NAND decoders only one node is discharged or charged up, independently of memory capacity. NAND decoders, however, suffer the drawback of a slower speed, because the node is discharged by serially connected (i.e. stacked) transistors. The number of stacked transistors is also limited by the body effect of the transistor. Static NAND decoders for the column are simple, as shown in Fig. 3.44c.

Figure 3.45 shows applications of dynamic decoders to the row and static decoders to the column. In dynamic decoders, a word line WL is activated by an RX pulse that is applied after the decoder output X_i has been settled. In the selected decoder, the Q_W gate-drain (i.e. RX terminal) capacitance C_{GD} is large, because the Q_W gate stays at the high level of $V_{DD} - V_T$. Thus, an RX pulse positively going from 0 V to V_{DD} can boost the Q_W gate voltage. The boost ratio is large, because a diode Q_D isolates the Q_W gate from the node X_i capacitance. Due to the resulting boosted gate voltage, to higher than $V_{DD} + V_T$, the word line is quickly driven to V_{DD} . In the non-selected decoders, an RX pulse application never raises the Q_W gate voltages, since the gate voltages are 0 V and thus their C_{GD} values are almost zero. For NOR decoders, even the heavily capacitive Q_W gate is quickly discharged by at least one transistor of the decoder. For NAND decoders, however, to accomplish rapid decoding, Q_W is driven with the help of a small CMOS inverter, whose input capacitance is small enough to be quickly driven even by stacked transistors. Despite the area penalty, the inverter added to each

 
 


Fig. (a) I
deco
reasc
ders

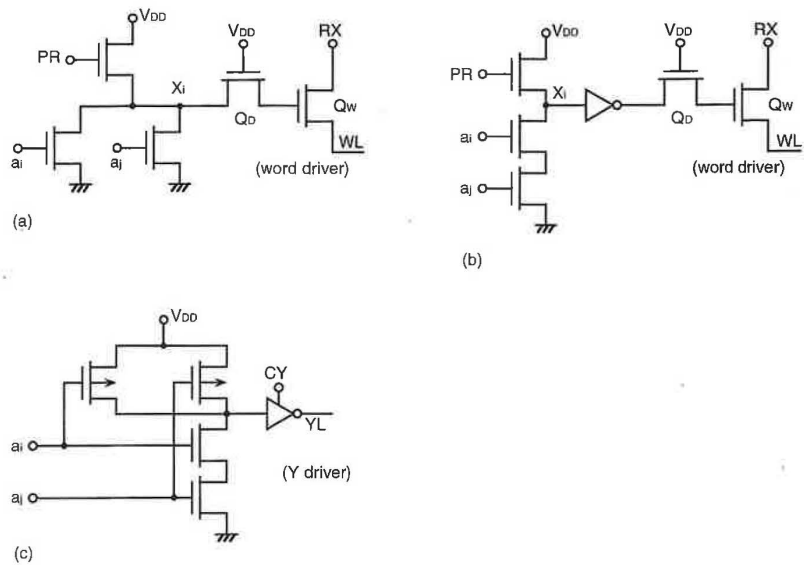


Fig. 3.45. Applications of decoders to word and column drivers [3.4]. (a) Dynamic NOR; (b) dynamic NAND; (c) static NAND

power. Even for a small memory capacity chip of 1 Mb, CMOS NAND decoders have reduced the decoder power down to 4% of that needed for NMOS NOR decoders [3.7, 3.23] as shown in Fig. 3.17. However, to improve the performance of CMOS NAND decoders further, it is essential to reduce the number of stacked transistors. This is realized by predecoding schemes [3.21], as follows.

A predecoding scheme achieves a faster decoding and area reduction of a decoder while reducing the number of stacked transistor in a CMOS NAND decoder. In addition, it reduces the input capacitance and the necessary address input lines of the decoder. Figure 3.46 compares predecoding schemes [3.4]. Direct decoding, 2 bit predecoding, and 3 bit predecoding are shown in Figs. 3.46a-c, respectively. A circle in the figures denotes a transistor connection. For example, when a high level is applied to a_0 and a_1 in Fig. 3.46a, decoders X_0 , X_4 , and X_8 are selected as a result of NAND decoding. Each 2 bit predecoder can select one of four address input lines coming to the decoders by using two sets of complementary addresses from two address buffers, while each 3 bit predecoder can select one of eight address input lines by using three sets of complementary addresses. Here, let us cite an example of a total external address bits of 6 bits (A_0 - A_5). The numbers of address lines to the decoders for direct decoding, 2 bit decoding, and 3 bit decoding are 12, 12, and 16, respectively. The numbers of transistors

 
 


Fig. 3.46. Predecoding [3.4]. (a) no predecoding; (b) 2-bit predecoding; (c) 3-bit predecoding

drivers [3.4]. (a) Dynamic

CMOS NAND decoder that needed for NMOS. However, to improve the is essential to reduce the decoding schemes [3.21],

and area reduction transistor in a CMOS capacitance and the necessary compares predecoding and 3 bit predecoding are the figures denotes a transistor is applied to a_0 and a_1 as a result of NAND four address input lines elementary addresses from select one of eight address addresses. Here, let us cite (A_0-A_5) . The numbers ing, 2 bit decoding, and the numbers of transistors

connected to each address line are 32, 16, and 8, and the numbers of transistors consisting of each decoder are six, three, and two, in the same order. Hence, the predecoding schemes achieve a higher speed with reduction of the address-line capacitance and the number of stacked transistors needed for each NAND decoder, given an acceptable number of address lines. They also reduce the decoder area. The resulting improvement in speed offsets an additional delay caused by the predecoders. Here, predecoding schemes with more than 4 bits are not practical because of a rapid increase in the number of address lines.

Figure 3.47 shows a reduction in the delay of an address line [3.24], which is an example of the buffer insertions shown in Fig. 3.20. Quite a long delay time is developed, despite the aluminum address line, because the line becomes resistive and capacitive due to fine patterning, and is loaded by the distributed gate capacitances of the decoder transistors, as shown in Fig. 3.47a. However, the delay is reduced by the multidivided decoder shown in Fig. 3.47b. The resulting block decoder is driven by a buffer. Each block is constructed so as to correspond to a subarray and only one block is selectively activated by the subarray activation pulse Φ_1 .

3.6.3 The Word Driver

A word driver needs to be designed carefully – more so than a column driver – because its load has the following unique features:

1. *A Boosted Word Voltage.* The need for a boosted word voltage, for full write and read operations, means that row decoders and word drivers


 


Fig. 3.47. The delay reduction of an address line running on decoders (*upper*) by insertion of buffers (*lower*) [3.4, 3.24]

have complicated designs. On the other hand, column-relevant circuits, such as column decoders and drivers, do not need any boosting. Even without boosting, an amplified signal voltage from a data line can be transmitted to the I/O line, and a data-input voltage of V_{DD} can be fully transmitted from the I/O line to the data line with the help of the CMOS sense amplifier.

 2. *A Large Word-Line Capacitance and Resistance.* The electrical characteristics of a word line differ from those of column line YL in the shared Y decoder scheme. Word-line capacitance is quite heavy, because of connections with many memory cells. On the other hand, column-line capacitance is light, because a small number of transistors, equal to the number of data-line divisions (i.e. q in Fig. 3.14), are connected to a YL line. Thus, a larger word driver is needed. As for line resistance, there is also a large difference between the two. A word line made of poly-Si or polycide is resistive for a folded data-line cell, while a column line is made of aluminum.
3. *Loss of Stored Information.* If the stored charges of a non-selected cell are allowed to escape to a data line through the transfer transistor, the refresh time or S/N ratio of the cell is degraded, as discussed in Chap. 4. Thus, noise suppression is essential on non-selected word lines. Moreover, to avoid loss of stored information, data-line precharging must be started after completely turning off the word pulse. Such considerations are not



ning on decoders (*upper*) by

, column-relevant circuits, need any boosting. Even from a data line can be voltage of V_{DD} can be fully with the help of the CMOS

nce. The electrical charac- column line YL in the sha- is quite heavy, because of e other hand, column-line of transistors, equal to the 4), are connected to a YL for line resistance, there is rd line made of poly-Si or while a column line is made

rages of a non-selected cell the transfer transistor, the d, as discussed in Chap. 4. cted word lines. Moreover, recharging must be started uch considerations are not

needed for the column. Here, an explanation of the column driver is omitted in what follows, because the driver is almost the same as in Fig. 3.45.

A Basic Word Driver. Figure 3.48 shows the basic unit of conventional word drivers [3.13, 3.21, 3.23]. Each word line is divided into two, to reduce word-line delay (see Fig. 3.40), and the resulting divided word line has its own word driver, Q_W . Since a CMOS NAND decoder cannot be placed at a tight word-line pitch, it is shared with two sets (left and right) of four word drivers, although only the right section is shown in the figure. Address signals X_j and X_k are inputted from 2-bit predecoders to the decoder. Each of the four word drivers selected by the decoder is selectively driven by decoded row select lines RX (RX_0 – RX_3), enabling the corresponding word line to be driven. The RX drivers in Fig. 3.48b provide a boost word voltage to one of RXs as a result of two-address bit (a_0, a_1) decoding, as follows. At first, node WDL is precharged almost to V_{DD} during the precharge period (i.e. $\overline{RP} : H$) and all address signals and thus all RX lines are fixed at 0 V. When the addresses have been valid after starting activation with $\overline{RP} : L$, a clock Φ_B generated by the \overline{RAS} buffer is applied, so that only one selected RX line is driven at a high enough voltage, boosted by C_B .

The latch transistor Q_L in the word driver suppresses noise on each non-selected word line while fixing the word line at 0 V as follows. During pre-charge period all of the non-selected word lines are fixed at 0 V because the Q_L s are turned on. When one set of four word lines is selected by a decoder, the gate voltages of the corresponding four Q_L s are changed from V_{DD} to 0 V and the Q_L s are thus cut off. At this moment, the gate voltages of the corresponding four word-driver transistors Q_W are increased from 0 V to $V_{DD} - V_T$. During this process, the word lines are not at any floating voltage that easily couples noise to the lines, because the four word lines WL_0 – WL_3 are fixed at the voltages (i.e. 0 V) of RX_0 – RX_3 through the respective Q_W s. After that, for example, RX_0 is selected and a V_{DH} pulse is sent to WL_0 , fixing the remaining non-selected word lines at 0 V. Note that all of the word lines belonging to the non-selected decoders continue to be fixed at 0 V, because the Q_L s are turned on. Thus, the noise coupled to each non-selected word line, even during signal amplifications performed at a large voltage swing of V_{DD} or a half- V_{DD} on data lines, can be sufficiently suppressed. To further reduce noise on the word lines, another scheme of an additional transistor, which is controlled by address signals, on each word line has been proposed [3.25].

High-speed driving of the RX line is also important, because a long delay is developed by the heavy loading of the large Q_W s and the long RX line running along a memory array. An RX driver placed at the end of the subarrays in Fig. 3.49a increases the line delay. However, a RX driver for each subarray in Fig. 3.49b [3.26], which is similar to the scheme in Fig. 3.47, shortens the delay. In this scheme, only one subarray is selected by the address signals and a subarray selection signal Φ_i . The node WDL of the RX line in Fig. 3.48 corresponds to a line WDL that is common to a number of subarrays in

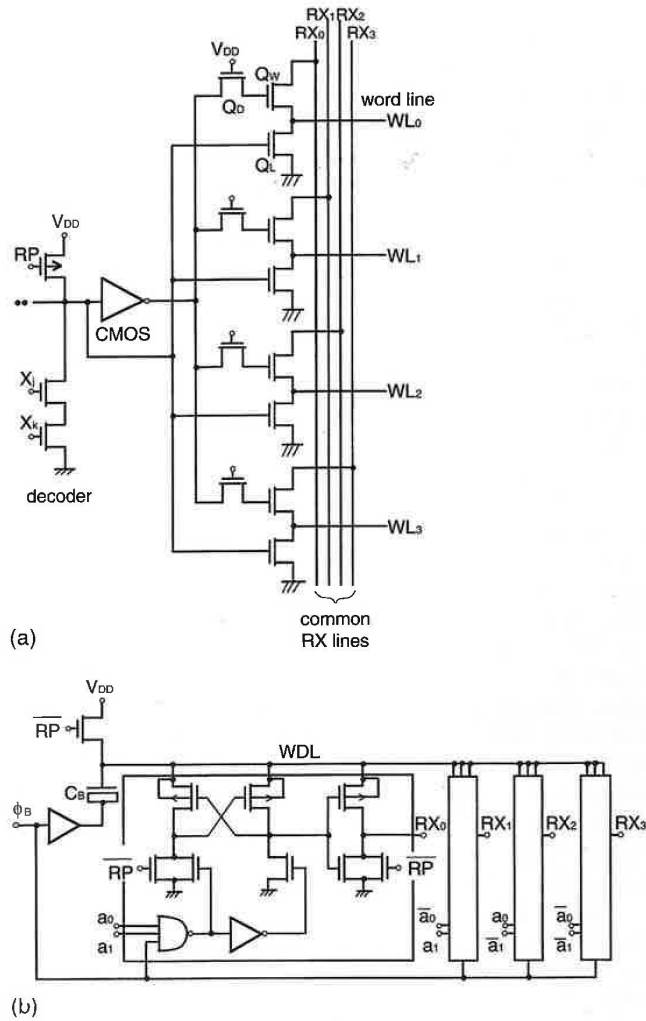


Fig. 3.48. The configuration of word drivers and relevant circuits [3.4, 3.13, 3.21, 3.23]. (a) Word drivers; (b) RX drivers

Fig. 3.49b. As soon as \overline{RAS} activation starts, the heavily capacitive WDL line is boosted. After that, the addresses are valid and a subarray is thus selected so that a V_{DH} pulse is applied to a common RX line belonging to the subarray. Consequently, the boosting time of the WDL line can be concealed and the RX line that the RX driver must drive is shortened to one subarray. Thus, the driving speed is improved.


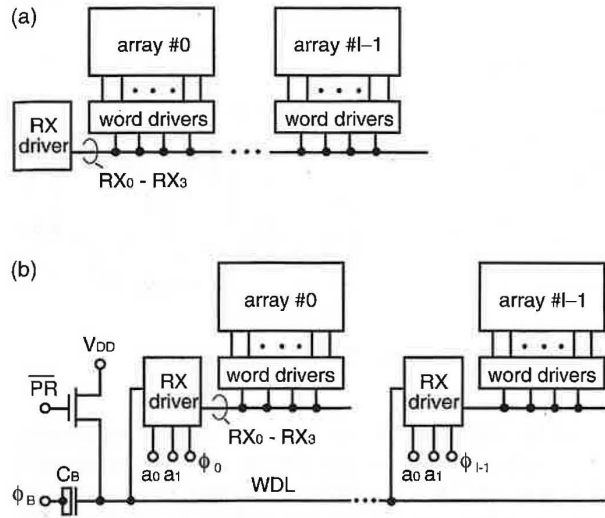


Fig. 3.49. Driving schemes of RX lines [3.4, 3.26]. (a) Direct driving of RX lines; (b) selective driving of multidivided RX lines

The Voltage-Stress Relaxed Word Driver. This is the word driver that must operate at the highest voltage in a DRAM chip. Therefore, many circuits have been proposed to relax the voltage stress applied at normal and/or burn-in test operations. They are categorized as the use of PMOS transistor in the word driver instead of NMOS transistor, the changing of the boost ratio according to V_{DD} , and the use of a well-regulated boosted dc voltage.

The PMOS Output Transistor [3.4]. The stress voltages applied to the word-driver output transistor are high, because the word-line voltage must be higher than $V_{DD} + V_{TM}$ (where V_{TM} is the threshold voltage of the memory-cell transistor). However, the PMOS transistor can relax the voltage stress, ensuring high reliability, as follows. For the NMOS transistor in Fig. 3.50a, in order that an increased voltage $V_{DH} (> V_{DD} + V_{TM})$ boosted by C_B at the drain (i.e. RX) is available at the source (i.e. word line), the gate voltage must be boosted to a level that is somewhat higher than $V_{DH} + V_{TD}$ by utilizing C_{GD} . Here, V_{TD} is threshold voltage of the output transistor, which is usually smaller than V_{TM} due to the narrow channel effect, and so on. This dual boosting raises the gate voltage to a considerably high voltage. The PMOS output transistor in Fig. 3.50b does not need dual boosting, since the activation is performed only by lowering the gate voltage from V_{DH} to 0V. Hence, the PMOS transistor reduces the gate voltage by at least V_{TD} . In actual practice, the difference in gate voltage between the PMOS and NMOS transistors becomes larger, due to variations in the boost ratio at the

 

rs and relevant circuits

e heavily capacitive WDL
id and a subarray is thus
n RX line belonging to the
VDL line can be concealed
shortened to one subarray.


 


Fig. 3.50. Word boosting for NMOS (a) and PMOS (b) drivers [3.4].

NMOS transistor caused by variations in the V_{DD} and fabrication-process. The PMOS transistor may allow the gate-source voltage to be large enough to achieve a faster speed despite the lower conductance of the PMOS, compared to the NMOS transistor, in which the gate-source voltage is usually insufficient. Moreover, for lower- V_{DD} operation, the boost ratio must be larger, since there is a minimal threshold voltage for V_{TD} to prevent a degradation of the V_{DH} level caused by a subthreshold current; this is discussed in Chap 8. Thus, the PMOS transistor has been widely used instead of the NMOS transistor.

The Varied Boost-Ratio Driver. There are some operating modes in which MOS devices must not break down even when the operating voltage varies widely. These are the burn-in test mode, which ensures device reliability by applying an increased voltage, and battery operations, which require a wide voltage margin. Figure 3.51a shows a word driver for boosting a well-regulated low-voltage V_{DL} , which is lowered from V_{DD} ($= 3.3\text{ V}$) using an on-chip voltage down-converter [3.27]. The node WDL, which corresponds to WDL in Figs. 3.48 and 3.49, is boosted by activating $\bar{\phi}_B$ to a low level after it has been precharged to V_{DL} . An excessively high stress voltage is applied to devices in the burn-in test mode, since the boost ratio is almost constant. A voltage down-converter dedicated to the test mode relaxes the stress voltage in a high-voltage region as follows. The reference voltage V_{RN} increases when V_{DD} is increased. Eventually, however, it is clamped at a voltage of two MOS-diode drops and thus V_{DL} becomes equal to $r_1 V_{RN}$. Here, r_1 is a resistance division ratio. Although V_{DL} increases slightly with V_{DD} because of a slight increase in the diode drops caused by the increased diode current, V_{DL} is determined in turn by the other voltage down-converter for the burn-in mode. The converter generates a boosted voltage, monitoring the threshold voltage V_{TM} of the memory-cell transistor as follows. The input voltage V_{RB} of the comparator is given by

 

IOS (b) drivers [3.4].

V_{DD} and fabrication-process. The gate voltage to be large enough to overcome the resistance of the PMOS, compared to the NMOS. The source voltage is usually insufficient. The boost ratio must be larger, since the boost ratio must be larger, since to prevent a degradation of the device is discussed in Chap 8. Thus, instead of the NMOS transistor.

Some operating modes in which the operating voltage varies with V_{DD} ensures device reliability by variations, which require a wide range for boosting a well-regulated V_{WDL} ($= 3.3\text{ V}$) using an on-chip boost circuit, which corresponds to WDL being $\bar{\phi}_B$ to a low level after it is high stress voltage is applied to the boost ratio is almost constant. In burn-in mode relaxes the stress voltage. The gate voltage V_{RN} increases when operated at a voltage of two MOSFETs V_{RN} . Here, r_1 is a resistance in series with V_{DD} because of a slight increase in diode current, V_{DL} is a voltage divider for the burn-in mode. Monitoring the threshold voltage V_{TM} . The input voltage V_{RB} of the

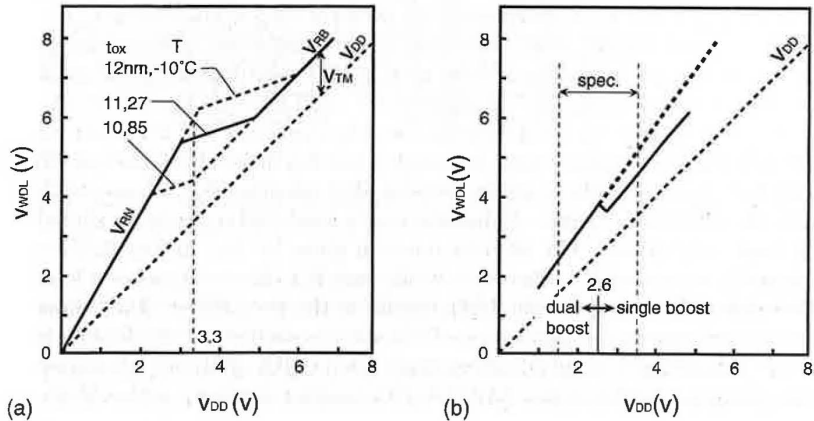
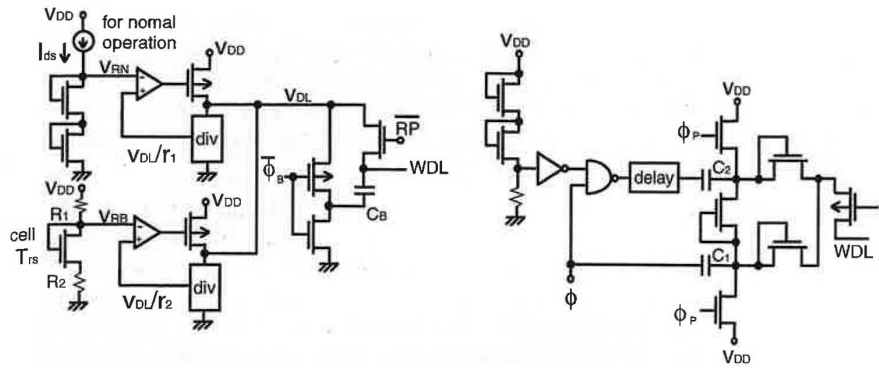


Fig. 3.51. Varied boost ratio word drivers [3.4, 3.27, 3.28]. Switching of raised voltages (a) and boost number (b)

$$V_{RB} = \frac{R_2}{R_1 + R_2} \left\{ V_{DD} + \frac{R_1 + R_2}{R_2} V_{TM} \right\},$$

$$\therefore V_{WDL} = BV_{DL} = B(r_2 V_{RB}),$$

where $V_{DD} \gg V_{TM}$, r_2 is a resistance division ratio, and B is a boost ratio. Hence,

$$V_{WDL} = V_{DD} + r_2 B V_{TM},$$

for $B r_2 R_2 / (R_1 + R_2) = 1$. An additional voltage $r_2 B V_{TM}$ is thus V_{TM} for $r_2 B = 1$, which minimizes the necessary boosted voltage. The boosted word voltage V_{WDL} can track variations of V_{TM} because a memory-cell transistor is used.

Figure 3.51b shows a voltage up-converter for a battery operation [3.28]. It features dual boosting in the low- V_{DD} region, but single boosting in the

high- V_{DD} region. Thus, a raised S/N ratio even in the low- V_{DD} region, and the suppression of an excessive stress voltage in the high- V_{DD} region are obtained. This is essential to ensure the wide operational range of $V_{DD} = 2.6 \pm 1$ V that is inherent in battery operations. A voltage up-converter [3.29] described in Chap. 5 is a variation of this concept, in which the boost ratio is almost continuously changed over a wide range of V_{DD} values.

The Raised dc Supply-Voltage Driver [3.29–3.32]. A quasi-static supply-voltage (V_{DH}) generator, discussed in Chap. 5, would not only minimize the stress voltage to devices, but also enable fast operation, as follows. Figure 3.52a shows a word driver using the dc power supply V_{DH} . One decoder is shared with four word lines through transistors controlled by the decoded signals ϕ_{X0} – ϕ_{X3} . At the beginning of activation, the non-selected three of the four signals, which were all at V_{DD} , go down to 0 V while the remaining selected one goes to V_{DD} . After that, the decoder output goes down to 0 V and the selected PMOS word transistor is thus turned on, with a change in the gate voltage from V_{DH} to 0 V, so that the word line is activated at V_{DH} . During this process, the remaining three word lines are latched at 0 V. This driver eliminates the need to drive a heavily capacitive RX line and thus eventually realizes a higher speed, although it needs a little additional time to ensure the sequence of the enabling decoder after enabling ϕ_{X_i} . Figure 3.52b shows the other word driver. A decoder and a level shifter are both shared with four word drivers. The decoder function given by ϕ_{X_i} in Fig. 3.52a is replaced by a decoded RX scheme, in which each RX driver comprises a level shifter and an inverter (see Fig. 3.54), similar to the word driver. The timing requirement between the application of RX and the enabling of the decoder is relaxed, permitting even an advanced application of RX. Without a boosting effect, which is available at the NMOS word transistor combined with a MOS-

 


Fig. 3.52. A word driver using a raised dc supply voltage [3.4, 3.29–3.32]. (a) Static driver; (b) dynamic driver

dec. driver (a)


M¹ dec. driver (b)

Fig. 3.18

diode is du
The ved
rema
show
word
is be
num
in th
incre
(
conc
sche
subv
cont
activ
RX₁
the s
poly
a hu

in the low- V_{DD} region, and the high- V_{DD} region are obtained. range of $V_{DD} = 2.6 \pm 1$ V that γ -converter [3.29] described in which the boost ratio is almost γ values.

 3.32]. A quasi-static supply-5, would not only minimize fast operation, as follows. Fewer supply V_{DH} . One decoder outputs controlled by the decoded input, the non-selected three of which output goes down to 0 V as turned on, with a change the word line is activated at word lines are latched at 0 V. ly capacitive RX line and thus needs a little additional time to er enabling Φ_{Xi} . Figure 3.52b, level shifter are both shared given by Φ_{Xi} in Fig. 3.52a is h RX driver comprises a level o the word driver. The timing e the enabling of the decoder is on of RX. Without a boosting asistor combined with a MOS-



oltage [3.4, 3.29–3.32]. (a) Static

 
 


Fig. 3.53. The concept behind partial activation of a multidivided word line [3.18, 3.19, 3.33]. (a) No division; (b) multidivision

diode shown in Fig. 3.48, an increased word voltage is quickly outputted. This is due to the use of a V_{DH} level shifter.

The Reduction of Word-Line Delay. Even if word-driver speed is improved by using a PMOS transistor, the need to reduce a large word-line delay remains. Although the aluminum-strapped poly-Si or polycide word line, as shown in Fig. 3.53a, has been popular since the 1 Mb generation, a large RC word-line delay has been prominent in the 64 Mb generation and beyond. This is because of the ever-finer and longer aluminum line and the ever-increasing number of memory cells connected to a word line. Unfortunately, an increase in the number of word-line divisions causes an area penalty, with a resulting increased number of word drivers.

One solution is the hierarchical word-line structure [3.18, 3.19, 3.33], as conceptually shown in Fig. 3.53b. This is an example of the delay reduction scheme in Fig. 3.19d. One word line is divided into several by the small subword-line (SWL) drivers. All of the subword lines in a row are commonly controlled by a main word line (MWL). Therefore, they are simultaneously activated by selecting a main word line and all of the row select lines (RX_0 , RX_1 , etc.). The choice of aluminum lines for MWL and RX would improve the speed of the simple aluminum strapping in Fig. 3.53a, despite poly-Si or polycide subword lines. In simple strapping, a word line is heavily loaded with a huge number of memory cells in a row. The resulting heavy capacitance

develops a long delay even on a low-resistance aluminum line. In this case the total delay is approximately the sum of a large MWL delay and the subword-line delay. On the other hand, in the hierarchical structure a main word line is loaded by only quite a small number of AND logic gates, which is the same as the number of word-line divisions. Considering that the number of memory cells connected to one subword line ranges from 256 to 512, the loading for the main word line is quite light, which enables an extremely small delay compared with the subword-line delay. An RX line also enables a small delay because of the aluminum material. The delay could be further shortened if it is driven by a RX driver located at each data-line division. Eventually, the total delay of the hierarchical structure is almost confined to the subword-line delay. Thus, the delay is less than that for simple strapping.

Figure 3.54 shows an actual hierarchical structure applied to a 256 Mb chip [3.18, 3.19, 3.33]. It relaxes the MWL pitch to one-quarter so that aluminum wiring is enabled even on the top surface of the substrate, and it allows SWL drivers to be placed alternately to meet the tight word-line layout pitch. Eight-row word lines, each of which is divided into a number of subword lines ($SWL_{00}, SWL_{10}, \dots$), are controlled by a set of complimentary main word lines (MWL, \overline{MWL}), which are driven by a row decoder and a set of word drivers. One set of four SWL drivers is located at each end of each subarray. One of four SWL drivers is activated by one of the decoded RX lines from a RX driver. The full use of NMOS transistors realizes a small

 


Fig. 3.54. Hierarchical word-line architecture [3.18, 3.19]