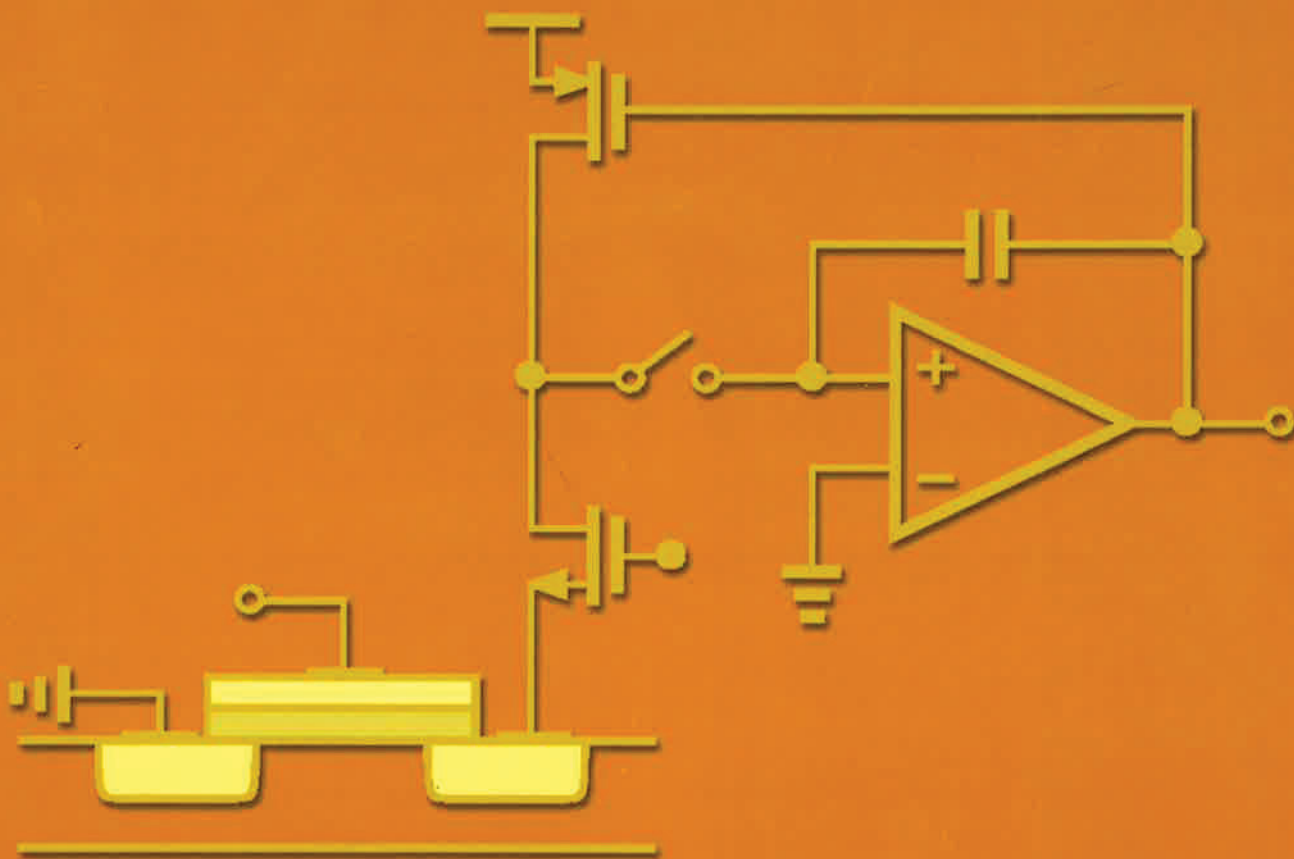


# Design of Analog CMOS Integrated Circuits



Behzad Razavi

Intel 1441

# McGraw-Hill Higher Education

A Division of The McGraw-Hill Companies

## DESIGN OF ANALOG CMOS INTEGRATED CIRCUITS

Published by McGraw-Hill, an imprint of The McGraw-Hill companies, Inc. 1221 Avenue of the Americas, New York, NY, 10020. Copyright © 2001, by The McGraw-Hill Companies, Inc. All rights reserved. No part of this publication may be reproduced or distributed in any form or by any means, or stored in a database or retrieval system, without the prior written consent of The McGraw-Hill Companies, Inc., including, but not limited to, in any network or other electronic storage or transmission, or broadcast for distance learning. Some Ancillaries, including electronic and print components, may not be available to customers outside the United States.

This book is printed on acid-free paper.

1 2 3 4 5 6 7 8 9 0 FGR/FGR 90 9 8 7 6 5 4 3 2 1 0

ISBN 0-07-238032-2

Vice president/Editor-in-chief: *Kevin T. Kane*

Publisher: *Thomas Casson*

Sponsoring editor: *Catherine Fields*

Developmental editor: *Michelle L. Flomenhoft*

Senior marketing manager: *John T. Wannemacher*

Project manager: *Jim Labeots*

Production supervisor: *Gina Hangos*

Senior designer: *Kierd Cunningham*

New media: *Phillip Meek*

Compositor: *Interactive Composition Corporation*

Typeface: *10/12 Times Roman*

Printer: *Quebecor Printing Book Company/Fairfield*

### Library of Congress Cataloging-in-Publication Data

Razavi, Behzad.

Design of analog CMOS integrated circuits / Behzad Razavi.

p. cm.

ISBN 0-07-238032-2 (alk. paper)

1. Linear integrated circuits—Design and construction. 2. Metal oxide semiconductors, Complementary. I. Title.

TK7874.654. R39 2001

621.39'732—dc21

00-044789

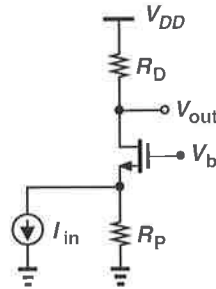


Figure 3.49

The output impedance is simply equal to

$$R_{out} = \{[1 + (g_m + g_{mb})r_O]R_P + r_O\} \parallel R_D. \tag{3.116}$$

(3.114)

### 3.5 Cascode Stage

As mentioned in Example 3.10 the input signal of a common-gate stage may be a current. We also know that a transistor in a common-source arrangement converts a voltage signal to a current signal. The cascade of a CS stage and a CG stage is called a “cascode”<sup>1</sup> topology, providing many useful properties. Fig. 3.50 shows the basic configuration:  $M_1$  generates a small-signal drain current proportional to  $V_{in}$  and  $M_2$  simply routes the current to  $R_D$ .

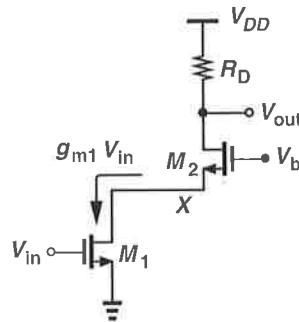


Figure 3.50 Cascode stage.

We call  $M_1$  the input device and  $M_2$  the cascode device. Note that in this example,  $M_1$  and  $M_2$  carry equal currents. As we describe the attributes of the circuit in this section, many advantages of the cascode topology over a simple common-source stage become evident.

First, let us study the bias conditions of the cascode. For  $M_1$  to operate in saturation,  $V_X \geq V_{in} - V_{TH1}$ . If  $M_1$  and  $M_2$  are both in saturation, then  $V_X$  is determined primarily by

<sup>1</sup>The term *cascode* is believed to be the acronym for “cascaded triodes,” possibly invented in vacuum tube days.

(3.115)

$V_b$ :  $V_X = V_b - V_{GS2}$ . Thus,  $V_b - V_{GS2} \geq V_{in} - V_{TH1}$  and hence  $V_b > V_{in} + V_{GS2} - V_{TH1}$  (Fig. 3.51). For  $M_2$  to be saturated,  $V_{out} \geq V_b - V_{TH2}$ , that is,  $V_{out} \geq V_{in} - V_{TH1} + V_{GS2} -$

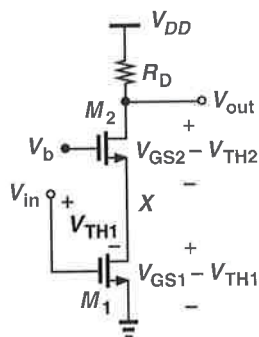


Figure 3.51 Allowable voltages in cascode stage.

$V_{TH2}$  if  $V_b$  is chosen to place  $M_1$  at the edge of saturation. Consequently, the minimum output level for which both transistors operate in saturation is equal to the overdrive voltage of  $M_1$  plus that of  $M_2$ . In other words, addition of  $M_2$  to the circuit reduces the output voltage swing by at least the overdrive voltage of  $M_2$ . We also say  $M_2$  is “stacked” on top of  $M_1$ .

We now analyze the large-signal behavior of the cascode stage shown in Fig. 3.50 as  $V_{in}$  goes from zero to  $V_{DD}$ . For  $V_{in} \leq V_{TH1}$ ,  $M_1$  and  $M_2$  are off,  $V_{out} = V_{DD}$ , and  $V_X \approx V_b - V_{TH2}$  (if subthreshold conduction is neglected) (Fig. 3.52). As  $V_{in}$  exceeds  $V_{TH1}$ ,  $M_1$  begins to draw current, and  $V_{out}$  drops. Since  $I_{D2}$  increases,  $V_{GS2}$  must increase

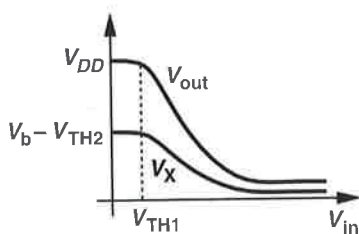


Figure 3.52 Input-output characteristic of a cascode stage.

as well, causing  $V_X$  to fall. As  $V_{in}$  assumes sufficiently large values, two effects occur: (1)  $V_X$  drops below  $V_{in}$  by  $V_{TH1}$ , forcing  $M_1$  into the triode region; (2)  $V_{out}$  drops below  $V_b$  by  $V_{TH2}$ , driving  $M_2$  into the triode region. Depending on the device dimensions and the values of  $R_D$  and  $V_b$ , one effect may occur before the other. For example, if  $V_b$  is relatively low,  $M_1$  may enter the triode region first. Note that if  $M_2$  goes into deep triode region,  $V_X$  and  $V_{out}$  become nearly equal.

Let us now consider the small-signal characteristics of a cascode stage, assuming both transistors operate in saturation. If  $\lambda = 0$ , the voltage gain is equal to that of a common-source stage because the drain current produced by the input device must flow through the cascode device. Illustrated in the equivalent circuit of Fig. 3.53, this result is independent of the transconductance and body effect of  $M_2$ .

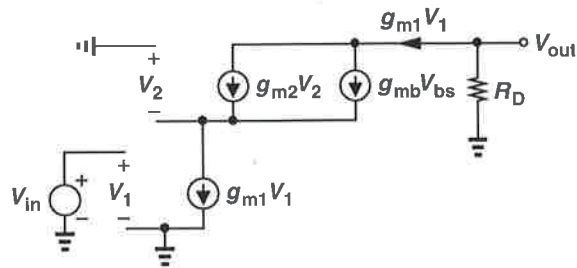


Figure 3.53 Small-signal equivalent circuit of cascode stage.

Example 3.14

Calculate the voltage gain of the circuit shown in Fig. 3.54 if  $\lambda = 0$ .

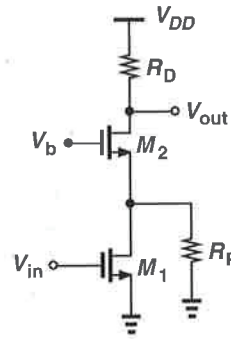


Figure 3.54

Solution

The small-signal drain current of  $M_1$ ,  $g_{m1}V_{in}$ , is divided between  $R_P$  and the impedance seen looking into the source of  $M_2$ ,  $1/(g_{m2} + g_{mb2})$ . Thus, the current flowing through  $M_2$  is

$$I_{D2} = g_{m1}V_{in} \frac{(g_{m2} + g_{mb2})R_P}{1 + (g_{m2} + g_{mb2})R_P} \quad (3.117)$$

The voltage gain is therefore given by

$$A_v = -\frac{g_{m1}(g_{m2} + g_{mb2})R_P R_D}{1 + (g_{m2} + g_{mb2})R_P} \quad (3.118)$$

An important property of the cascode structure is its high output impedance. As illustrated in Fig. 3.55, for calculation of  $R_{out}$ , the circuit can be viewed as a common-source stage with a degeneration resistor equal to  $r_{O1}$ . Thus, from (3.60),

$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{O2}]r_{O1} + r_{O2} \quad (3.119)$$

# Explore Litigation Insights

Docket Alarm provides insights to develop a more informed litigation strategy and the peace of mind of knowing you're on top of things.

## Real-Time Litigation Alerts



Keep your litigation team up-to-date with **real-time alerts** and advanced team management tools built for the enterprise, all while greatly reducing PACER spend.

Our comprehensive service means we can handle Federal, State, and Administrative courts across the country.

## Advanced Docket Research



With over 230 million records, Docket Alarm's cloud-native docket research platform finds what other services can't. Coverage includes Federal, State, plus PTAB, TTAB, ITC and NLRB decisions, all in one place.

Identify arguments that have been successful in the past with full text, pinpoint searching. Link to case law cited within any court document via Fastcase.

## Analytics At Your Fingertips



Learn what happened the last time a particular judge, opposing counsel or company faced cases similar to yours.

Advanced out-of-the-box PTAB and TTAB analytics are always at your fingertips.

## API

Docket Alarm offers a powerful API (application programming interface) to developers that want to integrate case filings into their apps.

## LAW FIRMS

Build custom dashboards for your attorneys and clients with live data direct from the court.

Automate many repetitive legal tasks like conflict checks, document management, and marketing.

## FINANCIAL INSTITUTIONS

Litigation and bankruptcy checks for companies and debtors.

## E-DISCOVERY AND LEGAL VENDORS

Sync your system to PACER to automate legal marketing.