

# An introduction to the Wireless Power Consortium standard and TI's compliant solutions

By **Bill Johns**

*Senior Applications Engineer*

## Introduction

Wireless power is beginning to show great potential in the consumer market. The ability to power an electronic device without the use of wires provides a convenient solution for the users of portable devices and also gives designers the ability to develop more creative answers to problems. This technology's benefits can be seen in the many portable devices, from cell phones to electric cars, that normally operate on battery power.

Inductive coupling is the method by which efficient and versatile wireless power can be achieved. For ease of use and the benefit of both designers and consumers, the Wireless Power Consortium (WPC) has developed a standard (see Reference 1) that creates interoperability between the device providing power (power transmitter, charging station) and the device receiving power (power receiver, portable device). Established in 2008, the WPC is a group of Asian, European, and American companies in diverse industries, including electronics manufacturers and original equipment manufacturers (OEMs). The WPC standard defines the type of inductive coupling (coil configuration) and the communications protocol to be used for low-power wireless devices. Any device operating under this standard will be able to pair with any other WPC-compliant device. One key benefit to this approach is


that it makes use of the coils for communications between the power transmitter and the power receiver. See Figure 1 for a typical application diagram.

## WPC standard for wireless power

Under the WPC standard, "low power" for wireless transfer means a draw of 0 to 5 W. Systems that fall within the scope of this standard are those that use inductive coupling between two planar coils to transfer power from the power transmitter to the power receiver. The distance between the two coils is typically 5 mm. Regulation of the output voltage is provided by a global digital control loop where the power receiver communicates with the power transmitter and requests more or less power. Communication is unidirectional from the power receiver to the power transmitter via backscatter modulation. In backscatter modulation, the power-receiver coil is loaded, changing the current draw at the power transmitter. These current changes are monitored and demodulated into the information required for the two devices to work together.

The WPC standard defines the three key areas of the system—the power transmitter that will supply power, the power receiver that will use the power, and the communications protocol between the two devices. These three areas are explored next.

**Figure 1. Typical wireless-power functional diagram**

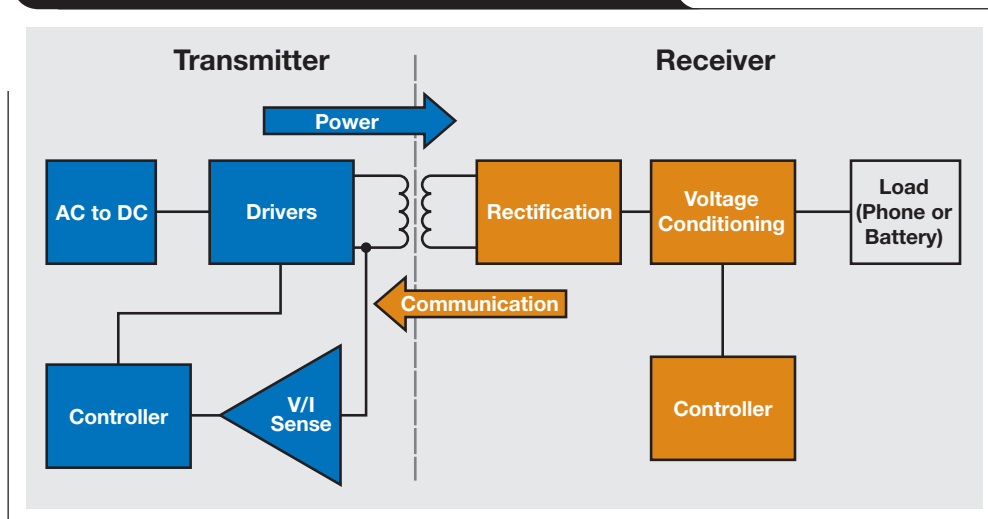

### Power transmitter

The direction of power transfer is always from the power transmitter to the power receiver. The key circuits of the power transmitter are the primary coil, used to transfer power to the power-receiver coil; the control unit for driving the primary coil; and the communications circuit for demodulating the voltage or current from the primary coil. Flexibility of the power-transmitter design is limited to provide consistent power and voltage levels to the power receiver.

The power receiver identifies itself to the power transmitter as a compliant device and also provides configuration information. Once the transmitter initiates power transfer, the power receiver sends error packets to the power transmitter requesting more or less power. The power transmitter stops supplying power upon receiving an “End Power” message, or if no packets are received for more than 1.25 seconds. While no power is being transmitted, the power transmitter enters a low-power standby mode.

The WPC specification allows for both fixed- and moving-coil configurations. A single fixed coil, referred to as type A1, is the solution that Texas Instruments (TI) supports.

The power transmitter, typically a flat surface upon which the user places the power receiver, is connected to the power source. The coils of a WPC-compliant device operate as a resonant half bridge on a 50% duty cycle, with a 19-VDC input ( $\pm 1$  V). If more or less power is needed at the power receiver, the frequency in the coil changes but stays between 110 and 205 kHz, depending on power demands.

### Power receiver

The power receiver is typically a portable device. The key circuits of the power receiver are the secondary coil, used to receive power from the power-transmitter coil; the rectification circuit, used to convert AC to DC; the power-conditioning circuit, which buffers the unregulated DC into regulated DC; and the communications circuit, which modulates the signal to the secondary coil. The power receiver is responsible for all communications of its authentication and power requirements, as the power transmitter is only a “listener.”

While design of the power transmitter is restricted to keep it WPC-compliant, much more freedom is permitted for designing the power receiver. The coil dimension of the power receiver can be adjusted to meet the device's form factor. The coil voltage at the power receiver is full-wave rectified, with a typical efficiency of 70% for a 5-V, 500-mA output. Because communication between the two devices is unidirectional, the WPC selected the power receiver to be the “talker.” Inductive power transfer works by coupling a magnetic field from primary to secondary coils. Uncoupled field lines rotate around the primary coil and do not represent loss as long as the field lines don't couple a parasitic load (for example, eddy-current loss in metal).

### Communications protocol

The communications protocol includes analog and digital pinging; identification and configuration; and power transfer. A typical start-up sequence that occurs when a power receiver is placed on a power transmitter proceeds as follows:

1. An analog ping from the power transmitter detects the presence of an object.
2. A digital ping from the power transmitter is a longer version of the analog ping and gives the power receiver time to reply with a signal-strength packet. If the signal-strength packet is valid, the power transmitter keeps power on the coil and proceeds to the next phase.
3. During the identification and configuration phase, the power receiver sends packets that identify it and that provide configuration and setup information to the power transmitter.
4. In the power-transfer phase, the power receiver sends control error packets to the power transmitter to increase or decrease the power supply. These packets are sent approximately every 250 ms during normal operation or every 32 ms during large signal changes. Also during normal operation, the power transmitter sends power packets every 5 seconds.
5. To end the power transfer, the power receiver sends an “End Power” message or sends no communications for 1.25 seconds. Either of these events places the power transmitter in a low-power state.

### TI's WPC-compliant solutions

TI is a founding member of the WPC and has taken an active role in developing a robust wireless-power specification. TI has developed reliable solutions for both a power receiver and a power transmitter in the form of three newly developed ICs. The power receiver uses the MSP430bq1010 and bq25046 devices. The power transmitter is based on the bq500110, which supports type A1 (single-coil) configurations. Both receiver and transmitter ICs are designed to be interoperable with other WPC-compliant solutions.

The MSP430bq1010 in the power receiver handles all of the logic functions and communications. The onboard analog-to-digital converters monitor the levels of voltage into and current out of the bq25046. The bq25046 provides load-current information to the MSP430bq1010, which then uses this information to control the power transmitter's operating point. The bq25046 provides a low-current, 3.3-V low-dropout regulator (LDO) to power the MSP430bq1010 and logic circuit, while a larger 5.0-V LDO is capable of providing up to 1 A of current to the main output.

The power-transmitter solution is provided with the bq500110. This device demodulates and decodes serial data from the power receiver. The control circuits first

certify that the power receiver is indeed a WPC-compliant device, then configure the power transmitter accordingly.

TI's BQTESLA100LP EVM kit combines separate transmitter and receiver designs into a single kit that includes mechanical packaging. This kit can be used for evaluation of the ICs or as a design example. The WPC has certified that both the power-transmitter and the power-receiver solutions meet the Version 1.0 specification. No software is required to operate the EVM, which needs only a 19-V input. The EVM kit's output will be 5 V at up to 1 A. The transmitter EVM includes multiple LED options for visual indication of power-transmission status. Also, two buzzer options provide audio indication of the start of power transfer.

**Conclusion**

The WPC standard is a set of guidelines that allows manufacturers to develop solutions with the confidence that their components will mesh with a variety of other WPC-certified components designed for inductive power transfer.

**References**

For more information related to this article, you can download an Acrobat® Reader® file at [www.ti.com/lit/litnumber](http://www.ti.com/lit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

<b>Document Title</b>	<b>TI Lit. #</b>
1. Wireless Power Consortium. "System Description Wireless Power Transfer, Vol. 1, Part 1," Version 1.0 [Online]. Available: <a href="http://www.wirelesspowerconsortium.com/downloads/wireless-power-specification-part-1.html">http://www.wirelesspowerconsortium.com/downloads/wireless-power-specification-part-1.html</a>	—

<b>Document Title</b>	<b>TI Lit. #</b>
2. "Wireless Power Transmitter Manager," bq500110 Data Sheet. . . . .	slusae0
3. "1.1A, Single-Input 5-V Power Supply IC for Wireless Power Applications," bq25046 Data Sheet . . . . .	slusa83
4. "Wireless Receiver-Side Communication and Power Monitoring IC for Wireless Power," MSP430bq1010 Data Sheet. . . . .	slas696
5. "bq500110EVM-688 Evaluation Module," User's Guide . . . . .	slvu429a
6. "bq25046EVM-687 Evaluation Module," User's Guide . . . . .	slvu420

**Related Web sites**

[www.ti.com/wirelesspower](http://www.ti.com/wirelesspower)  
[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)  
 Replace *partnumber* with bq25046, bq500110, or MSP430bq1010

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

**Americas** Phone +1(972) 644-5580

**Brazil** Phone 0800-891-2616

**Mexico** Phone 0800-670-7544

Fax +1(972) 927-6377  
Internet/Email [support.ti.com/sc/pic/americas.htm](http://support.ti.com/sc/pic/americas.htm)

### Europe, Middle East, and Africa

Phone

European Free Call 00800-ASK-TEXAS  
(00800 275 83927)  
International +49 (0) 8161 80 2121  
Russian Support +7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +1(49) (0) 8161 80 2045  
Internet [support.ti.com/sc/pic/euro.htm](http://support.ti.com/sc/pic/euro.htm)  
Direct Email [asktexas@ti.com](mailto:asktexas@ti.com)

### Japan

Phone Domestic 0120-92-3326  
Fax International +81-3-3344-5317  
Domestic 0120-81-0036  
Internet/Email International [support.ti.com/sc/pic/japan.htm](http://support.ti.com/sc/pic/japan.htm)  
Domestic [www.tij.co.jp/pic](http://www.tij.co.jp/pic)

## Asia

Phone

International +91-80-41381665  
Domestic [Toll-Free Number](http://support.ti.com/sc/pic/asia.htm)

**Note:** Toll-free numbers do not support mobile and IP phones.

Australia 1-800-999-084  
China 800-820-8682  
Hong Kong 800-96-5941  
India 1-800-425-7888  
Indonesia 001-803-8861-1006  
Korea 080-551-2804  
Malaysia 1-800-80-3973  
New Zealand 0800-446-934  
Philippines 1-800-765-7404  
Singapore 800-886-1028  
Taiwan 0800-006800  
Thailand 001-800-886-0010

Fax +8621-23073686  
Email [tiasia@ti.com](mailto:tiasia@ti.com) or [ti-china@ti.com](mailto:ti-china@ti.com)  
Internet [support.ti.com/sc/pic/asia.htm](http://support.ti.com/sc/pic/asia.htm)

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A122010

E2E is a trademark of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated