

Find authenticated court documents without watermarks at docketalarm.com.

### MICROELECTRONIC CIRCUIT DESIGN

Copyright © 1997 by The McGraw-Hill Companies, Inc. All rights reserved. Printed in the United States of America. Except as permitted under the United States Copyright Act of 1976, no part of this publication may be reproduced or distributed in any form or by any means, or stored in a data base or retrieval system, without the prior written permission of the Publisher.

This book is printed on acid-free paper.

1 2 3 4 5 6 7 8 9 DOW DOW 9 0 3 2 1 0 9 8 7

### ISBN 0-07-032482-4

This book was set in Times Roman by Publication Services. The editor was Lynn B. Cox; the editing supervisor was Eva Marie Strock; the interior designer was Mel Haber; the cover designer was Francis Owens; the production supervisor was Natalie Durbin. R. R. Donnelley & Sons, Wilard, was the printer and binder.

#### Library of Congress Cataloging-in-Publication Data

Jaeger, Richard C. Microelectronic circuit design / Richard C. Jaeger. p. cm. — (McGraw-Hill series in electrical and computer engineering) Includes bibliographical references and index. ISBN 0-07-032482-4 1. Integrated circuits—Design and construction. 2. Semiconductors—Design and construction. 3. Electronic circuit design. I. Title. II. Series. TK7874.J333 1996 621.3815—dc20 96-26208 CIP

INTERNATIONAL EDITION

Copyright 1997. Exclusive rights by The McGraw-Hill Companies, Inc. for manufacture and export. This book cannot be re-exported from the country to which it is consigned by McGraw-Hill. The International Edition is not available in North America.

When ordering this title, use ISBN 0-07-114386-6

### http://www.mhcollege.com

1--

RM

DOCKE.

### **12.1 THE DIFFERENTIAL AMPLIFIER**

The basic differential amplifier is shown in schematic form in Fig. 12.1. The amplifier has two inputs, to which the input signals  $v_+$  and  $v_-$  are connected, and a single output  $v_0$ , all referenced to the common (ground) terminal between the two power supplies  $V_{CC}$  and  $V_{EE}$ . In most applications,  $V_{CC} \ge 0$  and  $-V_{EE} \le 0$ , and the voltages are often symmetric—that is,  $\pm 5$  V,  $\pm 12$  V,  $\pm 15$  V,  $\pm 18$  V,  $\pm 22$  V, and so on. These power supply voltages limit the output voltage range:  $-V_{EE} \leq v_O \leq V_{CC}$ .

For simplicity, the amplifier is most often drawn without explicitly showing the power supplies, as in Fig. 12.2(a), or the ground connection, as in Fig. 12.2(b)—but we must remember that the power and ground terminals are always present in the implementation of a real circuit.

For purposes of signal analysis, the differential amplifier can be represented by its input resistance  $R_{ID}$ , output resistance  $R_O$ , and controlled voltage source  $Av_{id}$ , as in Fig. 12.3. This is the simplified g-parameter two-port representation from Chap. 11 with  $g_{12} = 0.$ 

A = voltage gain (open-circuit voltage gain)

 $v_{id} = (v_+ - v_-) =$  differential input signal voltage (12.1)

 $R_{ID}$  = amplifier input resistance

 $R_O$  = amplifier output resistance





Figure 12.2 (a) Amplifier without power supplies explicitly included. (b) Differ-

ground connection.







Find authenticated court documents without watermarks at docketalarm.com.

The signal voltage developed at the output of the amplifier is in phase with the voltage applied to the + input terminal and 180° out of phase with the signal applied to the - input terminal. The  $v_+$  and  $v_-$  terminals are therefore referred to as the **noninverting input** and **inverting input**, respectively.

In a typical application, the amplifier is driven by a signal source having a Thévenin equivalent voltage  $v_s$  and resistance  $R_s$  and is connected to a load represented by the resistor  $R_L$ , as in Fig. 12.4. For this simple circuit, the output voltage can be written in terms of the dependent source as

$$\mathbf{v_o}^* = A\mathbf{v_{id}}\frac{R_L}{R_O + R_L} \tag{12.2}$$

and the voltage vid is

$$\mathbf{v}_{id} = \mathbf{v}_s \frac{R_{ID}}{R_{ID} + R_S} \tag{12.3}$$

Combining Eqs. (12.2) and (12.3) yields an expression for the overall voltage gain of the amplifier circuit in Fig. 12.4 for arbitrary values of  $R_s$  and  $R_L$ :

$$A_V = \frac{\mathbf{v}_0}{\mathbf{v}_s} = A \frac{R_{ID}}{R_S + R_{ID}} \frac{R_L}{R_O + R_L}$$
(12.4)

Operational-amplifier circuits are most often **dc-coupled amplifiers**, and the signals  $v_o$  and  $v_s$  may in fact have a dc component that represents a dc shift of the input away from the Q-point. The op amp amplifies not only the ac components of the signal but also this dc component. We must remember that the ratio needed to find  $A_V$ , as indicated in Eq. (12.4), is determined by the amplitude and phase of the individual signal components and is not a time-varying quantity, but  $\omega = 0$  is a valid signal frequency!



EXAMPLE 12.1: Calculate the voltage gain for an amplifier with the following parameters: A = 100,  $R_{ID} = 100 \text{ k}\Omega$ , and  $R_O = 100 \Omega$ , with  $R_S = 10 \text{ k}\Omega$  and  $R_L = 1000 \Omega$ . Express the result in dB.

SOLUTION: Using Eq. (12.4)

$$A_V = 100 \left( \frac{100 \text{ k}\Omega}{10 \text{ k}\Omega + 100 \text{ k}\Omega} \right) \left( \frac{1000 \Omega}{100 \Omega + 1000 \Omega} \right) = 82.6$$
$$A_{VdB} = 20 \log |A_V| = 20 \log |82.6| = 38.3 \text{ dB}$$

\*Author's note: Recall from Chapters 1 and 11 that  $v_s$ ,  $v_o$ ,  $i_2$  and so on represent our signal voltages and currents and are generally functions of time:  $v_s(t)$ ,  $v_o(t)$ ,  $i_2(t)$ . But whenever we do algebraic calculations of voltage gain, current gain, input resistance, output resistance, and so on, we must use **phasor** representations of the individual signal components in our calculations:  $v_s$ ,  $v_o$ ,  $i_2$ . Note that the signals  $v_s(t)$ ,  $v_o(t)$ ,  $i_2(t)$  may be composed of many individual signal components, one of which may be a dc shift away from the Q-point value.

Figure 12.4 Amplifier with source and load attached.

DISCUSSION: The amplifier's internal voltage gain capability is A = 100, but an overall gain of only 82.6 is being realized because a portion of the signal source voltage ( $\approx 9$  percent) is being dropped across  $R_S$  and part of the internal amplifier voltage ( $Av_{id}$ ) (also  $\approx 9$  percent) is being lost across  $R_O$ .

### The Ideal Differential Amplifier

An ideal differential amplifier would produce an output that depends only on the voltage difference  $v_{id}$  between its two input terminals, and this voltage would be independent of source and load resistances. Referring to Eq. (12.4), we see that this behavior can be achieved if the input resistance of the amplifier is infinite and the output resistance is zero (as pointed out previously in Sec. 11.5). For this case, Eq. (12.4) reduces to

$$\mathbf{v}_{\mathbf{o}} = A\mathbf{v}_{\mathbf{id}}$$
 or  $A_V = \frac{\mathbf{v}_{\mathbf{o}}}{\mathbf{v}_{\mathbf{id}}} = A$  (12.5)

and the full amplifier gain is realized. A is referred to as either the **open-circuit voltage** gain or **open-loop gain** of the amplifier and represents the maximum voltage gain available from the device.

As also mentioned in Chapter 11, we often want to achieve the fully mismatched resistance condition in voltage amplifier applications ( $R_{ID} \gg R_S$  and  $R_O \ll R_L$ ), so that maximum voltage gain in Eq. (12.5) can be achieved. For the mismatched case, the overall amplifier gain is independent of the source and load resistances, and multiple amplifier stages can be cascaded without concern for interaction between stages.

### **12.2 THE IDEAL OPERATIONAL AMPLIFIER**

DOCKE

As noted earlier, the term "operational amplifier" grew from use of these high-performance amplifiers to perform specific electronic circuit functions or operations, such as scaling, summation, and integration, in analog computers. The operational amplifier used in these applications is an ideal differential amplifier with an additional property: infinite voltage gain. Although it is impossible to realize the **ideal operational amplifier**, its conceptual use allows us to understand the basic performance to be expected from a given analog circuit and serves as a model to help in circuit design. Once the properties of the ideal amplifier and its use in basic circuits are understood, then various ideal assumptions can be removed in order to understand their effect on circuit performance.

The ideal operational amplifier is a special case of the ideal difference amplifier in Fig. 12.3, in which  $R_{ID} = \infty$ ,  $R_O = 0$ , and, most importantly, voltage gain  $A = \infty$ . Infinite gain leads to the first of two assumptions used to analyze circuits containing ideal op amps. Solving for  $v_{id}$  in Eq. (12.5),

$$\mathbf{v_{id}} = \frac{\mathbf{v_o}}{A}$$
 and  $\lim_{A \to \infty} \mathbf{v_{id}} = 0$  (12.6)

If A is infinite, then the input voltage  $v_{id}$  will be zero for any finite output voltage. We will refer to this condition as Assumption 1 for ideal op-amp circuit analysis.

An infinite value for the input resistance  $R_{ID}$  forces the two input currents  $i_+$  and  $i_-$  to be zero, which will be Assumption 2 for analysis of ideal op-amp circuits. These two results, combined with Kirchhoff's voltage and current laws, form the basis for analysis of all ideal op-amp circuits.

# DOCKET



## Explore Litigation Insights

Docket Alarm provides insights to develop a more informed litigation strategy and the peace of mind of knowing you're on top of things.

## **Real-Time Litigation Alerts**



Keep your litigation team up-to-date with **real-time** alerts and advanced team management tools built for the enterprise, all while greatly reducing PACER spend.

Our comprehensive service means we can handle Federal, State, and Administrative courts across the country.

## **Advanced Docket Research**



With over 230 million records, Docket Alarm's cloud-native docket research platform finds what other services can't. Coverage includes Federal, State, plus PTAB, TTAB, ITC and NLRB decisions, all in one place.

Identify arguments that have been successful in the past with full text, pinpoint searching. Link to case law cited within any court document via Fastcase.

## **Analytics At Your Fingertips**



Learn what happened the last time a particular judge, opposing counsel or company faced cases similar to yours.

Advanced out-of-the-box PTAB and TTAB analytics are always at your fingertips.

### API

Docket Alarm offers a powerful API (application programming interface) to developers that want to integrate case filings into their apps.

### LAW FIRMS

Build custom dashboards for your attorneys and clients with live data direct from the court.

Automate many repetitive legal tasks like conflict checks, document management, and marketing.

### **FINANCIAL INSTITUTIONS**

Litigation and bankruptcy checks for companies and debtors.

### **E-DISCOVERY AND LEGAL VENDORS**

Sync your system to PACER to automate legal marketing.

