

*A practical
introduction to
electronic circuits*

Third edition

MARTIN HARTLEY JONES

Published by the Press Syndicate of the University of Cambridge
The Pitt Building, Trumpington Street, Cambridge CB2 1RP
40 West 20th Street, New York, NY 10011-4211, USA
10 Stamford Road, Oakleigh, Melbourne 3166, Australia

© Cambridge University Press 1977, 1985, 1995

First published 1977
Reprinted 1978, 1979, 1980, 1981 (with corrections), 1982, 1983
Second edition 1985
Reprinted 1987, 1988, 1990, 1992, 1993
Third edition 1995

Printed in Great Britain at the University Press, Cambridge

A Catalogue record for this book is available from the British Library

Library of Congress cataloguing in publication data

Jones, Martin Hartley, 1942–
A practical introduction to electronic circuits / Martin Hartley Jones. — 3rd ed.
p. cm.
Includes bibliographical references and index.
ISBN 0-521-47286-5. — ISBN 0-521-47879-0 (pbk.)
1. Electronic circuits. I. Title.
TK7867.J62 1995
621.3815—dc20 95-4035 CIP

ISBN 0 521 47286 5 hardback
ISBN 0 521 47879 0 paperback

Cover illustration from radar processing circuit.
Courtesy Kelvin Hughes Ltd.

wv

Integrated circuit analogue building bricks

11.1 Introduction

The integrated circuit (IC) is clearly the building brick of electronic circuits. We have already had a flavour of IC applications when looking at power supply regulators. Now we turn towards the full range of IC capabilities. A glance through a component distributor's catalogue reveals a seemingly limitless range of ICs for virtually every conceivable function. An IC may contain from a dozen transistors to a million depending on the application, together with all necessary resistors, diodes etc. The intimate thermal connection achieved by fabricating all the components on one chip of silicon generally leads to excellent stability and predictability in use.

The understanding of discrete components gained from earlier chapters will be found essential to the proper interfacing of ICs: in fact even today very few analogue circuit applications dispense totally with discrete semiconductors. However, the IC designer has today relieved the circuit designer of much of the 'donkey work'. In addition, the small size and low power consumption of ICs has made possible products like the Camcorder and hand-held GPS position-fixing satellite receiver.

This chapter deals with applications of linear ICs. They are designed to handle *analogue* signals, which carry their information in terms of amplitude and waveshape. Most audio and radio signals come into this category; they are distinct from the standard binary pulses of digital circuits which are discussed in chapter 13. To give an idea of the scope of this chapter, fig. 11.1 includes many of the basic building bricks which will be discussed and provides a quick reference to the outline circuits.

11.2 The operational amplifier

11.2.1 Simplifying assumptions

All the circuits of fig. 11.1 make use of an *operational amplifier* (op amp). The term 'operational' is generally used nowadays to describe a high-gain voltage amplifier, particularly one in IC form; the name is derived from the original use of such amplifiers in analogue computing *operations*. The characteristics of an op amp are such that the following simplifying assumptions can be made in most practical circuits:

infinite open-loop voltage gain, A_{VOL} (typically 2×10^5)
infinite input impedance (typically $2 \text{ M}\Omega$)
zero output impedance (typically 75Ω)

The parameter values quoted above refer to the popular 741 type IC amplifier which is used in many of the practical circuits in this book.

11.2.2 Input bias current and offset voltage

The input terminals of an op amp connect to internal transistor bases or gates which must be given some d.c. reference and be able to draw a small bias current if the amplifier is to function (there are no coupling capacitors on the chip). Input bias current in the 741 amplifier is about 100 nA. The first design consideration, therefore, is that each input of any IC amplifier must have some sort of d.c. path to earth, even if it is through a high-value resistor.

Ideally, both the inverting and non-inverting inputs should 'see' the same resistance to earth; otherwise, as fig. 11.2 shows, an effective input offset voltage will appear. We can assume that the two input bias currents are equal, i.e.

$$I_1 = I_2.$$

Hence, if $R_1 = R_2$, V_1 and V_2 will be equal and there will be zero effective differential offset voltage ($V_2 - V_1$) at the amplifier inputs. In most circuits, the inverting input will normally have a feedback resistor R_f connected through to the output as in fig. 11.3 and therefore a proportion of the bias current will be drawn from the output through R_f . Now, if our circuit is designed correctly so that the offset voltage is zero, then the output will be at 0 V level under quiescent conditions. This means that, as far as the input bias current is

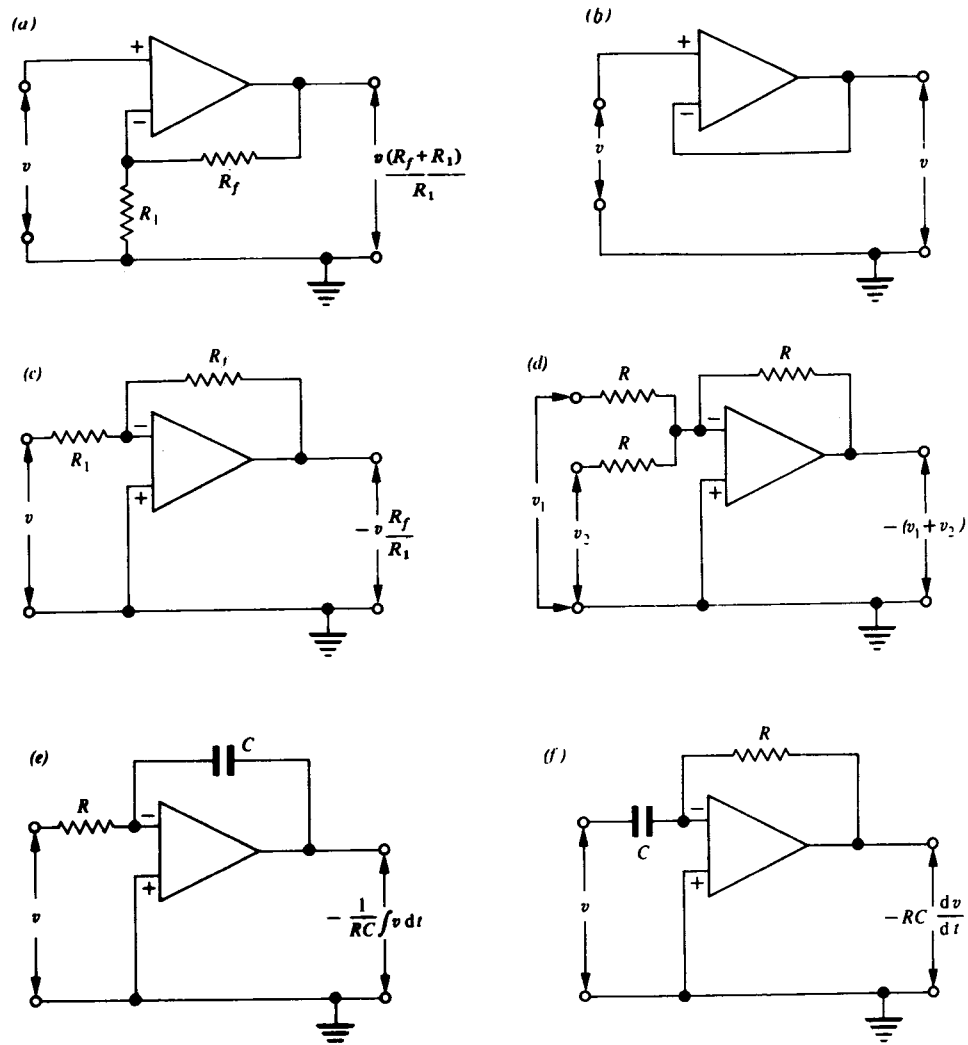


Fig. 11.1. (a) Non-inverting amplifier. (b) Voltage follower. (c) Inverting amplifier. (d) Adder. (e) Integrator. (f) Differentiator.

Explore Litigation Insights

Docket Alarm provides insights to develop a more informed litigation strategy and the peace of mind of knowing you're on top of things.

Real-Time Litigation Alerts



Keep your litigation team up-to-date with **real-time alerts** and advanced team management tools built for the enterprise, all while greatly reducing PACER spend.

Our comprehensive service means we can handle Federal, State, and Administrative courts across the country.

Advanced Docket Research



With over 230 million records, Docket Alarm's cloud-native docket research platform finds what other services can't. Coverage includes Federal, State, plus PTAB, TTAB, ITC and NLRB decisions, all in one place.

Identify arguments that have been successful in the past with full text, pinpoint searching. Link to case law cited within any court document via Fastcase.

Analytics At Your Fingertips



Learn what happened the last time a particular judge, opposing counsel or company faced cases similar to yours.

Advanced out-of-the-box PTAB and TTAB analytics are always at your fingertips.

API

Docket Alarm offers a powerful API (application programming interface) to developers that want to integrate case filings into their apps.

LAW FIRMS

Build custom dashboards for your attorneys and clients with live data direct from the court.

Automate many repetitive legal tasks like conflict checks, document management, and marketing.

FINANCIAL INSTITUTIONS

Litigation and bankruptcy checks for companies and debtors.

E-DISCOVERY AND LEGAL VENDORS

Sync your system to PACER to automate legal marketing.