 


THE
ART
OF
ELECTRONICS


PAUL HOROWITZ
WINFIELD HILL

SECOND EDITION



Paul Horowitz HARVARD UNIVERSITY

 Winfield Hill ROWLAND INSTITUTE FOR SCIENCE, CAMBRIDGE, MASSACHUSETTS



CAMBRIDGE UNIVERSITY PRESS
Cambridge, New York, Melbourne, Madrid, Cape Town, Singapore, São Paulo

Cambridge University Press
40 West 20th Street, New York, NY 10011-4211, USA
www.cambridge.org
Information on this title: www.cambridge.org/9780521370990

© Cambridge University Press 1980, 1989

This publication is in copyright. Subject to statutory exception
and to the provisions of relevant collective licensing agreements,
no reproduction of any part may take place without
the written permission of Cambridge University Press.

First edition published 1980
Second edition published 1989
20th printing 2006

Printed in the United States of America

A catalogue record for this book is available from the British Library.

ISBN-13 978-0-521-37095-0 hardback
ISBN-10 0-521-37095-7 hardback

ISBN-13 978-0-521-42228-4 paperback
ISBN-10 0-521-42228-0 paperback

Cambridge University Press has no responsibility for
the persistence or accuracy of URLs for external or
third-party Internet Web sites referred to in this publication
and does not guarantee that any content on such
Web sites is, or will remain, accurate or appropriate.

 


Figure 3.58. CMOS logic inverter.

impedance in both states, and no quiescent current whatsoever. It's called a CMOS (complementary MOS) inverter, and it is the basic structure of all digital CMOS logic, the logic family that has become dominant in large-scale integrated circuits (LSI), and seems destined to replace earlier logic families (with names like "TTL") based on bipolar transistors. Note that the CMOS inverter is two complementary MOSFET switches in *series*, alternately enabled, while the CMOS analog switch (treated earlier in the chapter) is two complementary MOSFET switches in *parallel*, enabled simultaneously.

QUIPOTE 3.14

The complementary MOS transistors in the CMOS inverter are both operating as common-

source inverters, whereas the complementary bipolar transistors in the push-pull circuits of Section 2.15 are (non-inverting) emitter followers. Try drawing a "complementary BJT inverter," analogous to the CMOS inverter. Why won't it work?

We'll be saying much more of digital CMOS in the chapters on digital logic and microprocessors (Chapters 8-11). For now, it should be evident that CMOS is a low-power logic family (with zero quiescent power) with high-impedance inputs, and with stiff outputs that swing the full supply range. Before leaving the subject, however, we can't resist the temptation to show you one additional CMOS circuit (Fig. 3.59). This is a logic *NAND* gate, whose output goes LOW only if input A AND input B are both HIGH. The operation is surprisingly easy to understand: If A and B are both HIGH, series NMOS switches Q_1 and Q_2 are both ON, pulling the output stiffly to ground; PMOS switches Q_3 and Q_4 cooperate by being OFF; thus, no current flows. However, if either A or B (or both) is LOW, the corresponding PMOS transistor is ON, pulling the output HIGH; since one (or both) of the series chain Q_1, Q_2 is OFF, no current flows.

This is called a "NAND" gate because it performs the logical AND function, but

 


Figure 3.59. CMOS NAND gate, AND gate.