 


Second Edition

# POWER ELECTRONICS

Converters,  
Applications,  
and Design



MOHAN / UNDELAND / ROBBINS

Petitioners  
Ex. 1032, p. Cover

---

---

## ABOUT THE AUTHORS

---

---

**Ned Mohan** is a professor in the Department of Electrical Engineering at the University of Minnesota, where he holds the Oscar A. Schott Chair in Power Electronics. He has worked on several power electronics projects sponsored by the industry and the electric power utilities, including the Electric Power Research Institute. He has numerous publications and patents in this field.

**Tore M. Undeland** is a Professor in Power Electronics in the Faculty of Electrical Engineering and Computer Science at the Norwegian Institute of Technology. He is also Scientific Advisor to the Norwegian Electric Power Research Institute of Electricity Supply. He has been a visiting scientific worker in the Power Electronics Converter Department of ASEA in Vaasteras, Sweden, and at Siemens in Trondheim, Norway, and a visiting professor in the Department of Electrical Engineering at the University of Minnesota. He has worked on many industrial research and development projects in the power electronics field and has numerous publications.

**William P. Robbins** is a professor in the Department of Electrical Engineering at the University of Minnesota. Prior to joining the University of Minnesota, he was a research engineer at the Boeing Company. He has taught numerous courses in electronics and semiconductor device fabrication. His research interests are in ultrasonics, pest insect detection via ultrasonics, and micromechanical devices, and he has numerous publications in this field.

---

---

# POWER ELECTRONICS

---

---

Converters, Applications,  
and Design

SECOND EDITION

**NED MOHAN**

*Department of Electrical Engineering  
University of Minnesota  
Minneapolis, Minnesota*

**TORE M. UNDELAND**

*Faculty of Electrical Engineering and Computer Science  
Norwegian Institute of Technology  
Trondheim, Norway*

**WILLIAM P. ROBBINS**

*Department of Electrical Engineering  
University of Minnesota  
Minneapolis, Minnesota*



**JOHN WILEY & SONS, INC.**  
New York Chichester Brisbane Toronto Singapore

Petitioners  
Ex. 1032, p. v

Acquisitions Editor	Steven M. Elliot
Developmental Editor	Sean M. Culhane
Marketing Manager	Susan Elbe
Senior Production Editor	Savoula Amanatidis
Text Designer	Lynn Rogan
Cover Designer	David Levy
Manufacturing Manager	Lori Bulwin
Illustration Coordinator	Jaime Perea

This book was typeset in Times Roman by The Clarinda Company, and printed and bound by Hamilton Printing Company. The cover was printed by NEBC.

Recognizing the importance of preserving what has been written, it is a policy of John Wiley & Sons, Inc. to have books of enduring value published in the United States printed on acid-free paper, and we exert our best efforts to that end.

PSpice is a registered trademark of MicroSim Corporation.  
MATLAB is a registered trademark of The MathWorks, Inc.

Copyright © 1989, 1995 by John Wiley & Sons, Inc.

All rights reserved. Published simultaneously in Canada.

Reproduction or translation of any part of this work beyond that permitted by Sections 107 and 108 of the 1976 United States Copyright Act without the permission of the copyright owner is unlawful. Requests for permission or further information should be addressed to the Permissions Department, John Wiley & Sons, Inc.

*Library of Congress Cataloging in Publication Data:*

Mohan, Ned.

Power electronics : converters, applications, and design / Ned

Mohan, Tore M. Undeland, William P. Robbins.—2nd ed.

p. cm.

Includes bibliographical references and indexes.

ISBN 0-471-58408-8 (cloth)

1. Power electronics. 2. Electric current converters. 3. Power semiconductors. I. Undeland, Tore M. II. Robbins, William P. III. Title.

TK7881.15.M64 1995

621.317—dc20

94-21158

CIP

Printed in the United States of America.

10 9 8 7 6 5 4 3 2

Petitioners  
Ex. 1032, p. vi

---

---

# PREFACE

---

---

## SECOND EDITION

The first edition of this book was published in 1989. The basic intent of this edition remains the same; that is, as a cohesive presentation of power electronics fundamentals for applications and design in the power range of 500 kW or less, where a huge market exists and where the demand for power electronics engineers is likely to be. Based on the comments collected over a five-year period, we have made a number of substantial changes to the text. The key features are as follows:

- An introductory chapter has been added to provide a review of basic electrical and magnetic circuit concepts, making it easier to use this book in introductory power electronics courses.
- A chapter on computer simulation has been added that describes the role of computer simulations in power electronics. Examples and problems based on PSpice® and MATLAB® are included. However, we have organized the material in such a way that any other simulation package can be used instead or the simulations can be skipped altogether.
- Unlike the first edition, the diode rectifiers and the phase-controlled thyristor converters are covered in a complete and easy-to-follow manner. These two chapters now contain 56 problems.
- A new chapter on the design of inductors and transformers has been added that describes easy-to-understand concepts for step-by-step design procedures. This material will be extremely useful in introducing the design of magnetics into the curriculum.
- A new chapter on heat sinks has been added.

## ORGANIZATION OF THE BOOK

This book is divided into seven parts. Part 1 presents an introduction to the field of power electronics, an overview of power semiconductor switches, a review of pertinent electric and magnetic circuit concepts, and a generic discussion of the role of computer simulations in power electronics.

Part 2 discusses the generic converter topologies that are used in most applications. The actual semiconductor devices (transistors, diodes, and so on) are assumed to be ideal, thus allowing us to focus on the converter topologies and their applications.

Part 3 discusses switch-mode dc and uninterruptible power supplies. Power supplies represent one of the major applications of power electronics.

Petitioners

Ex. 1032, p. vii

vii

Part 4 considers motor drives, which constitute another major applications area.

Part 5 includes several industrial and commercial applications in one chapter. Another chapter describes various high-power electric utility applications. The last chapter in this part of the book examines the harmonics and electromagnetic interference concerns and remedies for interfacing power electronic systems with the electric utilities.

Part 6 discusses the power semiconductor devices used in power electronic converters including diodes, bipolar junction thyristors, metal-oxide-semiconductor (MOS) field effect transistors, thyristors, gate turn-off thyristors, insulated gate bipolar transistors, and MOS-controlled thyristors.

Part 7 discusses the practical aspects of power electronic converter design including snubber circuits, drive circuits, circuit layout, and heat sinks. An extensive new chapter on the design of high-frequency inductors and transformers has been added.

## PSPICE SIMULATIONS FOR TEACHING AND DESIGN

As a companion to this book, a large number of computer simulations are available directly from Minnesota Power Electronics Research and Education, P.O. Box 14503, Minneapolis, MN 55414 (Phone/Fax: 612-646-1447) to aid in teaching and in the design of power electronic systems. The simulation package comes complete with a diskette with 76 simulations of power electronic converters and systems using the classroom (evaluation) version of PSpice for IBM-PC-compatible computers, a 261-page detailed manual that describes each simulation and a number of associated exercises for home assignments and self-learning, a 5-page instruction set to illustrate PSpice usage using these simulations as examples, and two high-density diskettes containing a copy of the classroom (evaluation) version of PSpice. This package (for a cost of \$395 plus a postage of \$4 within North America and \$25 outside) comes with a site license, which allows it to be copied for use at a single site within a company or at an educational institution in regular courses given to students for academic credits.

## SOLUTIONS MANUAL

As with the first edition of this book, a solutions manual with completely worked-out solutions to all the problems is available from the publisher.

## ACKNOWLEDGMENTS

We wish to thank all the instructors who have allowed us this opportunity to write the second edition of our book by adopting its first edition. Their comments have been most useful. We are grateful to Professors Peter Lauritzen of the University of Washington, Thomas Habetler of the Georgia Institute of Technology, Daniel Chen of the Virginia Institute of Technology, Alexander Emanuel of the Worcester Polytechnic Institute, F. P. Dawson of the University of Toronto, and Marian Kazimierzczuk of the Wright State University for their helpful suggestions in the second edition manuscript. We express our sincere appreciation to the Wiley editorial staff, including Steven Elliot, Sean Culhane, Lucille Buonocore, and Savoula Amanatidis, for keeping us on schedule and for many spirited discussions.

Ned Mohan  
Tore M. Undeland  
William P. Robbins

Petitioners

Ex. 1032, p. viii

---

---

# CONTENTS

---

---

<b>PART 1 INTRODUCTION</b>	<b>1</b>
<b>Chapter 1 Power Electronic Systems</b>	<b>3</b>
1-1 Introduction	3
1-2 Power Electronics versus Linear Electronics	4
1-3 Scope and Applications	7
1-4 Classification of Power Processors and Converters	9
1-5 About the Text	12
1-6 Interdisciplinary Nature of Power Electronics	13
1-7 Convention of Symbols Used	14
<i>Problems</i>	14
<i>References</i>	15
<b>Chapter 2 Overview of Power Semiconductor Switches</b>	<b>16</b>
2-1 Introduction	16
2-2 Diodes	16
2-3 Thyristors	18
2-4 Desired Characteristics in Controllable Switches	20
2-5 Bipolar Junction Transistors and Monolithic Darlingtons	24
2-6 Metal-Oxide-Semiconductor Field Effect Transistors	25
2-7 Gate-Turn-Off Thyristors	26
2-8 Insulated Gate Bipolar Transistors	27
2-9 MOS-Controlled Thyristors	29
2-10 Comparison of Controllable Switches	29
2-11 Drive and Snubber Circuits	30
2-12 Justification for Using Idealized Device Characteristics	31
<i>Summary</i>	32
<i>Problems</i>	32
<i>References</i>	32
<b>Chapter 3 Review of Basic Electrical and Magnetic Circuit Concepts</b>	<b>33</b>
3-1 Introduction	33
3-2 Electric Circuits	33
3-3 Magnetic Circuits	46
<i>Summary</i>	57
<i>Problems</i>	58
<i>References</i>	60

<b>Chapter 4 Computer Simulation of Power Electronic Converters and Systems</b>	<b>61</b>
4-1 Introduction	61
4-2 Challenges in Computer Simulation	62
4-3 Simulation Process	62
4-4 Mechanics of Simulation	64
4-5 Solution Techniques for Time-Domain Analysis	65
4-6 Widely Used, Circuit-Oriented Simulators	69
4-7 Equation Solvers	72
<i>Summary</i>	74
<i>Problems</i>	74
<i>References</i>	75
<b>PART 2 GENERIC POWER ELECTRONIC CIRCUITS</b>	<b>77</b>
<b>Chapter 5 Line-Frequency Diode Rectifiers: Line-Frequency ac → Uncontrolled dc</b>	<b>79</b>
5-1 Introduction	79
5-2 Basic Rectifier Concepts	80
5-3 Single-Phase Diode Bridge Rectifiers	82
5-4 Voltage-Doubler (Single-Phase) Rectifiers	100
5-5 Effect of Single-Phase Rectifiers on Neutral Currents in Three-Phase, Four-Wire Systems	101
5-6 Three-Phase, Full-Bridge Rectifiers	103
5-7 Comparison of Single-Phase and Three-Phase Rectifiers	112
5-8 Inrush Current and Overvoltages at Turn-On	112
5-9 Concerns and Remedies for Line-Current Harmonics and Low Power Factor	113
<i>Summary</i>	113
<i>Problems</i>	114
<i>References</i>	116
<i>Appendix</i>	117
<b>Chapter 6 Line-Frequency Phase-Controlled Rectifiers and Inverters: Line-Frequency ac ↔ Controlled dc</b>	<b>121</b>
6-1 Introduction	121
6-2 Thyristor Circuits and Their Control	122
6-3 Single-Phase Converters	126
6-4 Three-Phase Converters	138
6-5 Other Three-Phase Converters	153
<i>Summary</i>	153
<i>Problems</i>	154
<i>References</i>	157
<i>Appendix</i>	158
<b>Chapter 7 dc–dc Switch-Mode Converters</b>	<b>161</b>
7-1 Introduction	161
7-2 Control of dc–dc Converters	162



7-3 Step-Down (Buck) Converter	164	
7-4 Step-Up (Boost) Converter	172	
7-5 Buck-Boost Converter	178	
7-6 Cúk dc-dc Converter	184	
7-7 Full Bridge dc-dc Converter	188	
7-8 dc-dc Converter Comparison	195	
<i>Summary</i>	196	
<i>Problems</i>	197	
<i>References</i>	199	
<b>Chapter 8 Switch-Mode dc-ac Inverters: dc ↔ Sinusoidal ac</b>		<b>200</b>
8-1 Introduction	200	
8-2 Basic Concepts of Switch-Mode Inverters	202	
8-3 Single-Phase Inverters	211	
8-4 Three-Phase Inverters	225	
8-5 Effect of Blanking Time on Output Voltage in PWM Inverters	236	
8-6 Other Inverter Switching Schemes	239	
8-7 Rectifier Mode of Operation	243	
<i>Summary</i>	244	
<i>Problems</i>	246	
<i>References</i>	248	
<b>Chapter 9 Resonant Converters: Zero-Voltage and/or Zero-Current Switchings</b>		<b>249</b>
9-1 Introduction	249	
9-2 Classification of Resonant Converters	252	
9-3 Basic Resonant Circuit Concepts	253	
9-4 Load-Resonant Converters	258	
9-5 Resonant-Switch Converters	273	
9-6 Zero-Voltage-Switching, Clamped-Voltage Topologies	280	
9-7 Resonant-dc-Link Inverters with Zero-Voltage Switchings	287	
9-8 High-Frequency-Link Integral-Half-Cycle Converters	289	
<i>Summary</i>	291	
<i>Problems</i>	291	
<i>References</i>	295	
<b>PART 3 POWER SUPPLY APPLICATIONS</b>		<b>299</b>
<b>Chapter 10 Switching dc Power Supplies</b>		<b>301</b>
10-1 Introduction	301	
10-2 Linear Power Supplies	301	
10-3 Overview of Switching Power Supplies	302	
10-4 dc-dc Converters with Electrical Isolation	304	
10-5 Control of Switch-Mode dc Power Supplies	322	
10-6 Power Supply Protection	341	
10-7 Electrical Isolation in the Feedback Loop	344	
10-8 Designing to Meet the Power Supply Specifications	346	
<i>Summary</i>	349	

*Problems* 349  
*References* 351

**Chapter 11 Power Conditioners and Uninterruptible Power Supplies 354**

11-1 Introduction 354  
 11-2 Power Line Disturbances 354  
 11-3 Power Conditioners 357  
 11-4 Uninterruptible Power Supplies (UPSs) 358  
     *Summary* 363  
     *Problems* 363  
     *References* 364

**PART 4 MOTOR DRIVE APPLICATIONS 365**

**Chapter 12 Introduction to Motor Drives 367**

12-1 Introduction 367  
 12-2 Criteria for Selecting Drive Components 368  
     *Summary* 375  
     *Problems* 376  
     *References* 376

**Chapter 13 dc Motor Drives 377**

13-1 Introduction 377  
 13-2 Equivalent Circuit of dc Motors 377  
 13-3 Permanent-Magnet dc Motors 380  
 13-4 dc Motors with a Separately Excited Field Winding 381  
 13-5 Effect of Armature Current Waveform 382  
 13-6 dc Servo Drives 383  
 13-7 Adjustable-Speed dc Drives 391  
     *Summary* 396  
     *Problems* 396  
     *References* 398

**Chapter 14 Induction Motor Drives 399**

14-1 Introduction 399  
 14-2 Basic Principles of Induction Motor Operation 400  
 14-3 Induction Motor Characteristics at Rated (Line) Frequency and Rated Voltage 405  
 14-4 Speed Control by Varying Stator Frequency and Voltage 406  
 14-5 Impact of Nonsinusoidal Excitation on Induction Motors 415  
 14-6 Variable-Frequency Converter Classifications 418  
 14-7 Variable-Frequency PWM-VSI Drives 419  
 14-8 Variable-Frequency Square-Wave VSI Drives 425  
 14-9 Variable-Frequency CSI Drives 426  
 14-10 Comparison of Variable-Frequency Drives 427

14-11 Line-Frequency Variable-Voltage Drives	428	
14-12 Reduced Voltage Starting ("Soft Start") of Induction Motors		430
14-13 Speed Control by Static Slip Power Recovery	431	
<i>Summary</i>	432	
<i>Problems</i>	433	
<i>References</i>	434	
<b>Chapter 15 Synchronous Motor Drives</b>		<b>435</b>
15-1 Introduction	435	
15-2 Basic Principles of Synchronous Motor Operation	435	
15-3 Synchronous Servomotor Drives with Sinusoidal Waveforms		439
15-4 Synchronous Servomotor Drives with Trapezoidal Waveforms		440
15-5 Load-Commutated Inverter Drives	442	
15-6 Cycloconverters	445	
<i>Summary</i>	445	
<i>Problems</i>	446	
<i>References</i>	447	
<b>PART 5 OTHER APPLICATIONS</b>		<b>449</b>
<b>Chapter 16 Residential and Industrial Applications</b>		<b>451</b>
16-1 Introduction	451	
16-2 Residential Applications	451	
16-3 Industrial Applications	455	
<i>Summary</i>	459	
<i>Problems</i>	459	
<i>References</i>	459	
<b>Chapter 17 Electric Utility Applications</b>		<b>460</b>
17-1 Introduction	460	
17-2 High-voltage dc Transmission	460	
17-3 Static var Compensators	471	
17-4 Interconnection of Renewable Energy Sources and Energy Storage Systems to the Utility Grid	475	
17-5 Active Filters	480	
<i>Summary</i>	480	
<i>Problems</i>	481	
<i>References</i>	482	
<b>Chapter 18 Optimizing the Utility Interface with Power     Electronic Systems</b>		<b>483</b>
18-1 Introduction	483	
18-2 Generation of Current Harmonics	484	
18-3 Current Harmonics and Power Factor	485	
18-4 Harmonic Standards and Recommended Practices		485
18-5 Need for Improved Utility Interface	487	

18-6 Improved Single-Phase Utility Interface	488
18-7 Improved Three-Phase Utility Interface	498
18-8 Electromagnetic Interference	500
<i>Summary</i>	502
<i>Problems</i>	503
<i>References</i>	503

**PART 6 SEMICONDUCTOR DEVICES** **505**

**Chapter 19 Basic Semiconductor Physics** **507**

19-1 Introduction	507
19-2 Conduction Processes in Semiconductors	507
19-3 <i>pn</i> Junctions	513
19-4 Charge Control Description of <i>pn</i> -Junction Operation	518
19-5 Avalanche Breakdown	520
<i>Summary</i>	522
<i>Problems</i>	522
<i>References</i>	523

**Chapter 20 Power Diodes** **524**

20-1 Introduction	524
20-2 Basic Structure and <i>I-V</i> Characteristics	524
20-3 Breakdown Voltage Considerations	526
20-4 On-State Losses	531
20-5 Switching Characteristics	535
20-6 Schottky Diodes	539
<i>Summary</i>	543
<i>Problems</i>	543
<i>References</i>	545

**Chapter 21 Bipolar Junction Transistors** **546**

21-1 Introduction	546
21-2 Vertical Power Transistor Structures	546
21-3 <i>I-V</i> Characteristics	548
21-4 Physics of BJT Operation	550
21-5 Switching Characteristics	556
21-6 Breakdown Voltages	562
21-7 Second Breakdown	563
21-8 On-State Losses	565
21-9 Safe Operating Areas	567
<i>Summary</i>	568
<i>Problems</i>	569
<i>References</i>	570

**Chapter 22 Power MOSFETs** **571**

22-1 Introduction	571
22-2 Basic Structure	571

22-3 <i>I</i> - <i>V</i> Characteristics	574	
22-4 Physics of Device Operation	576	
22-5 Switching Characteristics	581	
22-6 Operating Limitations and Safe Operating Areas	587	
<i>Summary</i>	593	
<i>Problems</i>	594	
<i>References</i>	595	
<b>Chapter 23 Thyristors</b>		<b>596</b>
23-1 Introduction	596	
23-2 Basic Structure	596	
23-3 <i>I</i> - <i>V</i> Characteristics	597	
23-4 Physics of Device Operation	599	
23-5 Switching Characteristics	603	
23-6 Methods of Improving <i>di/dt</i> and <i>dv/dt</i> Ratings	608	
<i>Summary</i>	610	
<i>Problems</i>	611	
<i>References</i>	612	
<b>Chapter 24 Gate Turn-Off Thyristors</b>		<b>613</b>
24-1 Introduction	613	
24-2 Basic Structure and <i>I</i> - <i>V</i> Characteristics	613	
24-3 Physics of Turn-Off Operation	614	
24-4 GTO Switching Characteristics	616	
24-5 Overcurrent Protection of GTOs	623	
<i>Summary</i>	624	
<i>Problems</i>	624	
<i>References</i>	625	
<b>Chapter 25 Insulated Gate Bipolar Transistors</b>		<b>626</b>
25-1 Introduction	626	
25-2 Basic Structure	626	
25-3 <i>I</i> - <i>V</i> Characteristics	628	
25-4 Physics of Device Operation	629	
25-5 Latchup in IGBTs	631	
25-6 Switching Characteristics	634	
25-7 Device Limits and SOAs	637	
<i>Summary</i>	639	
<i>Problems</i>	639	
<i>References</i>	640	
<b>Chapter 26 Emerging Devices and Circuits</b>		<b>641</b>
26-1 Introduction	641	
26-2 Power Junction Field Effect Transistors	641	
26-3 Field-Controlled Thyristor	646	
26-4 JFET-Based Devices versus Other Power Devices	648	
26-5 MOS-Controlled Thyristors	649	

26-6 Power Integrated Circuits	656
26-7 New Semiconductor Materials for Power Devices	661
<i>Summary</i>	664
<i>Problems</i>	665
<i>References</i>	666

**PART 7 PRACTICAL CONVERTER DESIGN CONSIDERATIONS** **667**

**Chapter 27 Snubber Circuits** **669**

27-1 Function and Types of Snubber Circuits	669
27-2 Diode Snubbers	670
27-3 Snubber Circuits for Thyristors	678
27-4 Need for Snubbers with Transistors	680
27-5 Turn-Off Snubber	682
27-6 Overvoltage Snubber	686
27-7 Turn-On Snubber	688
27-8 Snubbers for Bridge Circuit Configurations	691
27-9 GTO Snubber Considerations	692
<i>Summary</i>	693
<i>Problems</i>	694
<i>References</i>	695

**Chapter 28 Gate and Base Drive Circuits** **696**

28-1 Preliminary Design Considerations	696
28-2 dc-Coupled Drive Circuits	697
28-3 Electrically Isolated Drive Circuits	703
28-4 Cascode-Connected Drive Circuits	710
28-5 Thyristor Drive Circuits	712
28-6 Power Device Protection in Drive Circuits	717
28-7 Circuit Layout Considerations	722
<i>Summary</i>	728
<i>Problems</i>	729
<i>References</i>	729

**Chapter 29 Component Temperature Control and Heat Sinks** **730**

29-1 Control of Semiconductor Device Temperatures	730
29-2 Heat Transfer by Conduction	731
29-3 Heat Sinks	737
29-4 Heat Transfer by Radiation and Convection	739
<i>Summary</i>	742
<i>Problems</i>	743
<i>References</i>	743

**Chapter 30 Design of Magnetic Components** **744**

30-1 Magnetic Materials and Cores	744
30-2 Copper Windings	752

30-3 Thermal Considerations 754  
30-4 Analysis of a Specific Inductor Design 756  
30-5 Inductor Design Procedures 760  
30-6 Analysis of a Specific Transformer Design 767  
30-7 Eddy Currents 771  
30-8 Transformer Leakage Inductance 779  
30-9 Transformer Design Procedure 780  
30-10 Comparison of Transformer and Inductor Sizes 789  
    *Summary* 789  
    *Problems* 790  
    *References* 792

**Index**

**793**

---

---

## CHAPTER 7

---

---

# dc-dc SWITCH-MODE CONVERTERS

---

### 7-1 INTRODUCTION

The dc-dc converters are widely used in regulated switch-mode dc power supplies and in dc motor drive applications. As shown in Fig. 7-1, often the input to these converters is an unregulated dc voltage, which is obtained by rectifying the line voltage, and therefore it will fluctuate due to changes in the line-voltage magnitude. Switch-mode dc-to-dc converters are used to convert the unregulated dc input into a controlled dc output at a desired voltage level.

Looking ahead to the application of these converters, we find that these converters are very often used with an electrical isolation transformer in the switch-mode dc power supplies and almost always without an isolation transformer in case of dc motor drives. Therefore, to discuss these circuits in a generic manner, only the nonisolated converters are considered in this chapter, since the electrical isolation is an added modification.

The following dc-dc converters are discussed in this chapter:

1. Step-down (buck) converter
2. Step-up (boost) converter
3. Step-down/step-up (buck-boost) converter
4. Cúk converter
5. Full-bridge converter

Of these five converters, only the step-down and the step-up are the basic converter topologies. Both the buck-boost and the Cúk converters are combinations of the two basic topologies. The full-bridge converter is derived from the step-down converter.

 


Figure 7-1 A dc-dc converter system.



The converters listed are discussed in detail in this chapter. Their variations, as they apply to specific applications, are described in the chapters dealing with switch-mode dc power supplies and dc motor drives.

In this chapter, the converters are analyzed in steady state. The switches are treated as being ideal, and the losses in the inductive and the capacitive elements are neglected. Such losses can limit the operational capacity of some of these converters and are discussed separately.

The dc input voltage to the converters is assumed to have zero internal impedance. It could be a battery source; however, in most cases, the input is a diode rectified ac line voltage (as is discussed in Chapter 5) with a large filter capacitance, as shown in Fig. 7-1 to provide a low internal impedance and a low-ripple dc voltage source.

In the output stage of the converter, a small filter is treated as an integral part of the dc-to-dc converter. The output is assumed to supply a load that can be represented by an equivalent resistance, as is usually the case in switch-mode dc power supplies. A dc motor load (the other application of these converters) can be represented by a dc voltage in series with the motor winding resistance and inductance.

## 7-2 CONTROL OF dc-dc CONVERTERS

In dc-dc converters, the average dc output voltage must be controlled to equal a desired level, though the input voltage and the output load may fluctuate. Switch-mode dc-dc converters utilize one or more switches to transform dc from one level to another. In a dc-dc converter with a given input voltage, the average output voltage is controlled by controlling the switch on and off durations ( $t_{on}$  and  $t_{off}$ ). To illustrate the switch-mode conversion concept, consider a basic dc-dc converter shown in Fig. 7-2a. The average value  $V_o$  of the output voltage  $v_o$  in Fig. 7-2b depends on  $t_{on}$  and  $t_{off}$ . One of the methods for controlling the output voltage employs switching at a constant frequency (hence, a constant switching time period  $T_s = t_{on} + t_{off}$ ) and adjusting the on duration of the switch to control the average output voltage. In this method, called *pulse-width modulation* (PWM) switching, the switch duty ratio  $D$ , which is defined as the ratio of the on duration to the switching time period, is varied.

The other control method is more general, where both the switching frequency (and hence the time period) and the on duration of the switch are varied. This method is used only in dc-dc converters utilizing force-commutated thyristors and therefore will not be discussed in this book. Variation in the switching frequency makes it difficult to filter the ripple components in the input and the output waveforms of the converter.

 


Figure 7-2 Switch-mode dc-dc conversion.

Petitioners

Ex. 1032, p. 162

 


Figure 7-3 Pulse-width modulator: (a) block diagram; (b) comparator signals.

In the PWM switching at a constant switching frequency, the switch control signal, which controls the state (on or off) of the switch, is generated by comparing a signal-level control voltage  $v_{\text{control}}$  with a repetitive waveform as shown in Figs. 7-3a and 7-3b. The control voltage signal generally is obtained by amplifying the error, or the difference between the actual output voltage and its desired value. The frequency of the repetitive waveform with a constant peak, which is shown to be a sawtooth, establishes the switching frequency. This frequency is kept constant in a PWM control and is chosen to be in a few kilohertz to a few hundred kilohertz range. When the amplified error signal, which varies very slowly with time relative to the switching frequency, is greater than the sawtooth waveform, the switch control signal becomes high, causing the switch to turn on. Otherwise, the switch is off. In terms of  $v_{\text{control}}$  and the peak of the sawtooth waveform  $\hat{V}_{\text{st}}$  in Fig. 7-3, the switch duty ratio can be expressed as

$$D = \frac{t_{\text{on}}}{T_s} = \frac{v_{\text{control}}}{\hat{V}_{\text{st}}} \tag{7-1}$$

The dc-dc converters can have two distinct modes of operation: (1) continuous current conduction and (2) discontinuous current conduction. In practice, a converter may operate in both modes, which have significantly different characteristics. Therefore, a converter and its control should be designed based on both modes of operation.

Petitioners

Ex. 1032, p. 163

## 7-3 STEP-DOWN (BUCK) CONVERTER

As the name implies, a step-down converter produces a lower average output voltage than the dc input voltage  $V_d$ . Its main application is in regulated dc power supplies and dc motor speed control.

Conceptually, the basic circuit of Fig. 7-2a constitutes a step-down converter for a purely resistive load. Assuming an ideal switch, a constant instantaneous input voltage  $V_d$ , and a purely resistive load, the instantaneous output voltage waveform is shown in Fig. 7-2b as a function of the switch position. The average output voltage can be calculated in terms of the switch duty ratio:

$$V_o = \frac{1}{T_s} \int_0^{T_s} v_o(t) dt = \frac{1}{T_s} \left( \int_0^{t_{on}} V_d dt + \int_{t_{on}}^{T_s} 0 dt \right) = \frac{t_{on}}{T_s} V_d = DV_d \quad (7-2)$$

Substituting for  $D$  in Eq. 7-2 from Eq. 7-1 yields

$$V_o = \frac{V_d}{\hat{V}_{st}} v_{\text{control}} = k v_{\text{control}}$$

where

$$k = \frac{V_d}{\hat{V}_{st}} = \text{constant}$$

By varying the duty ratio  $t_{on}/T_s$  of the switch,  $V_o$  can be controlled. Another important observation is that the average output voltage  $V_o$  varies linearly with the control voltage, as is the case in linear amplifiers. In actual applications, the foregoing circuit has two drawbacks: (1) In practice the load would be inductive. Even with a resistive load, there would always be certain associated stray inductance. This means that the switch would have to absorb (or dissipate) the inductive energy and therefore it may be destroyed. (2) The output voltage fluctuates between zero and  $V_d$ , which is not acceptable in most applications. The problem of stored inductive energy is overcome by using a diode as shown in Fig. 7-4a. The output voltage fluctuations are very much diminished by using a low-pass filter, consisting of an inductor and a capacitor. Figure 7-4b shows the waveform of the input  $v_o$ , to the low-pass filter (same as the output voltage in Fig. 7-2b without a low-pass filter), which consists of a dc component  $V_o$ , and the harmonics at the switching frequency  $f_s$  and its multiples, as shown in Fig. 7-4b. The low-pass filter characteristic with the damping provided by the load resistor  $R$  is shown in Fig. 7-4c. The corner frequency  $f_c$  of this low-pass filter is selected to be much lower than the switching frequency, thus essentially eliminating the switching frequency ripple in the output voltage.

During the interval when the switch is on, the diode in Fig. 7-4a becomes reverse biased and the input provides energy to the load as well as to the inductor. During the interval when the switch is off, the inductor current flows through the diode, transferring some of its stored energy to the load.

In the steady-state analysis presented here, the filter capacitor at the output is assumed to be very large, as is normally the case in applications requiring a nearly constant instantaneous output voltage  $v_o(t) \approx V_o$ . The ripple in the capacitor voltage (output voltage) is calculated later.

From Fig. 7-4a we observe that in a step-down converter, the average inductor current is equal to the average output current  $I_o$ , since the average capacitor current in steady state is zero (as discussed in Chapter 3, Section 3-2-5-1).

Petitioners  
Ex. 1032, p. 164

 


Figure 7-4 Step-down dc-dc converter.

7-3-1 CONTINUOUS-CONDUCTION MODE

Figure 7-5 shows the waveforms for the continuous-conduction mode of operation where the inductor current flows continuously [ $i_L(t) > 0$ ]. When the switch is on for a time duration  $t_{on}$ , the switch conducts the inductor current and the diode becomes reverse biased. This results in a positive voltage  $v_L = V_d - V_o$  across the inductor in Fig. 7-5a. This voltage causes a linear increase in the inductor current  $i_L$ . When the switch is turned off, because of the inductive energy storage,  $i_L$  continues to flow. This current now flows through the diode, and  $v_L = -V_o$  in Fig. 7-5b.

Petitioners

Ex. 1032, p. 165

 


Figure 7-5 Step-down converter circuit states (assuming  $i_L$  flows continuously): (a) switch on; (b) switch off.

Since in steady-state operation the waveform must repeat from one time period to the next, the integral of the inductor voltage  $v_L$  over one time period must be zero, as discussed in Chapter 3 (Eq. 3-51), where  $T_s = t_{on} + t_{off}$ :

$$\int_0^{T_s} v_L dt = \int_0^{t_{on}} v_L dt + \int_{t_{on}}^{T_s} v_L dt = 0$$

In Fig. 7-5, the foregoing equation implies that the areas A and B must be equal. Therefore,

$$(V_d - V_o)t_{on} = V_o(T_s - t_{on})$$

or

$$\frac{V_o}{V_d} = \frac{t_{on}}{T_s} = D \quad (\text{duty ratio}) \tag{7-3}$$

Therefore, in this mode, the voltage output varies linearly with the duty ratio of the switch for a given input voltage. It does not depend on any other circuit parameter. The foregoing equation can also be derived by simply averaging the voltage  $v_{oi}$  in Fig. 7-4b and recognizing that the average voltage across the inductor in steady-state operation is zero:

$$\frac{V_d t_{on} + 0 \cdot t_{off}}{T_s} = V_o$$

or

$$\frac{V_o}{V_d} = \frac{t_{on}}{T_s} = D$$

Neglecting power losses associated with all the circuit elements, the input power  $P_d$  equals the output power  $P_o$ :

$$P_d = P_o$$

Therefore,

$$V_d I_d = V_o I_o$$

and

$$\frac{I_o}{I_d} = \frac{V_d}{V_o} = \frac{1}{D} \tag{7-4}$$

Therefore, in the continuous-conduction mode, the step-down converter is equivalent to a dc transformer where the turns ratio of this equivalent transformer can be continuously controlled electronically in a range of 0–1 by controlling the duty ratio of the switch.

We observe that even though the average input current  $I_d$  follows the transformer relationship, the instantaneous input current waveform jumps from a peak value to zero every time the switch is turned off. An appropriate filter at the input may be required to eliminate the undesirable effects of the current harmonics.

### 7-3-2 BOUNDARY BETWEEN CONTINUOUS AND DISCONTINUOUS CONDUCTION

In this section, we will develop equations that show the influence of various circuit parameters on the conduction mode of the inductor current (continuous or discontinuous). At the edge of the continuous-current-conduction mode, Fig. 7-6a shows the waveforms for  $v_L$  and  $i_L$ . Being at the boundary between the continuous and the discontinuous mode, by definition, the inductor current  $i_L$  goes to zero at the end of the off period.

At this boundary, the average inductor current, where the subscript  $B$  refers to the boundary, is

$$I_{LB} = \frac{1}{2} i_{L,peak} = \frac{t_{on}}{2L} (V_d - V_o) = \frac{DT_s}{2L} (V_d - V_o) = I_{oB} \tag{7-5}$$

 


Figure 7-6 Current at the boundary of continuous–discontinuous conduction: (a) current waveform; (b)  $I_{LB}$  versus  $D$  keeping  $V_d$  constant.

Petitioners

Ex. 1032, p. 167

Therefore, during an operating condition (with a given set of values for  $T_s$ ,  $V_d$ ,  $V_o$ ,  $L$ , and  $D$ ), if the average output current (and, hence, the average inductor current) becomes less than  $I_{LB}$  given by Eq. 7-5, then  $i_L$  will become discontinuous.

**7-3-3 DISCONTINUOUS-CONDUCTION MODE**

Depending on the application of these converters, either the input voltage  $V_d$  or the output voltage  $V_o$  remains constant during the converter operation. Both of these types of operation are discussed below.

**7-3-3-1 Discontinuous-Conduction Mode with Constant  $V_d$**

In an application such as a dc motor speed control,  $V_d$  remains essentially constant and  $V_o$  is controlled by adjusting the converter duty ratio  $D$ .

Since  $V_o = DV_d$ , the average inductor current at the edge of the continuous-conduction mode from Eq. 7-5 is

$$I_{LB} = \frac{T_s V_d}{2L} D(1 - D) \tag{7-6}$$

Using this equation, we find that Fig. 7-6b shows the plot of  $I_{LB}$  as a function of the duty ratio  $D$ , keeping  $V_d$  and all other parameters constant. It shows that the output current required for a continuous-conduction mode is maximum at  $D = 0.5$ :

$$I_{LB,max} = \frac{T_s V_d}{8L} \tag{7-7}$$

From Eqs. 7-6 and 7-7

$$I_{LB} = 4I_{LB,max}D(1 - D) \tag{7-8}$$

Next the voltage ratio  $V_o/V_d$  will be calculated in the discontinuous mode. Let us assume that initially the converter is operating at the edge of continuous conduction, as in Fig. 7-6a, for given values of  $T$ ,  $L$ ,  $V_d$ , and  $D$ . If these parameters are kept constant and the output load power is decreased (i.e., the load resistance goes up), then the average inductor current will decrease. As is shown in Fig. 7-7, this dictates a higher value of  $V_o$  than before and results in a discontinuous inductor current.

 


Figure 7-7 Discontinuous conduction in step-down converter.

During the interval  $\Delta_2 T_s$  where the inductor current is zero, the power to the load resistance is supplied by the filter capacitor alone. The inductor voltage  $v_L$  during this interval is zero. Again, equating the integral of the inductor voltage over one time period to zero yields

$$(V_d - V_o) DT_s + (-V_o)\Delta_1 T_s = 0 \quad (7-9)$$

$$\therefore \frac{V_o}{V_d} = \frac{D}{D + \Delta_1} \quad (7-10)$$

where  $D + \Delta_1 < 1.0$ . From Fig. 7-7,

$$i_{L,\text{peak}} = \frac{V_o}{L} \Delta_1 T_s \quad (7-11)$$

Therefore,

$$I_o = i_{L,\text{peak}} \frac{D + \Delta_1}{2} \quad (7-12)$$

$$= \frac{V_o T_s}{2L} (D + \Delta_1) \Delta_1 \quad (\text{using Eq. 7-11}) \quad (7-13)$$

$$= \frac{V_d T_s}{2L} D \Delta_1 \quad (\text{using Eq. 7-10}) \quad (7-14)$$

$$= 4I_{LB,\text{max}} D \Delta_1 \quad (\text{using Eq. 7-7}) \quad (7-15)$$

$$\therefore \Delta_1 = \frac{I_o}{4I_{LB,\text{max}} D} \quad (7-16)$$

From Eqs. 7-10 and 7-16

$$\frac{V_o}{V_d} = \frac{D^2}{D^2 + \frac{1}{4}(I_o/I_{LB,\text{max}})} \quad (7-17)$$

Figure 7-8 shows the step-down converter characteristic in both modes of operation for a constant  $V_d$ . The voltage ratio ( $V_o/V_d$ ) is plotted as a function of  $I_o/I_{LB,\text{max}}$  for various values of duty ratio using Eqs. 7-3 and 7-17. The boundary between the continuous and the discontinuous mode, shown by the dashed curve, is established by Eq. 7-3 and 7-8.

### 7-3-3-2 Discontinuous-Conduction Mode with Constant $V_o$

In applications such as regulated dc power supplies,  $V_d$  may fluctuate but  $V_o$  is kept constant by adjusting the duty ratio  $D$ .

Since  $V_d = V_o/D$ , the average inductor current at the edge of the continuous-conduction mode from Eq. 7-5 is

$$I_{LB} = \frac{T_s V_o}{2L} (1 - D) \quad (7-18)$$

Equation 7-18 shows that if  $V_o$  is kept constant, the maximum value of  $I_{LB}$  occurs at  $D = 0$ :

$$I_{LB,\text{max}} = \frac{T_s V_o}{2L} \quad (7-19)$$



 


Figure 7-8 Step-down converter characteristics keeping  $V_d$  constant.

It should be noted that the operation corresponding to  $D = 0$  and a finite  $V_o$  is, of course, hypothetical because it would require  $V_d$  to be infinite.

From Eqs. 7-18 and 7-19

$$I_{LB} = (1 - D)I_{LB,max} \tag{7-20}$$

For the converter operation where  $V_o$  is kept constant, it will be useful to obtain the required duty ratio  $D$  as a function of  $I_o/I_{LB,max}$ . Using Eqs. 7-10 and 7-13 (which are valid in the discontinuous-conduction mode whether  $V_o$  or  $V_d$  is kept constant) along with Eq. 7-19 for the case where  $V_o$  is kept constant yields

$$D = \frac{V_o}{V_d} \left( \frac{I_o/I_{LB,max}}{1 - V_o/V_d} \right)^{1/2} \tag{7-21}$$

The duty ratio  $D$  as a function of  $I_o/I_{LB,max}$  is plotted in Fig. 7-9 for various values of  $V_d/V_o$ , keeping  $V_o$  constant. The boundary between the continuous and the discontinuous mode of operation is obtained by using Eq. 7-20.

### 7-3-4 OUTPUT VOLTAGE RIPPLE

In the previous analysis, the output capacitor is assumed to be so large as to yield  $v_o(t) = V_o$ . However, the ripple in the output voltage with a practical value of capacitance can be calculated by considering the waveforms shown in Fig. 7-10 for a continuous-conduction mode of operation. Assuming that all of the ripple component in  $i_L$  flows through the capacitor and its average component flows through the load resistor, the shaded area in Fig. 7-10 represents an additional charge  $\Delta Q$ . Therefore, the peak-to-peak voltage ripple  $\Delta V_o$  can be written as

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{1}{C} \frac{1}{2} \frac{\Delta I_L T_s}{2}$$

From Fig. 7-5 during  $t_{off}$

$$\Delta I_L = \frac{V_o}{L}(1 - D)T_s \tag{7-22}$$

Petitioners

Ex. 1032, p. 170

 


Figure 7-9 Step-down converter characteristics keeping  $V_o$  constant.

 


Figure 7-10 Output voltage ripple in a step-down converter.

Therefore, substituting  $\Delta I_L$  from Eq. 7-22 into the previous equation gives

$$\Delta V_o = \frac{T_s}{8C} \frac{V_o}{L} (1-D) T_s \quad (7-23)$$

$$\therefore \frac{\Delta V_o}{V_o} = \frac{1}{8} \frac{T_s^2 (1-D)}{LC} = \frac{\pi^2}{2} (1-D) \left( \frac{f_c}{f_s} \right)^2 \quad (7-24)$$

where switching frequency  $f_s = 1/T_s$  and

$$f_c = \frac{1}{2\pi\sqrt{LC}} \quad (7-25)$$

Equation 7-24 shows that the voltage ripple can be minimized by selecting a corner frequency  $f_c$  of the low-pass filter at the output such that  $f_c \ll f_s$ . Also, the ripple is independent of the output load power, so long as the converter operates in the continuous-conduction mode. A similar analysis can be performed for the discontinuous-conduction mode.

We should note that in switch-mode dc power supplies, the percentage ripple in the output voltage is usually specified to be less than, for instance, 1%. Therefore, the analysis in the previous sections assuming  $v_o(t) = V_o$  is valid. It should be noted that the output ripple in Eq. 7-24 is consistent with the discussion of the low-pass filter characteristic in Fig. 7-4c.

## 7-4 STEP-UP (BOOST) CONVERTER


Figure 7-11 shows a step-up converter. Its main application is in regulated dc power supplies and the regenerative braking of dc motors. As the name implies, the output voltage is always greater than the input voltage. When the switch is on, the diode is reversed biased, thus isolating the output stage. The input supplies energy to the inductor. When the switch is off, the output stage receives energy from the inductor as well as from the input. In the steady-state analysis presented here, the output filter capacitor is assumed to be very large to ensure a constant output voltage  $v_o(t) \approx V_o$ .

### 7-4-1 CONTINUOUS-CONDUCTION MODE

Figure 7-12 shows the steady-state waveforms for this mode of conduction where the inductor current flows continuously [ $i_L(t) > 0$ ].

Since in steady state the time integral of the inductor voltage over one time period must be zero,
 
$$V_d t_{\text{on}} + (V_d - V_o) t_{\text{off}} = 0$$



Petitioners  
Ex. 1032, p. 172

Figure 7-11 Step-up dc-dc converter.

The presence of the right-half zero can be explained by noting that in a flyback converter operating in a continuous mode, if the duty ratio  $d$  is increased instantaneously, the output voltage decreases momentarily because the inductor current has not had the time to increase, but the time interval  $(1 - d)T_s$  during which the inductor transfers energy to the output stage has been suddenly decreased. This initial decline in the output voltage with the increase in  $d$  is opposite of what eventually takes place. This effect results in a zero in the right-half plane, which introduces phase lag in the transfer function  $\bar{v}_o(s)/\bar{d}(s)$ .

In a flyback converter operating in a discontinuous mode, the foregoing effect does not occur and the output voltage always increases with the increased duty ratio. Therefore, in the discontinuous mode of operation, the right-half-plane zero in the transfer function of Eq. 10-86 does not exist; thus, compensating the feedback loop to provide enough gain and phase margins is simpler.

**10-5-2 TRANSFER FUNCTION  $\bar{d}(s)/\bar{v}_r(s)$  OF THE DIRECT DUTY RATIO PULSE-WIDTH MODULATOR**

In the direct duty ratio pulse-width modulator, the control voltage  $v_c(t)$ , which is the output of the error amplifier, is compared with a repetitive waveform  $v_r(t)$ , which establishes the switching frequency  $f_s$ , as shown in Fig. 10-23a. The control voltage  $v_c(t)$  consists of a dc component and a small ac perturbation

$$v_c(t) = V_c + \bar{v}_c(t) \tag{10-87}$$

where  $\bar{v}_c(t)$  is in a range between zero and  $\hat{V}_r$ , as shown in Fig. 10-23a. Here  $\bar{v}_c(t)$  is a sinusoidal ac perturbation in the control voltage at a frequency  $\omega$ , where  $\omega$  is much smaller than the switching frequency  $\omega_s (=2\pi f_s)$ . The ac perturbation in the control voltage can be expressed as

$$\bar{v}_c(t) = a \sin(\omega t - \phi) \tag{10-88}$$

by means of an amplitude  $a$  and an arbitrary phase angle  $\phi$ .

In Fig. 10-23b, the instantaneous switch duty ratio  $d(t)$  is as follows:

$$d(t) = \begin{cases} 1.0 & \text{if } v_c(t) \geq v_r(t) \\ 0 & \text{if } v_c(t) < v_r(t) \end{cases} \tag{10-89}$$

$$\tag{10-90}$$

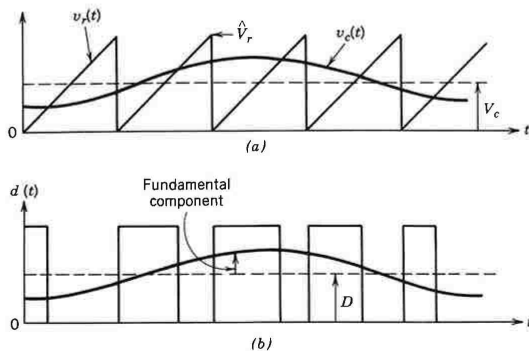


Figure 10-23 Pulse-width modulator.

Petitioners

Ex. 1032, p. 331

Similar to the analysis of sinusoidal PWM carried out in Chapter 8,  $d(t)$  in Fig. 10-23b can be expressed in terms of the Fourier series as

$$d(t) = \frac{V_c}{\hat{V}_r} + \frac{a}{\hat{V}_r} \sin(\omega t - \phi) + \text{other high-frequency components} \quad (10-91)$$

The higher frequency components in the output voltage  $v_o$  due to the high-frequency components in  $d(t)$  are eliminated because of the low-pass filter at the output of the converter. Therefore, the high-frequency components in Eq. 10-91 can be ignored. In terms of its dc value and its ac perturbation

$$d(t) = D + \tilde{d}(t) \quad (10-92)$$

Comparing Eqs. 10-91 and 10-92 yields

$$D = \frac{V_c}{\hat{V}_r} \quad (10-93)$$

and

$$\tilde{d}(t) = \frac{a}{\hat{V}_r} \sin(\omega t - \phi) \quad (10-94)$$

From Eqs. 10-88 and 10-94, the transfer function  $T_m(s)$  of the modulator is given by

$$T_m(s) = \frac{\tilde{d}(s)}{\tilde{v}_c(s)} = \frac{1}{\hat{V}_r} \quad (10-95)$$

Therefore, the theoretical transfer function of the pulse-width modulator is surprisingly simple, without any time delays. However, the time delay associated with the comparator can lead to a delay in the modulator response.

■ **Example 10-2** In practice, the transfer function of the modulator may not have to be calculated from Eq. 10-95. Figure 10-24 shows the approximate transfer function of a commonly used PWM integrated circuit, supplied as a part of the data sheets, in terms of the duty ratio  $d$  as a function of the control voltage  $v_c$ , where  $v_c$  is the output of the error amplifier.

Calculate the transfer function  $\tilde{d}(s)/\tilde{v}_c(s)$  for this PWM integrated circuit.

 


Figure 10-24 Pulse-width modulator transfer function.

Petitioners  
Ex. 1032, p. 332

**Solution** For this particular modulator, the duty ratio  $d$  increases from 0 (at  $v_c = 0.8$  V) to 0.95 (at  $v_c = 3.6$  V). Therefore, the slope of the transfer function in Fig. 10-24 is equal to the transfer function of this modulator:

$$\begin{aligned} \frac{\tilde{d}(s)}{\tilde{v}_c(s)} &= \frac{\Delta d}{\Delta v_c} \\ &= \frac{0.95 - 0}{3.6 - 0.8} \approx 0.34 \end{aligned} \quad (10-96)$$

With this modulator, the transfer function between  $v_o$  and the control voltage  $v_c$  can be obtained as

$$T_1(s) = \frac{\tilde{v}_o(s)}{\tilde{v}_c(s)} = \frac{\tilde{v}_o(s)}{\tilde{d}(s)} \frac{\tilde{d}(s)}{\tilde{v}_c(s)} = T_p(s)T_m(s) \quad (10-97)$$

The gain plot of the transfer function  $\tilde{v}_o(s)/\tilde{v}_c(s)$  can be obtained by adjusting the gain curve in the Bode plot of Fig. 10-21a or Fig. 10-22a to account for a constant gain of 0.34 ( $= -9.37$  dB) of the modulator. Assuming zero delay in the modulator, the phase plot of  $\tilde{v}_o(s)/\tilde{v}_c(s)$  is the same as that of  $\tilde{v}_o(s)/\tilde{d}(s)$ . ■

### 10-5-3 COMPENSATION OF THE FEEDBACK SYSTEM USING A DIRECT DUTY RATIO PULSE-WIDTH MODULATOR

In the switch-mode power supply shown in Fig. 10-19b, the overall open-loop transfer function is

$$T_{OL}(s) = T_1(s)T_c(s) \quad (10-98)$$

where  $T_1(s)$  is as given by Eq. 10-97 and

$$T_c(s) = \text{transfer function of compensated error amplifier} \quad (10-99)$$

For a given  $T_1(s)$ , the transfer function of the compensated error amplifier  $T_c(s)$  must be properly tailored so that  $T_{OL}(s)$  meets the performance requirements expected of the power supply. Some of the desired characteristics of the open-loop transfer function  $T_{OL}(s)$  are as follows:

1. The gain at low frequencies should be high to minimize the steady-state error in the power supply output.
2. The crossover frequency is the frequency at which the gain of  $T_{OL}(s)$  falls to 1.0 (0 dB), as shown in Fig. 10-25. This crossover frequency  $\omega_{\text{cross}}$  should be as high as possible but approximately an order of magnitude below the switching frequency to allow the power supply to respond quickly to the transients, such as a sudden change of load.
3. The phase margin (PM) is defined by means of Fig. 10-25 as

$$PM = \phi_{OL} + 180^\circ \quad (10-100)$$

where  $\phi_{OL}$  is the phase angle of  $T_{OL}(s)$  at the crossover frequency and is negative. The phase margin, which should be a positive quantity in Eq. 10-100, determines the transient response of the output voltage in response to sudden changes in the load and the input voltage. A phase margin in a range of  $45^\circ$ – $60^\circ$  is desirable.

 


Figure 10-25 Gain and phase margins.

To meet these requirements simultaneously, a general error amplifier is shown in Fig. 10-26, where the amplifier can be assumed to be ideal. One of the inputs to the amplifier is the output voltage  $v_o$  of the converter; the other input is the desired (reference) value  $V_{ref}$  of  $v_o$ . The output of the error amplifier is the control voltage  $v_c$ . In terms of  $Z_i$  and  $Z_f$  in Fig. 10-26, the transfer function between the input and the output perturbations can be obtained as

$$\frac{\bar{v}_c(s)}{\bar{v}_o(s)} = -\frac{Z_f(s)}{Z_i(s)} = -T_c(s) \tag{10-101}$$

where  $T_c(s)$  is as defined in Fig. 10-19b.

One of the options in the selection of  $T_c(s)$  is to introduce a pole-zero pair in addition to a pole at the origin so that  $T_c(s)$  is of the form

$$T_c(s) = \frac{A(s + \omega_z)}{s(s + \omega_p)} \tag{10-102}$$

where  $A$  is positive and  $\omega_z < \omega_p$ . In Eq. 10-102, due to the pole at the origin, the phase of  $T_c(s)$  starts with  $-90^\circ$ , as shown in Fig. 10-27a. The presence of the zero causes the phase angle to increase (or in other words provides a "boost") to be something greater than  $-90^\circ$ . Eventually, because of the pole at  $\omega_p$ , the phase angle of  $T_c(s)$  comes back down to  $-90^\circ$ . The gain plot is also shown in Fig. 10-27a. The parameters in Eq. 10-102 can be chosen such that the minimum phase lag in  $T_c(s)$  occurs at the specified (desired) crossover frequency of the overall open-loop transfer function  $T_{OL}(s)$ .

 


Figure 10-26 A general compensated error amplifier.

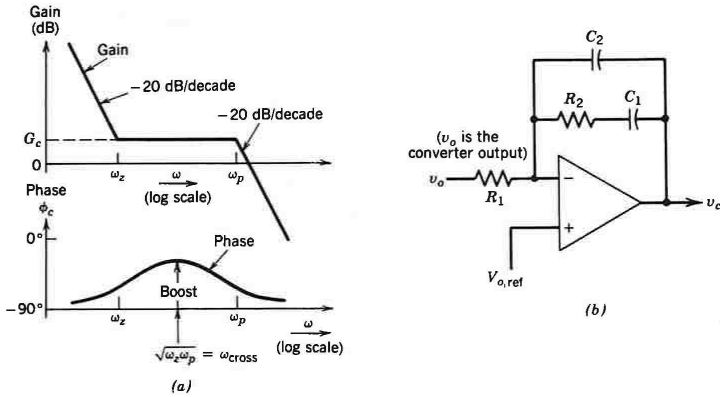


Figure 10-27 Error amplifier.

$$T_c(s) = \frac{1}{R_1 C_2} \frac{s + \omega_z}{s(s + \omega_p)}$$

The transfer function in Eq. 10-102 can be realized by means of the amplifier network shown in Fig. 10-27b, where

$$T_c(s) = \frac{1}{R_1 C_2} \frac{s + \omega_z}{s(s + \omega_p)} \tag{10-103}$$

$$\omega_z = \frac{1}{R_2 C_1} \tag{10-104}$$

$$\omega_p = \frac{C_1 + C_2}{R_2 C_1 C_2} \tag{10-105}$$

A step-by-step explanation that is easy to follow in the selection of the foregoing parameters has been provided in reference 16 using a *K*-factor approach. This procedure suggests that as a first-step, the crossover frequency  $\omega_{cross}$ , where  $|T_{OL}(s)|$  would equal 0 dB, should be selected. This crossover frequency also defines the frequency in Fig. 10-27a, where the minimum phase lag occurs in the transfer function of  $T_c(s)$ . The *K* factor is used such that in the transfer function  $T_c(s)$  of Eq. 10-103

$$\omega_z = \frac{\omega_{cross}}{K} \tag{10-106}$$

$$\omega_p = K \omega_{cross} \tag{10-107}$$

It is shown in reference 16 that *K* in Eqs. 10-106 and 10-107 is related to the boost (defined in Fig. 10-27a) in the following manner:

$$K = \tan\left(45^\circ + \frac{\text{boost}}{2}\right) \tag{10-108}$$

Therefore, the next step is to define the phase margin (PM) and, hence, the boost needed

Petitioners

Ex. 1032, p. 335



from the error amplifier at the crossover frequency to calculate  $K$  in Eqs. 10-106 and 10-107. From the definition of phase margin in Eq. 10-100

$$PM = 180^\circ + \phi_1 + \phi_c \quad (10-109)$$

where  $\phi_c$  is the phase angle of  $T_c(s)$  at the crossover frequency. From Eq. 10-97

$$\phi_1 = \phi_p(s) + \phi_m(s) \quad (10-110)$$

where  $\phi_1$  is the phase angle of  $T_1(s)$ ,  $\phi_p(s)$  is the phase angle of the power stage  $T_p(s)$ , and  $\phi_m(s)$  is the phase angle (if any) of the modulator  $T_m(s)$ . From the phase plot of the transfer function  $T_c(s)$  shown in Fig. 10-27a

$$\phi_c = -90^\circ + \text{boost} \quad (10-111)$$

From Eqs. 10-109 and 10-111,

$$\text{boost} = PM - \phi_1 - 90^\circ \quad (10-112)$$

Therefore, once the phase margin (usually in a range of  $45^\circ$ – $60^\circ$ ) is chosen, the boost is defined from Eq. 10-112 where  $\phi_1$  (assuming  $\phi_m$  to be zero) can be obtained from Fig. 10-21b or Fig. 10-22b at the frequency chosen to be the crossover frequency. Knowing the boost,  $K$  can be calculated from Eq. 10-108.

The next step in the design procedure is to ensure that the gain  $G_{OL}$  of the overall open-loop is equal to 1 (i.e.,  $G_{OL} = |T_{OL}(s)| = 1$ ) at the chosen crossover frequency. This requires that from Eq. 10-98, the gain  $G_c$  of the compensated error amplifier at  $\omega_{\text{cross}}$  be as follows:

$$G_c(\text{at } \omega_{\text{cross}}) = \frac{1}{G_1(\text{at } \omega_{\text{cross}})} \quad (10-113)$$

where  $G_1$  is the magnitude  $|T_1(j\omega_{\text{cross}})|$  of the transfer function  $T_1(s) = T_p(s)T_m(s)$  at  $\omega_{\text{cross}}$ . Therefore, at  $\omega = \omega_{\text{cross}}$ , from Eq. 10-113 and by the substitution of Eqs. 10-104 through 10-107 into Eq. 10-103,

$$G_c = \frac{1}{KC_2R_1\omega_{\text{cross}}} = \frac{1}{G_1} \quad (10-114)$$

In the circuit of Fig. 10-27b,  $R_1$  is chosen arbitrarily and the rest of the circuit parameters can be calculated as follows from the  $K$ -factor procedure outlined before using Eqs. 10-104 through 10-107 and Eq. 10-114,

$$C_2 = \frac{G_1}{KR_1\omega_{\text{cross}}} \quad (10-115)$$

$$C_1 = C_2(K^2 - 1) \quad (10-116)$$

$$R_2 = \frac{K}{(C_1\omega_{\text{cross}})} \quad (10-117)$$

For the converters, such as a flyback converter operating in a continuous mode, it may be necessary to use an error amplifier that has two pairs of poles and zeros in addition to the pole at the origin for a proper compensation.

#### 10-5-4 VOLTAGE FEED-FORWARD PWM CONTROL

In the direct duty ratio PWM control discussed in the previous two sections, if the input voltage changes, an error is produced in the output voltage, which eventually gets cor-

Petitioners

Ex. 1032, p. 336

rected by the feedback control. This results in a slow dynamic performance in regulating the output in response to the changes in input voltage.

If the duty ratio could be adjusted directly to accommodate the change in the input voltage, then the converter output would remain unchanged. This can be accomplished by feeding the input voltage level to the PWM IC. The PWM switching strategy here is very similar to the one discussed in connection with the direct duty ratio PWM control except for one difference: the ramp (and, hence, the peak) of the sawtooth waveform does not stay constant but varies in direct proportion to the input voltage, as shown in Fig. 10-28. This shows how an increased input voltage (hence, increased  $\hat{V}_r$ ) results in a decreased duty ratio, shown by dashed curves in Fig. 10-28. This type of control in step-down derived converters (e.g., forward converters) results in  $\bar{v}_o(s)/\bar{v}_d(s)$  equal to zero and hence in an excellent inherent regulation for the changes in the input voltage. The same is true for a flyback converter operating in a complete demagnetization mode.

If this voltage feed-forward is implemented in a double-ended power supply (like push-pull, half-bridge, full bridge), then care must be taken to provide a dynamic volt-time balance so that the on times of the two switches are kept equal on a dynamic basis to prevent the saturation of the high-frequency isolation transformer.

### 10-5-5 CURRENT-MODE CONTROL

The PWM direct duty ratio control discussed so far is shown in Fig. 10-29a, where the control voltage  $v_c$  (amplified error signal between the actual output and the reference) controls the duty ratio of the switch by comparing the control voltage with a fixed-frequency sawtooth waveform. This control of the switch duty ratio adjusts the voltage across the inductor and hence the inductor current (which feeds the output stage) and eventually brings the output voltage to its reference value.

In a current-mode control, an additional inner control loop is used as shown in Fig. 10-29b, where the control voltage  $v_c$  directly controls the output inductor current that feeds the output stage and thus the output voltage. Ideally, the control voltage should act to directly control the average value of the inductor current for the fastest response, though, as we will see later, various types of current-mode controls tend to accomplish this differently. The fact that the current feeding the output stage is controlled directly in a current-mode control has a profound effect on the dynamic behavior of the negative-feedback control loop.

 


Figure 10-28 Voltage feed-forward: effect on duty ratio.

Petitioners  
Ex. 1032, p. 337

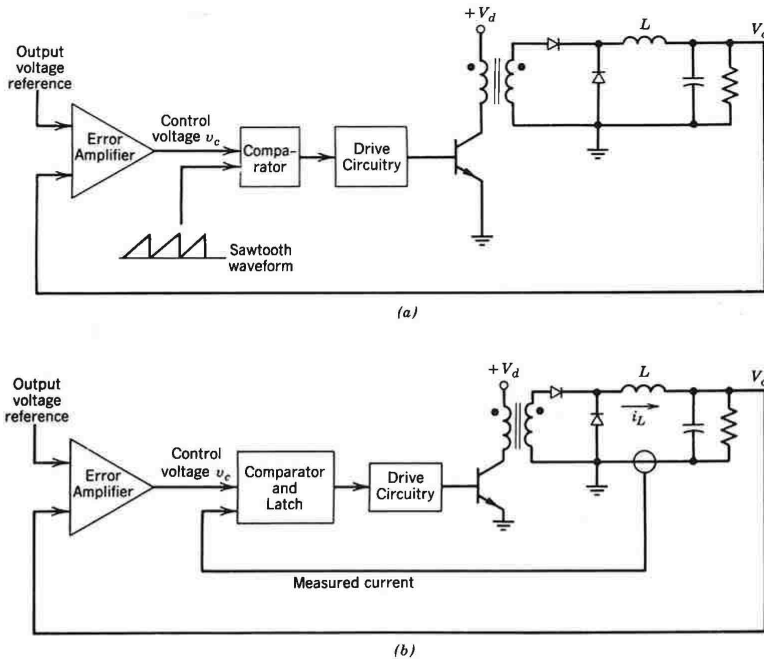


Figure 10-29 PWM duty ratio versus current-mode control: (a) PWM duty ratio control; (b) current-mode control.


There are three basic types of current-mode controls:

1. Tolerance band control
2. Constant-“off”-time control
3. Constant-frequency control with turn-on at clock time

In all these types of controls, either the inductor current or the switch current, which is proportional to the output inductor current, is measured and compared with the control voltage.

In the *tolerance band control*, the control voltage  $v_c$  dictates the average value of the inductor current as shown in Fig. 10-30a. The term  $\Delta I_L$  is a design parameter. The switching frequency depends on  $\Delta I_L$ , the converter parameters, and the operating conditions. This direct control over the average value of  $i_L$  is a very desirable feature of this type of control. However, this scheme works well only in the continuous-current-conduction mode. Otherwise, in the discontinuous-current-conduction mode, the inductor current becomes zero (though  $\frac{1}{2}\Delta I_L$  would actually be demanding a negative  $i_L$ , which is not possible). If the controller is not designed to handle this discontinuous current when  $i_L$  is zero and  $i_L$  being demanded by the controller is negative, the switch will never turn on and the inductor current will decay to zero.

In the *constant-off-time control*, the control voltage dictates  $\hat{i}_L$ , as is shown in Fig. 10-30b. Once  $\hat{i}_L$  is reached, the switch turns off for a fixed (constant) off time, which is

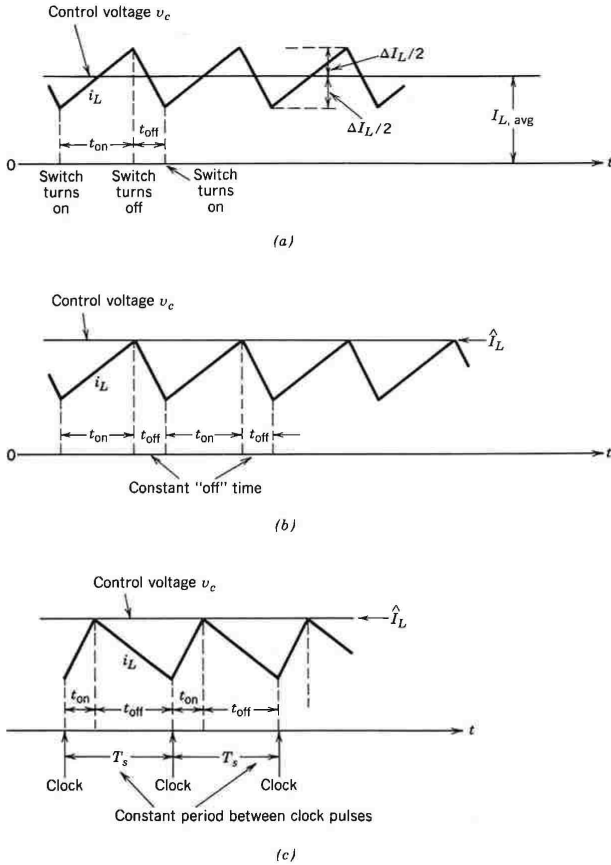


**Figure 10-30** Three types of current-mode control: (a) tolerance band control; (b) constant-off-time control; (c) constant frequency with turn-on at clock time.

a design parameter. Here also, the switching frequency is not fixed and depends on the converter parameters and its operating condition.

The *constant-frequency control with a turn-on at clock time* is thus far the most common type of current-mode control. Here, the switch is turned on at the beginning of each constant-frequency switching time period. The control voltage dictates  $\hat{I}_L$  and the instant at which the switch is turned off, as shown in Fig. 10-30c. The switch remains off until the beginning of the next switching cycle. A constant switching frequency makes it easier to design the output filter.

In the current-mode control in practice, a slope compensation is added to the control voltage, as shown in Fig. 10-31, to provide stability, to prevent subharmonic oscillations, and to provide a feed-forward property. Figure 10-31 shows the waveforms for a forward

 

**Figure 10-31** Slope compensation in current-mode control ( $D_2$  is smaller for a higher input voltage with a constant  $V_o$ ).

converter of the type shown in Fig. 10-29b, where the slope of the slope compensation waveform is one-half of the slope of the inductor current when the switch is off. With given input and output voltages, the duty ratio is  $D_1$  and the waveform of the inductor current  $i_L$  is shown by the solid lines. If the input voltage is increased but the output voltage is to remain unaffected, the duty ratio decreases to  $D_2$  and the inductor current waveform is shown by dashed lines. The average value of the inductor current, which equals the load current, remains the same in both cases in spite of a change in the input voltage. This shows the voltage feed-forward property of the current-mode control with a proper slope compensation.

The current-mode control has several advantages over the conventional direct duty ratio PWM control:

1. *It limits peak switch current.* Since either the switch current is directly measured or the current is measured somewhere in the circuit (like through the output inductor) where it represents the switch current without delay, the peak value of the switch current can be limited by simply putting an upper limit on the control voltage. This can be easily accomplished in the controllers that control  $\hat{i}_L$ .
2. *It removes one pole* (corresponding to the output filter inductor) from the control-to-output transfer function  $\bar{v}_o(s)/\bar{v}_c(s)$ , thus simplifying the compensation in the negative-feedback system, especially in the presence of the right-half-plane zero.
3. It allows a *modular design* of power supplies by equal current sharing where several power supplies can be operated in parallel and provide equal currents, if the same control voltage is fed to all the modules.
4. It results in a *symmetrical flux excursion* in a push-pull converter, thus eliminating the problem of transformer core saturation.
5. *It provides input voltage feed-forward.* As shown by Fig. 10-31, an input voltage feed-forward is automatically accomplished, resulting in an excellent rejection of input line transients.

Petitioners

Ex. 1032, p. 340