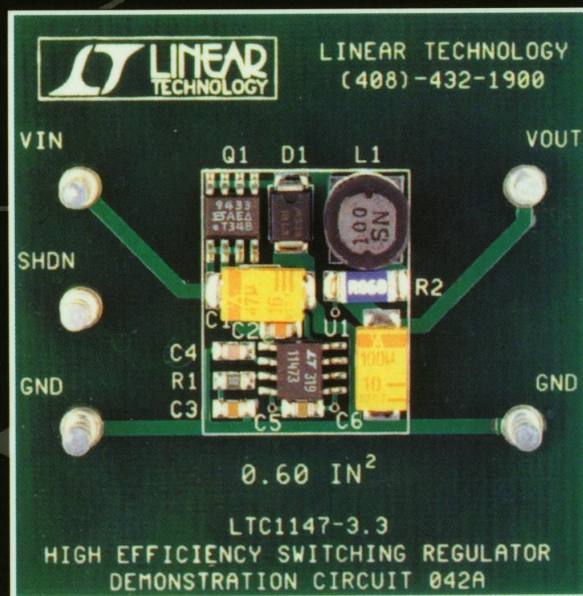


JOHN D. LENK

SIMPLIFIED DESIGN OF SWITCHING POWER SUPPLIES



EDN SERIES FOR DESIGN ENGINEERS

Simplified Design of Switching Power Supplies


John D. Lenk

Butterworth-Heinemann

Boston Oxford Melbourne Singapore Toronto Munich New Delhi Tokyo


Cover photograph courtesy of Linear Technology Corporation.

Copyright © 1995 by Butterworth-Heinemann

 A member of the Reed Elsevier group

All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher.

 Recognizing the importance of preserving what has been written, it is the policy of Butterworth-Heinemann to have the books it publishes printed on acid-free paper, and we exert our best efforts to that end.

Library of Congress Cataloging-in-Publication Data

Lenk, John D.

Simplified design of switching power supplies / by John D. Lenk.
p. cm.

Includes bibliographical references and index.

ISBN 0-7506-9507-2 (hardcover)

ISBN 0-7506-9821-7 (paperback)

1. Electronic apparatus and appliances—Power supply—Design and construction. 2. Switching power supplies—Design and construction. I. Title.

TK7868.P6L456 1995

621.381'044—dc20

94-32727
CIP

British Library Cataloguing-in-Publication Data

A catalogue record for this book is available from the British Library.

The publisher offers special discounts on bulk orders of this book.
For information, please contact:

Manager of Special Sales
Butterworth-Heinemann
313 Washington Street
Newton, MA 02158-1626
Tel: 617-928-2500
Fax: 617-928-2620

For information on all electronics publications available, contact our World Wide Web home page at: <http://www.bh.com/bh/>

109876543

Transferred to digital printing 2005

1.1.4 Transistor and Diode Characteristics

Switching regulators must use transistors with a gain-bandwidth product (fT) of at least 4 MHz to operate efficiently (an fT of 30 MHz is even better). Darlington transistors and MOSFETs are also used in switching regulators.

A fast-recovery rectifier, or a Schottky barrier diode, is used as a free-wheeling clamp diode to keep the switching-transistor load line within safe operating limits and to increase efficiency. Other solid-state devices used in some switching regulators include gates, flip-flops (FFs), op-amp comparators, timers, and rectifiers.

1.2 Typical Switching-Regulator Circuits

Figure 1-2 shows four typical PNP/NPN switching-regulator circuits. All of the circuits have the following common elements: switching transistor, clamp diode, LC filter, and a logic or control block. None of the circuits provide full isolation between the line and load, as would be the case if more than one series transistor is used. However, the one-transistor design is the simplest and most economical.

It is usually desirable to have at least one line in common with the input and output to reduce ground loops. The one-line approach also determines whether the output voltage is considered positive or negative. However, most circuits can operate from either supply because the input and output grounds are usually isolated. The one-transistor, one-line approach is the most popular switching-regulator design.


In the circuits of Figs. 1-2(a) and 1-2(b), the logic or control operates from the load voltage. Such circuits are not self-starting, and provisions must be made to operate from the line during start-up (and in the event of short circuits).

In the circuits of Figs. 1-2(c) and 1-2(d), the logic operates continuously from the line and is isolated from the load voltage. The sense and feedback elements must be electrically isolated (sometimes with an optocoupler).


The circuits of Figs. 1-2(b) and 1-2(d) are generally used in line-operated supplies because economical high-voltage NPN transistors are available whereas PNP types are not. Of the two, the circuit of Fig. 1-2(d) is most popular, because the logic is tied directly to the series switch and switching is more efficient. Driver transformers are used in some designs to interface between the logic and switching transistors. In such a case, the switching transistor may be either PNP or NPN.

Figure 1-3 shows three typical MOSFET switching-regulator (or -converter) circuits, representing the three basic configurations: *buck*, *boost*, and *buck-boost* (all of which are described more fully in Section 1.5). In brief, each of the three configurations meets a particular need. When output voltage is greater than the input, the converter is usually operated in the positive *voltage-boost* circuit (also known as a *step-up* converter). The buck circuit is used when the input voltage is always greater than the desired output voltage (and is also known as a *step-down* converter). The

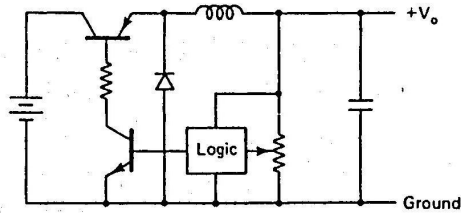
4 SIMPLIFIED DESIGN OF SWITCHING POWER SUPPLIES



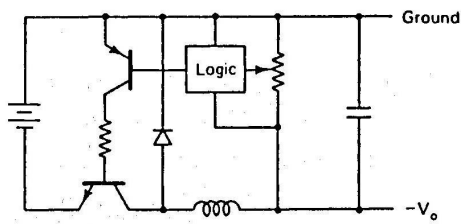
(a) Positive output, common logic and load



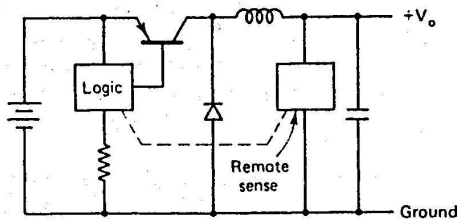(b) Negative output, common logic and load



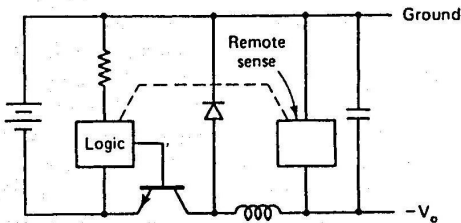(c) Positive output, isolated logic and load



(d) Negative output, isolated logic and load

Figure 1-2. Four typical switching-regulator circuits

Explore Litigation Insights

Docket Alarm provides insights to develop a more informed litigation strategy and the peace of mind of knowing you're on top of things.

Real-Time Litigation Alerts



Keep your litigation team up-to-date with **real-time alerts** and advanced team management tools built for the enterprise, all while greatly reducing PACER spend.

Our comprehensive service means we can handle Federal, State, and Administrative courts across the country.

Advanced Docket Research



With over 230 million records, Docket Alarm's cloud-native docket research platform finds what other services can't. Coverage includes Federal, State, plus PTAB, TTAB, ITC and NLRB decisions, all in one place.

Identify arguments that have been successful in the past with full text, pinpoint searching. Link to case law cited within any court document via Fastcase.

Analytics At Your Fingertips



Learn what happened the last time a particular judge, opposing counsel or company faced cases similar to yours.

Advanced out-of-the-box PTAB and TTAB analytics are always at your fingertips.

API

Docket Alarm offers a powerful API (application programming interface) to developers that want to integrate case filings into their apps.

LAW FIRMS

Build custom dashboards for your attorneys and clients with live data direct from the court.

Automate many repetitive legal tasks like conflict checks, document management, and marketing.

FINANCIAL INSTITUTIONS

Litigation and bankruptcy checks for companies and debtors.

E-DISCOVERY AND LEGAL VENDORS

Sync your system to PACER to automate legal marketing.