





## VALUES OF MATERIAL AND PHYSICAL CONSTANTS

Name	Symbol	Value	Units
Room temperature	$T$	300 (= 27°C)	K
Boltzman constant	$k$	$1.38 \times 10^{-23}$	J/K
Electron charge	$q$	$1.6 \times 10^{-19}$	C
Thermal voltage	$\phi_T = kT/q$	26	mV (at 300 K)
Intrinsic Carrier Concentration (Silicon)	$n_i$	$1.5 \times 10^{10}$	$\text{cm}^{-3}$ (at 300 K)
Permittivity of Si	$\epsilon_{si}$	$1.05 \times 10^{-12}$	F/cm
Permittivity of SiO <sub>2</sub>	$\epsilon_{ox}$	$3.5 \times 10^{-13}$	F/cm
Resistivity of Al	$\rho_{Al}$	$2.7 \times 10^{-8}$	$\Omega\text{-m}$
Resistivity of Cu	$\rho_{Cu}$	$1.7 \times 10^{-8}$	$\Omega\text{-m}$
Magnetic permeability of vacuum (similar for SiO <sub>2</sub> )	$\mu_0$	$12.6 \times 10^{-7}$	Wb/Am
Speed of light (in vacuum)	$c_0$	30	cm/nsec
Speed of light (in SiO <sub>2</sub> )	$c_{ox}$	15	cm/nsec

UNIVERSITY OF MICHIGAN LIBRARIES

# FORMULAS AND EQUATIONS

## Diode

$$I_D = I_S(e^{V_D/\phi_T} - 1) = Q_D/\tau_T$$

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} \times [( \phi_0 - V_{high} )^{1-m} - ( \phi_0 - V_{low} )^{1-m}]$$

## MOS Transistor

$$V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

$$I_D = \frac{k'_n W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \text{ (sat)}$$

$$I_D = v_{sat} C_{ox} W \left( V_{GS} - V_T - \frac{V_{DSAT}}{2} \right) (1 + \lambda V_{DS}) \text{ (velocity sat)}$$

$$I_D = k'_n \frac{W}{L} \left( (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right) \text{ (triode)}$$

$$I_D = I_S e^{\frac{V_{GS}}{kT/q}} \left( 1 - e^{-\frac{V_{DS}}{kT/q}} \right) \text{ (subthreshold)}$$

## Deep Submicron MOS Unified Model

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left( V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$

$$\text{with } V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT})$$

$$\text{and } V_{GT} = V_{GS} - V_T$$

## MOS Switch Model

$$R_{eq} = \frac{1}{2} \left( \frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{5}{6} \lambda V_{DD} \right)$$

## Inverter

$$V_{OH} = f(V_{OL})$$

$$V_{OL} = f(V_{OH})$$

$$V_M = f(V_M)$$

$$t_p = 0.69 R_{eq} C_L = \frac{C_L (V_{swing}/2)}{I_{avg}}$$

$$P_{dyn} = C_L V_{DD} V_{swing} f$$

$$P_{stat} = V_{DD} I_{DD}$$

## Static CMOS Inverter

$$V_{OH} = V_{DD}$$

$$V_{OL} = GND$$

$$V_M \approx \frac{r V_{DD}}{1+r} \text{ with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$\text{with } g \approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left( \frac{R_{eqn} + R_{eqp}}{2} \right)$$

$$P_{av} = C_L V_{DD}^2 f$$

## Interconnect

$$\text{Lumped RC: } t_p = 0.69 RC$$

$$\text{Distributed RC: } t_p = 0.38 RC$$

RC-chain:

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Transmission line reflection:

$$\rho = \frac{V_{refl}}{V_{inc}} = \frac{I_{refl}}{I_{inc}} = \frac{R - Z_0}{R + Z_0}$$

**DIGITAL  
INTEGRATED  
CIRCUITS**

---

A DESIGN PERSPECTIVE

**Prentice Hall Electronics and VLSI Series**

Charles S. Sodini, Series Editor

LEE, SHUR, FIELDLY, YTTERDAL *Semiconductor Devices Modeling for VLSI*

LEUNG *VLSI for Wireless Communications*

PLUMMER, DEAL, GRIFFIN *Silicon VLSI Technology: Fundamentals, Practice, and Modeling*

RABAEY, CHANDRAKASAN, NIKOLIĆ *Digital Integrated Circuits: A Design Perspective, Second Edition*

# **DIGITAL INTEGRATED CIRCUITS**

---

**A DESIGN PERSPECTIVE  
SECOND EDITION**

**JAN M. RABAEY  
ANANTHA CHANDRAKASAN  
BORIVOJE NIKOLIĆ**

PRENTICE HALL ELECTRONICS AND VLSI SERIES  
CHARLES G. SODINI, SERIES EDITOR



Pearson Education, Inc.  
Upper Saddle River, New Jersey 07458

Library of Congress Cataloging-in-Publication Data on file.

Vice President and Editorial Director, ECS: *Marcia J. Horton*  
Publisher: *Tom Robbins*  
Editorial Assistant: *Eric Van Ostenbridge*  
Vice President and Director of Production and Manufacturing, ESM: *David W. Riccardi*  
Executive Managing Editor: *Vince O'Brien*  
Managing Editor: *David A. George*  
Production Editor: *Daniel Sandin*  
Director of Creative Services: *Paul Belfanti*  
Creative Director: *Carole Anson*  
Art and Cover Director: *Jayne Conte*  
Art Editor: *Greg Dulles*  
Manufacturing Manager: *Trudy Piscioti*  
Manufacturing Buyer: *Lisa McDowell*  
Marketing Manager: *Holly Stark*

*About the Cover:* Detail of "Wet Orange," by Joan Mitchell (American, 1925–1992). Oil on canvas, 112 × 245 in. (284.5 × 622.3 cm). Carnegie Museum of Art, Pittsburgh, PA. Gift of Kaufmann's Department Store and the National Endowment for the Arts, 74.11. Photograph by Peter Harholdt, 1995.



© 2003, 1996 by Pearson Education, Inc.  
Pearson Education, Inc.  
Upper Saddle River, NJ 07458

The author and publisher of this book have used their best efforts in preparing this book. These efforts include the development, research, and testing of the theories and programs to determine their effectiveness. The author and publisher shall not be liable in any event for incidental and consequential damages in connection with, or arising out of, the furnishing, performance, or use of these programs.

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN 0-13-597444-5

Pearson Education Ltd., *London*  
Pearson Education Australia Pty, Ltd., *Sydney*  
Pearson Education Singapore, Pte. Ltd.  
Pearson Education North Asia Ltd., *Hong Kong*  
Pearson Education Canada Inc., *Toronto*  
Pearson Educación de México, S.A. de C.V.  
Pearson Education—Japan, *Tokyo*  
Pearson Education Malaysia, Pte. Ltd.  
Pearson Education Inc., *Upper Saddle River, New Jersey*



*To Kathelijn, Karthiyayani, Krithivasan,  
and our Parents*

*“Qu’est-ce que l’homme dans la nature?  
Un néant a l’égard de l’infini,  
un tout al l’égard du néant,  
un milieu entre rien et tout.”*

*“What is man in nature?  
Nothing in relation to the infinite,  
everything in relation to nothing,  
a mean between nothing and everything.”*

Blaise Pascal, *Pensées*, n. 4, 1670.

# Preface

## What is New?

Welcome to second edition of “*Digital Integrated Circuits: A Design Perspective.*” In the six years since the publication of the first, the field of digital integrated circuits has gone through some dramatic evolutions and changes. IC manufacturing technology has continued to scale to ever-smaller dimensions. Minimum feature sizes have scaled by a factor of almost ten since the writing of the first edition, and now are approaching the 100 nm realm. This scaling has a double impact on the design of digital integrated circuit. First of all, the complexity of the designs that can be put on a single die has increased dramatically. Dealing with the challenges this poses has led to new design methodologies and implementation strategies. At the same time, the plunge into the deep-submicron space causes devices to behave differently, and brings to the forefront a number of new issues that impact the reliability, cost, performance, and power dissipation of the digital IC. Addressing these issues in-depth is what differentiates this edition from the first.

A glance through the table of contents reveals extended coverage of issues such as deep-sub micron devices, circuit optimization, interconnect modeling and optimization, signal integrity, clocking and timing, and power dissipation. All these topics are illustrated with state-of-the-art design examples. Also, since MOS now represents more than 99% of the digital IC market, older technologies such as silicon bipolar and GaAs have been deleted (however, the interested reader can find the old chapters on these technologies on the web site of the book). Given the importance of methodology in today’s design process, we have included *Design Methodology Inserts* throughout the text, each of which highlights one particular aspect of the design process. This new edition represents a major reworking of the book. The biggest change is the addition of two co-authors, Anantha and Bora, who have brought a broader insight into digital IC design and its latest trends and challenges.

## Maintaining the Spirit of the First Edition

While introducing these changes, our intent has been to preserve the spirit and goals of the first edition—that is, to bridge the gap between the **circuit and system visions** on digital design. While starting from a solid understanding of the operation of electronic devices and an in-depth analysis of the nucleus of digital design—the inverter—we gradually channel this knowledge into the design of more complex modules such as gates, registers, controllers, adders, multipliers, and memories. We identify the compelling questions facing the designers of today’s

complex circuits: What are the dominant design parameters, what section of the design should he focus on and what details could she ignore? Simplification is clearly the only approach to address the increasing complexity of the digital systems. However, oversimplification can lead to circuit failure since global circuit effects such as timing, interconnect, and power consumption are ignored. To avoid this pitfall it is important to design digital circuits with both a circuits and a systems perspective in mind. This is the approach taken in this book, which brings the reader the knowledge and expertise needed to deal with complexity, using both analytical and experimental techniques.

### How to Use This Book

The core of the text is intended for use in a *senior-level digital circuit design class*. Around this kernel, we have included chapters and sections covering the more advanced topics. In the course of developing this book, it quickly became obvious that it is difficult to define a subset of the digital circuit design domain that covers everyone's needs. On the one hand, a newcomer to the field needs detailed coverage of the basic concepts. On the other hand, feedback from early readers and reviewers indicated that an in-depth and extensive coverage of advanced topics and current issues is desirable and necessary. Providing this complete vision resulted in a text that exceeds the scope of a single-semester class. The more advanced material can be used as the basis for a *graduate class*. The wide coverage and the inclusion of state-of-the-art topics also makes the text useful as a reference work for professional engineers. It is assumed that students taking this course are familiar with the basics of logic design.

The organization of the material is such that the chapters can be taught or read in many ways, as long as a number of precedence relations are adhered to. The core of the text consists of Chapters 5, 6, 7, and 8. Chapters 1 to 4 can be considered as introductory. In response to popular demand, we have introduced a short treatise on semiconductor manufacturing in Chapter 2. Students with a prior introduction to semiconductor devices can traverse quickly through Chapter 3. We urge everyone to do at least that, as a number of important notations and foundations are introduced in that chapter. In addition, an original approach to the modeling of deep-submicron transistors enabling manual analysis, is introduced. To emphasize the importance of interconnect in today's digital design, we have moved the modeling of interconnect forward in the text to Chapter 4.

Chapters 9 to 12 are of a more advanced nature and can be used to provide a certain focus to the course. A course with a focus on the circuit aspects, for example, can supplement the core material with Chapters 9 and 12. A course focused on the digital system design should consider adding (parts of) Chapters 9, 10, and 11. All of these advanced chapters can be used to form the core of a graduate or a follow-on course. Sections considered *advanced* are marked with an *asterisk* in the text.

A number of possible paths through the material for a senior-level class are enumerated below. In the *instructor documentation*, provided on the book's web site, we have included a number of complete syllabi based on courses run at some academic institutions.

*Basic circuit class (with minor prior device knowledge):*

1, 2.1–3, 3, 4, 5, 6, 7, 8, (9.1–9.3, 12).

*Somewhat more advanced circuit coverage:*

1, (2, 3), 4, 5, 6, 7, 8, 9, 10.1–10.3, 10.5–10.6, 12.

*Course with systems focus:*

1, (2, 3), 4, 5, 6, 7, 8, 9, 10.1–10.4, 11, 12.1–12.2.

The *design methodology inserts* are, by preference, covered in concurrence with the chapter to which they are attached.

In order to maintain a consistent flow through each of the chapters, the topics are *introduced* first, followed by a detailed and in-depth discussion of the ideas. A *Perspective* section discusses how the introduced concepts relate to real world designs and how they might be impacted by future evolutions. Each chapter finishes with a *Summary*, which briefly enumerates the topics covered in the text, followed by *To Probe Further* and *Reference* sections. These provide ample references and pointers for a reader interested in further details on some of the material.

As the title of the book implies, one of the goals of this book is to stress the design aspect of digital circuits. To achieve this more practical viewpoint and to provide a real perspective, we have interspersed actual *design examples* and layouts throughout the text. These case studies help to answer questions, such as “How much area or speed or power is really saved by applying this technique?” To mimic the real design process, we are making extensive use of design tools such as circuit- and switch-level simulation as well as layout editing and extraction. Computer analysis is used throughout to verify manual results, to illustrate new concepts, or to examine complex behavior beyond the reach of manual analysis.

Finally, to facilitate the learning process, there are numerous examples included in the text. Each chapter contains a number of *problems or brain-teasers* (answers for which can be found in the back of the book), that provoke thinking and understanding while reading.

## The Worldwide Web Companion

A worldwide web companion (<http://bwrc.eecs.berkeley.edu/IcBook/index.htm>) provides fully worked-out design problems and a complete set of overhead transparencies, extracting the most important figures and graphs from the text.

In contrast to the first edition, we have chosen **NOT to include problems sets and design problems** in the text. Instead we decided to make them available **on the book’s web site**. This gives us the opportunity to dynamically upgrade and extend the problems, providing a more effective tool for the instructor. More than 300 challenging *exercises* are currently provided. The goal is to provide the individual reader an independent gauge for his understanding of the material and to provide practice in the use of some of the design tools. Each problem is keyed to the text sections it refers to (e.g., <1.3>), the design tools that must be used when solving the problem (e.g., SPICE) and a rating, ranking the problems on difficulty: (E) easy, (M) moderate, and

(C) challenging. Problems marked with a (D) include a design or research elements. Solutions to the problem sets are available only to instructors of academic institutions that have chosen to adopt our book for classroom use. They are available through the publisher on a password-protected web site.

Open-ended *design problems* help to gain the all-important insight into design optimization and trade-off. The use of design editing, verification and analysis tools is recommended when attempting these design problems. Fully worked out versions of these problems can be found on the web site.

In addition, the book's web site also offers samples of hardware and software laboratories, extra background information, and useful links.

### Compelling Features of the Book

- Brings both circuit and systems views on design together. It offers a profound understanding of the design of complex digital circuits, while preparing the designer for new challenges that might be waiting around the corner.
- Design-oriented perspectives are advocated throughout. Design challenges and guidelines are highlighted. Techniques introduced in the text are illustrated with real designs and complete SPICE analysis.
- Is the first circuit design book that *focuses solely on deep-submicron devices*. To facilitate this, a simple transistor model for manual analysis, called the *unified MOS model*, has been developed.
- Unique in showing how to use the latest techniques to design complex high-performance or low-power circuits. Speed and power treated as equal citizens throughout the text.
- Covers crucial real-world system design issues such as signal integrity, power dissipation, interconnect, packaging, timing, and synchronization.
- Provides unique coverage of the latest design methodologies and tools, with a discussion of how to use them from a designers' perspective.
- Offers perspectives on how digital circuit technology might evolve in the future.
- Outstanding illustrations and a usable design-oriented four-color insert.
- To Probe Further and Reference sections provide ample references and pointers for a reader interested in further details on some of the material.
- Extensive instructional package is available over the internet from the author's web site. Includes design software, transparency masters, problem sets, design problems, actual layouts, and hardware and software laboratories.

### The Contents at a Glance

A quick scan of the table of contents shows how the ordering of chapters and the material covered are consistent with the advocated design methodology. Starting from a model of the semiconductor devices, we will gradually progress upwards, covering the inverter, the complex logic gate (NAND, NOR, XOR), the functional (adder, multiplier, shifter, register) and the system

module (datapath, controller, memory) levels of abstraction. For each of these layers, the dominant design parameters are identified and simplified models are constructed, abstracting away the nonessential details. While this layered modeling approach is the designer's best handle on complexity, it has some pitfalls. This is illustrated in Chapters 9 and 10, where topics with a global impact, such as interconnect parasitics and chip timing, are discussed. To further express the dichotomy between circuit and system design visions, we have divided the book contents into two major parts: Part II (Chapters 4–7) addresses mostly the circuit perspective of digital circuit design, while Part III (Chapters 8–12) presents a more system oriented vision. Part I (Chapters 1–4) provides the necessary foundation (design metrics, the manufacturing process, device and interconnect models).

**Chapter 1** serves as a global *introduction*. After a historical overview of digital circuit design, the concepts of hierarchical design and the different abstraction layers are introduced. A number of fundamental metrics, which help to quantify cost, reliability, and performance of a design, are introduced.

**Chapter 2** provides a short and compact introduction to the *MOS manufacturing process*. Understanding the basic steps in the process helps to create the three-dimensional understanding of the MOS transistor, which is crucial when identifying the sources of the device parasitics. Many of the variations in device parameters can also be attributed to the manufacturing process as well. The chapter further introduces the concept of design rules, which form the interface between the designer and the manufacturer. The chapter concludes with an overview of the chip packaging process, an often-overlooked but crucial element of the digital IC design cycle.

**Chapter 3** contains a summary of the primary design building blocks, *the semiconductor devices*. The main goal of this chapter is to provide an intuitive understanding of the operation of the MOS as well as to introduce the device models, which are used extensively in the later chapters. Major attention is paid to the artifacts of modern submicron devices, and the modeling thereof. Readers with prior device knowledge can traverse this material rather quickly.

**Chapter 4** contains a careful analysis of the *wire*, with interconnect and its accompanying parasitics playing a major role. We visit each of the parasitics that come with a wire (capacitance, resistance, and inductance) in turn. Models for both manual and computer analysis are introduced.

**Chapter 5** deals with the nucleus of digital design, the *inverter*. First, a number of fundamental properties of digital gates are introduced. These parameters, which help to quantify the performance and reliability of a gate, are derived in detail for two representative inverter structures: the static complementary CMOS. The techniques and approaches introduced in this chapter are of crucial importance, as they are repeated over and over again in the analysis of other gate structures and more complex gate structures.

In **Chapter 6** this fundamental knowledge is extended to address the design of *simple and complex digital CMOS gates*, such as NOR and NAND structures. It is demonstrated that, depending upon the dominant design constraint (reliability, area, performance, or power), other

CMOS gate structures besides the complementary static gate can be attractive. The properties of a number of contemporary gate-logic families are analyzed and compared. Techniques to optimize the performance and power consumption of complex gates are introduced.

**Chapter 7** discusses how memory function can be accomplished using either positive feedback or charge storage. Besides analyzing the traditional bistable flip-flops, other sequential circuits such as the mono- and astable multivibrators are also introduced. All chapters prior to Chapter 7 deal exclusively with combinational circuits, that is circuits without a sense of the past history of the system. *Sequential logic circuits*, in contrast, can remember and store the past state.

All chapters preceding **Chapter 8** present a circuit-oriented approach towards digital design. The analysis and optimization process has been constrained to the individual gate. In this chapter, we take our approach one step further and analyze how gates can be connected together to form the building blocks of a system. The system-level part of the book starts, appropriately, with a discussion of *design methodologies*. Design automation is the only way to cope with the ever-increasing complexity of digital designs. In Chapter 8, the prominent ways of producing large designs in a limited time are discussed. The chapter spends considerable time on the different implementation methodologies available to today's designer. Custom versus semi-custom, hardwired versus fixed, regular array versus ad-hoc are some of the issues put forward.

**Chapter 9** revisits the impact of *interconnect wiring* on the functionality and performance of a digital gate. A wire introduces parasitic capacitive, resistive, and inductive effects, which are becoming ever more important with the scaling of the technology. Approaches to minimize the impact of these interconnect parasitics on performance, power dissipation and circuit reliability are introduced. The chapter also addresses some important issues such as supply-voltage distribution, and input/output circuitry.

In **Chapter 10** details how that in order to operate sequential circuits correctly, a strict ordering of the switching events has to be imposed. Without these *timing* constraints, wrong data might be written into the memory cells. Most digital circuits use a synchronous, clocked approach to impose this ordering. In Chapter 10, the different approaches to digital circuit timing and clocking are discussed. The impact of important effects such as clock skew on the behavior of digital synchronous circuits is analyzed. The synchronous approach is contrasted with alternative techniques, such as self-timed circuits. The chapter concludes with a short introduction to synchronization and clock-generation circuits.

In **Chapter 11**, the design of a variety of complex *arithmetic building blocks* such as adders, multipliers, and shifters, is discussed. This chapter is crucial because it demonstrates how the design techniques introduced in chapters 5 and 6 are extended to the next abstraction layer. The concept of the critical path is introduced and used extensively in the performance analysis and optimization. Higher-level performance models are derived. These help the designer to get a fundamental insight into the operation and quality of a design module, without having to resort to an in-depth and detailed analysis of the underlying circuitry.

**Chapter 12** discusses in depth the different memory classes and their implementation. Whenever large amounts of data storage are needed, the digital designer resorts to special circuit modules, called *memories*. Semiconductor memories achieve very high storage density by compromising on some of the fundamental properties of digital gates. Instrumental in the design of reliable and fast memories is the implementation of the peripheral circuitry, such as the decoders, sense amplifiers, drivers, and control circuitry, which are extensively covered. Finally, as the primary issue in memory design is to ensure that the device works consistently under all operating circumstances, the chapter concludes with a detailed discussion of memory reliability. This chapter as well as the previous one are optional for undergraduate courses.

### Acknowledgments

The authors would like to thank all those who contributed to the emergence, creation and correction of this manuscript. First of all, thanks to all the graduate students that helped over the years to bring the text to where it is today. Thanks also to the students of the eecs141 and eecs241 courses at Berkeley and the 6.374 course at MIT, who suffered through many of the experimental class offerings based on this book. The feedback from instructors, engineers, and students from all over the world has helped tremendously in focusing the directions of this new edition, and in fine-tuning the final text. The continuous stream of e-mails indicate to us that we are on the right track.

In particular, we would like to acknowledge the contributions of Mary-Jane Irwin, Vijay Narayanan, Eby Friedman, Fred Rosenberger, Wayne Burleson, Sekhar Borkar, Ivo Bolsens, Duane Boning, Olivier Franza, Lionel Kimerling, Josie Ammer, Mike Sheets, Tufan Karalar, Huifang Qin, Rhett Davis, Nathan Chan, Jeb Durant, Andrei Vladimirescu, Radu Zlatanovici, Yasuhisa Shimazaki, Fujio Ishihara, Dejan Markovic, Vladimir Stojanovic, SeongHwan Cho, James Kao, Travis Simpkins, Siva Narendra, James Goodman, Vadim Gutnik, Theodoros Konstantakopoulos, Rex Min, Vikas Mehrotra, and Paul-Peter Sotiriadis. Their help, input, and feedback are greatly appreciated. Obviously, we remain thankful to those who helped create and develop the first edition.

I am extremely grateful to the staff at Prentice Hall, who have been instrumental in turning a rough manuscript into an enjoyable book. First of all, I would like to acknowledge the help and constructive feedback of Tom Robbins, Publisher, Daniel Sandin, Production Editor, and David George, Managing Editor. A special word of thanks to Brenda Vanoni at Berkeley, for her invaluable help in the copy editing and the website creation process. The web expertise of Carol Sitea came in very handy as well.

I would like to highlight to role of computer aids in developing this manuscript. All drafts were completely developed on the FrameMaker publishing system (Adobe Systems). Graphs were mostly created using MATLAB. Microsoft Frontpage is the tool of choice for the web-page creation. For circuit simulations, we used HSPICE (Avant!). All layouts were generated using the Cadence physical design suite.



Finally, some words of gratitude to the people that had to endure the creation process of this book, Kathelijn, Karthiyayani, Krithivasan, and Rebecca. While the generation of a new edition brings substantially less pain than a first edition, we consistently underestimate what it takes, especially in light of the rest of our daily loads. They been a constant support, help and encouragement during the writing of this manuscript.

JAN M. RABAEY  
ANANTHA CHANDRAKASAN  
BORIVOJE NIKOLIĆ  
*Berkeley, Calistoga, Cambridge*

# Contents

<b>Preface</b>	<b>vii</b>
<hr/> <b>Part 1 The Fabrics</b>	<hr/> <b>1</b>
<b>Chapter 1 Introduction</b>	<b>3</b>
1.1 A Historical Perspective	4
1.2 Issues in Digital Integrated Circuit Design	6
1.3 Quality Metrics of a Digital Design	15
1.3.1 Cost of an Integrated Circuit	16
1.3.2 Functionality and Robustness	18
1.3.3 Performance	27
1.3.4 Power and Energy Consumption	30
1.4 Summary	31
1.5 To Probe Further	31
Reference Books	32
References	33
<b>Chapter 2 The Manufacturing Process</b>	<b>35</b>
2.1 Introduction	36
2.2 Manufacturing CMOS Integrated Circuits	36
2.2.1 The Silicon Wafer	37
2.2.2 Photolithography	37
2.2.3 Some Recurring Process Steps	41
2.2.4 Simplified CMOS Process Flow	42
2.3 Design Rules—The Contract between Designer and Process Engineer	47
2.4 Packaging Integrated Circuits	51
2.4.1 Package Materials	52
2.4.2 Interconnect Levels	53
2.4.3 Thermal Considerations in Packaging	59
2.5 Perspective—Trends in Process Technology	61
2.5.1 Short-Term Developments	61
2.5.2 In the Longer Term	63
2.6 Summary	64

2.7	To Probe Further	64
	References	64
<b><i>Design Methodology Insert A IC LAYOUT</i></b>		<b>67</b>
A.1	To Probe Further	71
	References	71
<b><i>Chapter 3 The Devices</i></b>		<b>73</b>
3.1	Introduction	74
3.2	The Diode	74
3.2.1	A First Glance at the Diode—The Depletion Region	75
3.2.2	Static Behavior	77
3.2.3	Dynamic, or Transient, Behavior	80
3.2.4	The Actual Diode—Secondary Effects	84
3.2.5	The SPICE Diode Model	85
3.3	The MOS(FET) Transistor	87
3.3.1	A First Glance at the Device	87
3.3.2	The MOS Transistor under Static Conditions	88
3.3.3	The Actual MOS Transistor—Some Secondary Effects	114
3.3.4	SPICE Models for the MOS Transistor	117
3.4	A Word on Process Variations	120
3.5	Perspective—Technology Scaling	122
3.6	Summary	128
3.7	To Probe Further	129
	References	130
<b><i>Design Methodology Insert B Circuit Simulation</i></b>		<b>131</b>
	References	134
<b><i>Chapter 4 The Wire</i></b>		<b>135</b>
4.1	Introduction	136
4.2	A First Glance	136
4.3	Interconnect Parameters—Capacitance, Resistance, and Inductance	138
4.3.1	Capacitance	138
4.3.2	Resistance	144
4.3.3	Inductance	148
4.4	Electrical Wire Models	150
4.4.1	The Ideal Wire	151
4.4.2	The Lumped Model	151
4.4.3	The Lumped $RC$ Model	152
4.4.4	The Distributed $rc$ Line	156
4.4.5	The Transmission Line	159

<b>Contents</b>		<b>xvii</b>
4.5	SPICE Wire Models	170
4.5.1	Distributed $rc$ Lines in SPICE	170
4.5.2	Transmission Line Models in SPICE	170
4.5.3	Perspective: A Look into the Future	171
4.6	Summary	174
4.7	To Probe Further	174
	References	174
<hr/>		
<b>Part 2</b>	<b>A Circuit Perspective</b>	<b>177</b>
<hr/>		
<b>Chapter 5</b>	<b>The CMOS Inverter</b>	<b>179</b>
5.1	Introduction	180
5.2	The Static CMOS Inverter—An Intuitive Perspective	180
5.3	Evaluating the Robustness of the CMOS Inverter: The Static Behavior	184
5.3.1	Switching Threshold	185
5.3.2	Noise Margins	188
5.3.3	Robustness Revisited	191
5.4	Performance of CMOS Inverter: The Dynamic Behavior	193
5.4.1	Computing the Capacitances	194
5.4.2	Propagation Delay: First-Order Analysis	199
5.4.3	Propagation Delay from a Design Perspective	203
5.5	Power, Energy, and Energy Delay	213
5.5.1	Dynamic Power Consumption	214
5.5.2	Static Consumption	223
5.5.3	Putting It All Together	225
5.5.4	Analyzing Power Consumption Using SPICE	227
5.6	Perspective: Technology Scaling and its Impact on the Inverter Metrics	229
5.7	Summary	232
5.8	To Probe Further	233
	References	233
<b>Chapter 6</b>	<b>Designing Combinational Logic Gates in CMOS</b>	<b>235</b>
6.1	Introduction	236
6.2	Static CMOS Design	236
6.2.1	Complementary CMOS	237
6.2.2	Ratioed Logic	263
6.2.3	Pass-Transistor Logic	269
6.3	Dynamic CMOS Design	284
6.3.1	Dynamic Logic: Basic Principles	284
6.3.2	Speed and Power Dissipation of Dynamic Logic	287

6.3.3	Signal Integrity Issues in Dynamic Design	290
6.3.4	Cascading Dynamic Gates	295
6.4	Perspectives	303
6.4.1	How to Choose a Logic Style?	303
6.4.2	Designing Logic for Reduced Supply Voltages	303
6.5	Summary	306
6.6	To Probe Further	307
	References	308
<b><i>Design Methodology Insert C How to Simulate Complex Logic Circuits</i></b>		<b>309</b>
C.1	Representing Digital Data as a Continuous Entity	310
C.2	Representing Data as a Discrete Entity	310
C.3	Using Higher-Level Data Models	315
	References	317
<b><i>Design Methodology Insert D Layout Techniques for Complex Gates</i></b>		<b>319</b>
<b>Chapter 7</b>	<b>Designing Sequential Logic Circuits</b>	<b>325</b>
7.1	Introduction	326
7.1.1	Timing Metrics for Sequential Circuits	327
7.1.2	Classification of Memory Elements	328
7.2	Static Latches and Registers	330
7.2.1	The Bistability Principle	330
7.2.2	Multiplexer-Based Latches	332
7.2.3	Master-Slave Edge-Triggered Register	333
7.2.4	Low-Voltage Static Latches	339
7.2.5	Static SR Flip-Flops—Writing Data by Pure Force	341
7.3	Dynamic Latches and Registers	344
7.3.1	Dynamic Transmission-Gate Edge-triggered Registers	344
7.3.2	C <sup>2</sup> MOS—A Clock-Skew Insensitive Approach	346
7.3.3	True Single-Phase Clocked Register (TSPCR)	350
7.4	Alternative Register Styles*	354
7.4.1	Pulse Registers	354
7.4.2	Sense-Amplifier-Based Registers	356
7.5	Pipelining: An Approach to Optimize Sequential Circuits	358
7.5.1	Latch- versus Register-Based Pipelines	360
7.5.2	NORA-CMOS—A Logic Style for Pipelined Structures	361
7.6	Nonbistable Sequential Circuits	364
7.6.1	The Schmitt Trigger	364
7.6.2	Monostable Sequential Circuits	367
7.6.3	Astable Circuits	368
7.7	Perspective: Choosing a Clocking Strategy	370
7.8	Summary	371



















<b>Contents</b>		<b>xix</b>
7.9	To Probe Further	372
	References	372
<hr/> <b>Part 3 A System Perspective</b>		<b>375</b>
<hr/> <b>Chapter 8 Implementation Strategies for Digital ICS</b>		<b>377</b>
8.1	Introduction	378
8.2	From Custom to Semicustom and Structured-Array Design Approaches	382
8.3	Custom Circuit Design	383
8.4	Cell-Based Design Methodology	384
	8.4.1 Standard Cell	385
	8.4.2 Compiled Cells	390
	8.4.3 Macrocells, Megacells and Intellectual Property	392
	8.4.4 Semicustom Design Flow	396
8.5	Array-Based Implementation Approaches	399
	8.5.1 Prediffused (or Mask-Programmable) Arrays	399
	8.5.2 Prewired Arrays	404
8.6	Perspective—The Implementation Platform of the Future	420
8.7	Summary	423
8.8	To Probe Further	423
	References	424
<b>Design Methodology Insert E Characterizing Logic and Sequential Cells</b>		<b>427</b>
	References	434
<b>Design Methodology Insert F Design Synthesis</b>		<b>435</b>
	References	443
<b>Chapter 9 Coping with Interconnect</b>		<b>445</b>
9.1	Introduction	446
9.2	Capacitive Parasitics	446
	9.2.1 Capacitance and Reliability—Cross Talk	446
	9.2.2 Capacitance and Performance in CMOS	449
9.3	Resistive Parasitics	460
	9.3.1 Resistance and Reliability—Ohmic Voltage Drop	460
	9.3.2 Electromigration	462
	9.3.3 Resistance and Performance— <i>RC</i> Delay	464
9.4	Inductive Parasitics*	469
	9.4.1 Inductance and Reliability— Voltage Drop	469
	9.4.2 Inductance and Performance—Transmission-line Effects	475
9.5	Advanced Interconnect Techniques	480

9.5.1	Reduced-Swing Circuits	480
9.5.2	Current-Mode Transmission Techniques	486
9.6	Perspective: Networks-on-a-Chip	487
9.7	Summary	488
9.8	To Probe Further	489
	References	489
<b>Chapter 10</b>	<b>Timing Issues in Digital Circuits</b>	<b>491</b>
10.1	Introduction	492
10.2	Timing Classification of Digital Systems	492
	10.2.1 Synchronous Interconnect	492
	10.2.2 Mesochronous interconnect	493
	10.2.3 Plesiochronous Interconnect	493
	10.2.4 Asynchronous Interconnect	494
10.3	Synchronous Design—An In-depth Perspective	495
	10.3.1 Synchronous Timing Basics	495
	10.3.2 Sources of Skew and Jitter	502
	10.3.3 Clock-Distribution Techniques	508
	10.3.4 Latch-Based Clocking*	516
10.4	Self-Timed Circuit Design*	519
	10.4.1 Self-Timed Logic—An Asynchronous Technique	519
	10.4.2 Completion-Signal Generation	522
	10.4.3 Self-Timed Signaling	526
	10.4.4 Practical Examples of Self-Timed Logic	531
10.5	Synchronizers and Arbiters*	534
	10.5.1 Synchronizers—Concept and Implementation	534
	10.5.2 Arbiters	538
10.6	Clock Synthesis and Synchronization Using a Phase-Locked Loop*	539
	10.6.1 Basic Concept	540
	10.6.2 Building Blocks of a PLL	542
10.7	Future Directions and Perspectives	546
	10.7.1 Distributed Clocking Using DLLs	546
	10.7.2 Optical Clock Distribution	548
	10.7.3 Synchronous versus Asynchronous Design	549
10.8	Summary	550
10.9	To Probe Further	551
	References	551
<b>Design Methodology Insert G</b>	<b>Design Verification</b>	<b>553</b>
	References	557


<b>Chapter 11</b>	<b>Designing Arithmetic Building Blocks</b>	<b>559</b>
11.1	Introduction	560
11.2	Datapaths in Digital Processor Architectures	560
11.3	The Adder	561
11.3.1	The Binary Adder: Definitions	561
11.3.2	The Full Adder: Circuit Design Considerations	564
11.3.3	The Binary Adder: Logic Design Considerations	571
11.4	The Multiplier	586
11.4.1	The Multiplier: Definitions	586
11.4.2	Partial-Product Generation	587
11.4.3	Partial-Product Accumulation	589
11.4.4	Final Addition	593
11.4.5	Multiplier Summary	594
11.5	The Shifter	594
11.5.1	Barrel Shifter	595
11.5.2	Logarithmic Shifter	596
11.6	Other Arithmetic Operators	596
11.7	Power and Speed Trade-offs in Datapath Structures*	600
11.7.1	Design Time Power-Reduction Techniques	601
11.7.2	Run-Time Power Management	611
11.7.3	Reducing the Power in Standby (or Sleep) Mode	617
11.8	Perspective: Design as a Trade-off	618
11.9	Summary	619
11.10	To Probe Further	620
	References	621
<b>Chapter 12</b>	<b>Designing Memory and Array Structures</b>	<b>623</b>
12.1	Introduction	624
12.1.1	Memory Classification	625
12.1.2	Memory Architectures and Building Blocks	627
12.2	The Memory Core	634
12.2.1	Read-Only Memories	634
12.2.2	Nonvolatile Read-Write Memories	647
12.2.3	Read-Write Memories (RAM)	657
12.2.4	Contents-Addressable or Associative Memory (CAM)	670
12.3	Memory Peripheral Circuitry*	672
12.3.1	The Address Decoders	672
12.3.2	Sense Amplifiers	679
12.3.3	Voltage References	686
12.3.4	Drivers/Buffers	689
12.3.5	Timing and Control	689




12.4	Memory Reliability and Yield*	693
12.4.1	Signal-to-Noise Ratio	693
12.4.2	Memory Yield	698
12.5	Power Dissipation in Memories*	701
12.5.1	Sources of Power Dissipation in Memories	701
12.5.2	Partitioning of the Memory	702
12.5.3	Addressing the Active Power Dissipation	702
12.5.4	Data-Retention Dissipation	704
12.5.5	Summary	707
12.6	Case Studies in Memory Design	707
12.6.1	The Programmable Logic Array (PLA)	707
12.6.2	A 4-Mbit SRAM	710
12.6.3	A 1-Gbit NAND Flash Memory	712
12.7	Perspective: Semiconductor Memory Trends and Evolutions	714
12.8	Summary	716
12.9	To Probe Further	717
	References	718
<b><i>Design Methodology Insert H Validation and Test</i></b>		
<b>of Manufactured Circuits</b>		<b>721</b>
H.1	Introduction	721
H.2	Test Procedure	722
H.3	Design for Testability	723
H.3.1	Issues in Design for Testability	723
H.3.2	Ad Hoc Testing	725
H.3.3	Scan-Based Test	726
H.3.4	Boundary-Scan Design	729
H.3.5	Built-in Self-Test (BIST)	730
H.4	Test-Pattern Generation	734
H.4.1	Fault Models	734
H.4.2	Automatic Test-Pattern Generation (ATPG)	736
H.4.3	Fault Simulation	737
H.5	To Probe Further	737
	References	737
<b>Problem Solutions</b>		<b>739</b>
<b>Index</b>		<b>745</b>

Layer Description	Representation				
metal					
	m1	m2	m3	m4	m5
well					
	nw				
polysilicon					
	poly				
contacts & vias					
	ct	v12,v23,v34,v45	nwc	pwc	
active area and FETs					
	ndif	pdif	nfet	pfet	
select					
	nplus	pplus	prb		


**Colorplate 1.** CMOS layers and representations (for vanilla 0.25  $\mu\text{m}$  CMOS process)

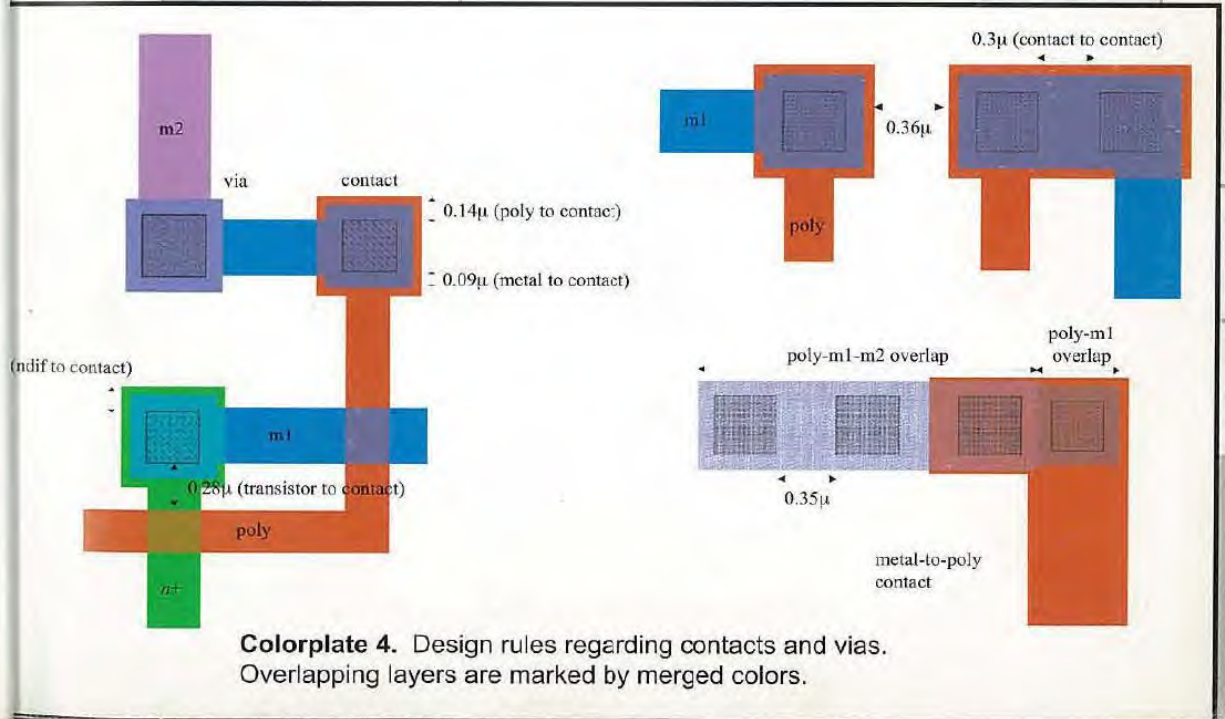


**Colorplate 4.** Design rules regarding contacts and vias. Overlapping layers are marked by merged colors.

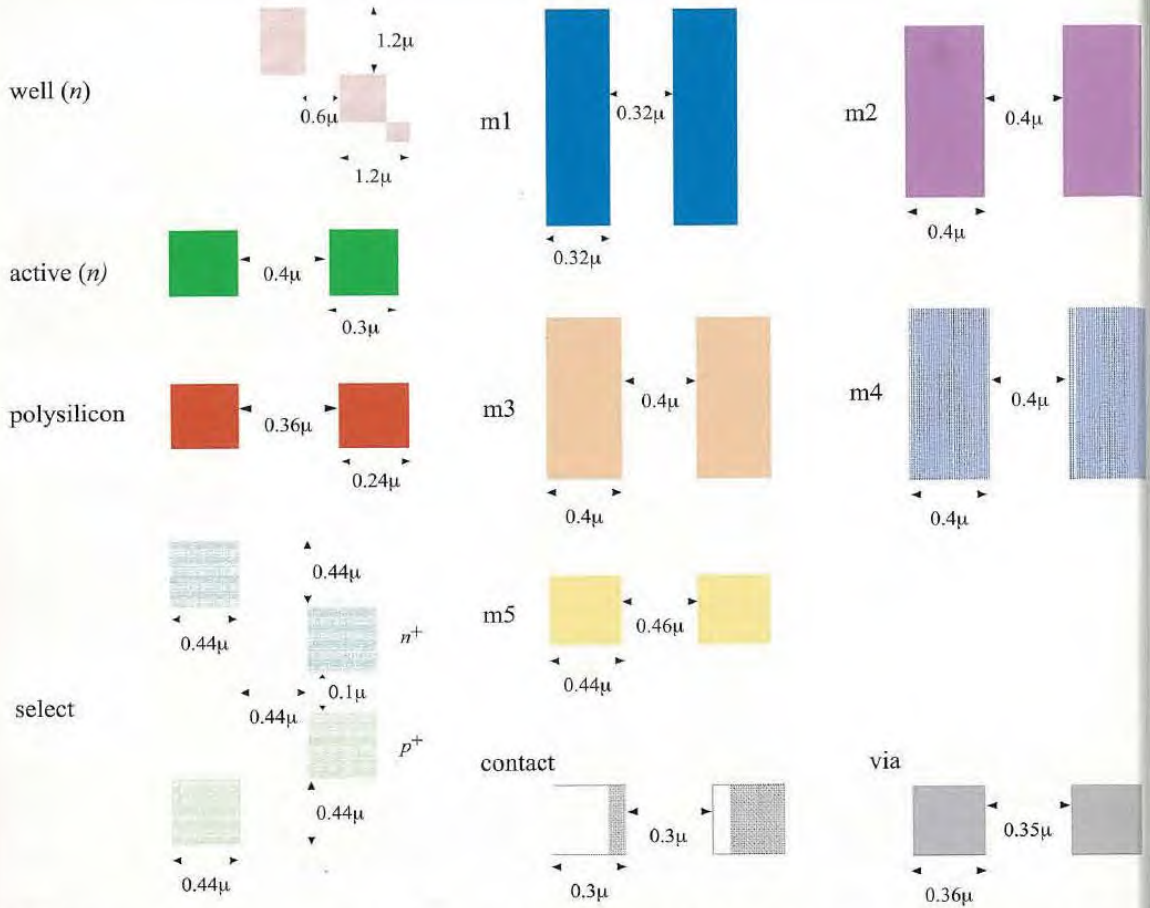


**Colorplate 2.** Intra-layer layout design rules, expressed as minimum dimensions and spacings.

 




**Colorplate 3.** Design rules concerning transistor layout. The device shown is a PMOS transistor.

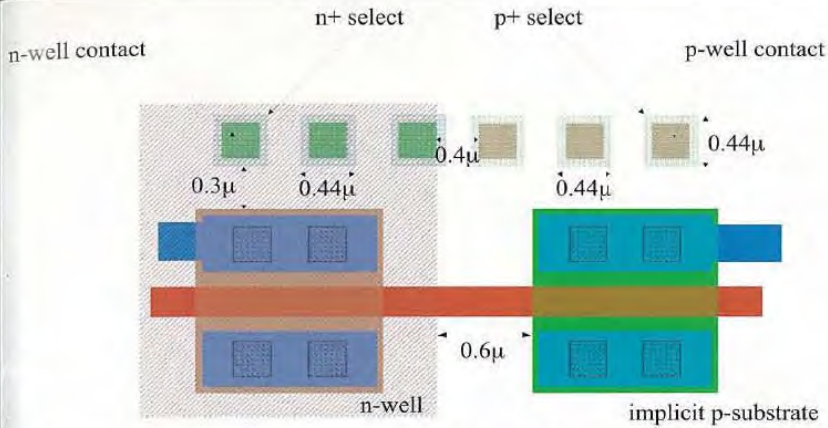

**Colorplate 5.** Design rules regarding well contacts and select layers.

 

   **Colorplate 6.** Layout of inverter in 0.25  $\mu$ m CMOS technology.



## CHAPTER

# 2

# The Manufacturing Process

*Overview of manufacturing process*

*Design rules*

*IC packaging*

*Future Trends in Integrated Circuit Technology*

- 2.1 Introduction
- 2.2 Manufacturing CMOS Integrated Circuits
  - 2.2.1 The Silicon Wafer
  - 2.2.2 Photolithography
  - 2.2.3 Some Recurring Process Steps
  - 2.2.4 Simplified CMOS Process Flow
- 2.3 Design Rules—Between the Designer and the Process Engineer
- 2.4 Packaging Integrated Circuits
  - 2.4.1 Package Materials
  - 2.4.2 Interconnect Levels
  - 2.4.3 Thermal Considerations in Packaging
- 2.5 Perspective—Trends in Process Technology
  - 2.5.1 Short-Term Developments
  - 2.5.2 In the Longer Term
- 2.6 Summary
- 2.7 To Probe Further

## 2.1 Introduction

Most digital designers will never be confronted with the details of the manufacturing process that lay at the core of the semiconductor revolution. Still, some insight into the steps that lead to an operational silicon chip comes in quite handy in understanding the physical constraints imposed on a designer of an integrated circuit, as well as the impact of the fabrication process on issues such as cost.

In this chapter, we briefly describe the steps and techniques used in a modern integrated circuit manufacturing process. It is not our aim to present a detailed description of the fabrication technology, which easily deserves a complete course [Plummer00]. Rather, we aim at presenting the general outline of the flow and the interaction between the various steps. We learn that a set of *optical masks* forms the central interface between the intrinsics of the manufacturing process and the design that the user wants to see transferred to the silicon fabric. The masks define the patterns that, when transcribed onto the different layers of the semiconductor material, form the elements of the electronic devices and the interconnecting wires. As such, these patterns have to adhere to some constraints, in terms of minimum width and separation, if the resulting circuit is to be fully functional. This collection of constraints is called the *design rule set*, and acts as the contract between the circuit designer and the process engineer. If the designer adheres to these rules, he gets a guarantee that his circuit will be manufacturable. An overview of the common design rules encountered in modern CMOS processes is given, as well as a perspective on the *IC packaging* options. The package forms the interface between the circuit implemented on the silicon die and the outside world, and as such has a major impact on the performance, reliability, longevity, and cost of the integrated circuit.

## 2.2 Manufacturing CMOS Integrated Circuits

A simplified cross section of a typical CMOS inverter is shown in Figure 2-1. The CMOS process requires that both *n*-channel (NMOS) and *p*-channel (PMOS) transistors be built in the same silicon material. To accommodate both types of devices, special regions called *wells* must be created in which the semiconductor material is opposite to the type of the channel. A PMOS transistor has to be created in either an *n*-type substrate or an *n*-well, while an NMOS device resides in either a *p*-type substrate or a *p*-well. The cross section shown in Figure 2-1 features an

 


Figure 2-1 Cross section of an *n*-well CMOS process.

 


Figure 2-2 Cross section of modern dual-well CMOS process.

*n*-well CMOS process, where the NMOS transistors are implemented in the *p*-doped substrate, and the PMOS devices are located in the *n*-well. Modern processes are increasingly using a *dual-well* approach that uses both *n*- and *p*-wells, grown on top of an epitaxial layer, as shown in Figure 2-2.

The CMOS process requires a large number of steps, each of which consists of a sequence of basic operations. A number of these steps and/or operations are executed very repetitively in the course of the manufacturing process. Rather than immediately delving into a description of the overall process flow, we first discuss the starting material followed by a detailed perspective on some of the most frequently recurring operations.

### 2.2.1 The Silicon Wafer

The base material for the manufacturing process comes in the form of a single-crystalline, lightly doped *wafers*. These wafers have typical diameters between 4 and 12 inches (10 and 30 cm, respectively) and a thickness of, at most 1 mm. They are obtained by cutting a single-crystal ingot into thin slices (see Figure 2-3). A starting wafer of the *p*<sup>-</sup>-type might be doped around the levels of  $2 \times 10^{21}$  impurities/m<sup>3</sup>. Often, the surface of the wafer is doped more heavily, and a single crystal *epitaxial layer* of the opposite type is grown over the surface before the wafers are handed to the processing company. One important metric is the defect density of the base material. High defect densities lead to a larger fraction of nonfunctional circuits, and consequently an increase in cost of the final product.

### 2.2.2 Photolithography

In each processing step, a certain area on the chip is masked out using the appropriate optical mask so that a desired processing step can be selectively applied to the remaining regions. The processing step can be any of a wide range of tasks, including oxidation, etching, metal and polysilicon deposition, and ion implantation. The technique to accomplish this selective masking, called *photolithography*, is applied throughout the manufacturing process. Figure 2-4 gives



 


Figure 2-3 Single-crystal ingot and sliced wafers (from [Fullman99]).

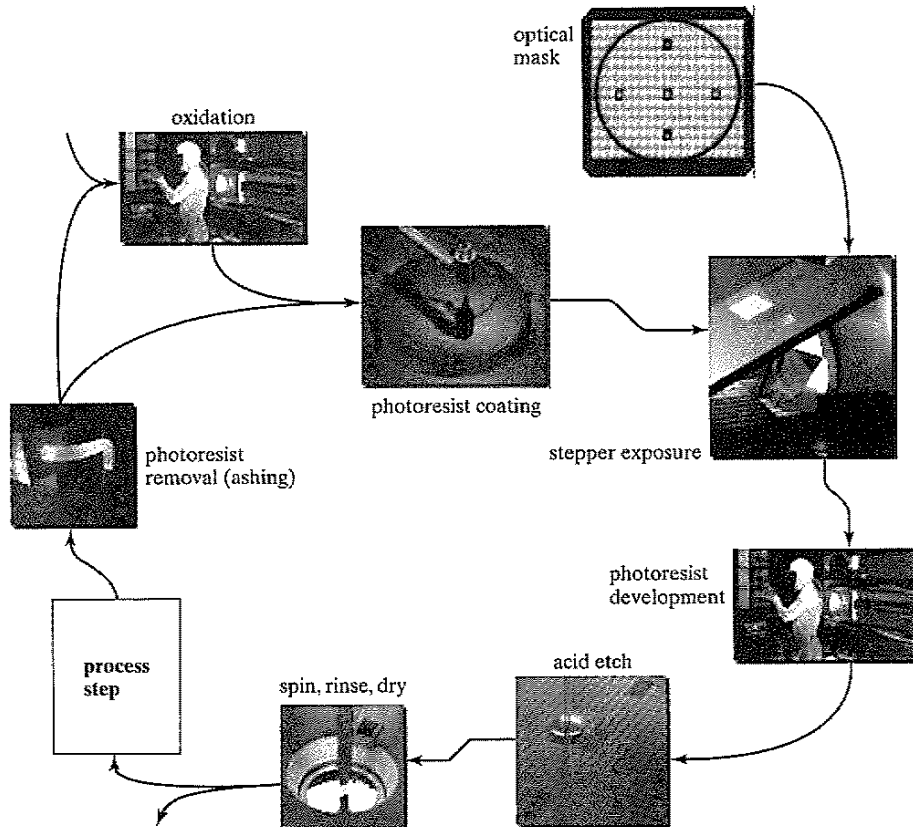


Figure 2-4 Typical operations in a single photolithographic cycle (from [Fullman99]).

a graphical overview of the different operations involved in a typical photolithographic process. The following steps can be identified:

1. *Oxidation layering*—this optional step deposits a thin layer of  $\text{SiO}_2$  over the complete wafer by exposing it to a mixture of high-purity oxygen and hydrogen at approximately  $1000^\circ\text{C}$ . The oxide is used as an insulation layer and also forms transistor gates.
2. *Photoresist coating*—a light-sensitive polymer (similar to latex) is evenly applied to a thickness of approximately  $1\ \mu\text{m}$  by spinning the wafer. This material is originally soluble in an organic solvent, but has the property that the polymers cross-link when exposed to light, making the affected regions insoluble. A photoresist of this type is called *negative*. A positive photoresist has the opposite properties; originally insoluble, but soluble after exposure. By using both positive and negative resists, a single mask can sometimes be used for two steps, making complementary regions available for processing. Since the cost of a mask is increasing quite rapidly with the scaling of technology, reducing the number of masks surely is a high priority.
3. *Stepper exposure*—a glass mask (or reticle) containing the patterns that we want to transfer to the silicon is brought in close proximity to the wafer. The mask is opaque in the regions that we want to process, and transparent in the others (assuming a negative photoresist). The glass mask can be thought of as the negative of one layer of the microcircuit. The combination of mask and wafer is now exposed to ultraviolet light. Where the mask is transparent, the photoresist becomes insoluble.
4. *Photoresist development and bake*—the wafers are developed in either an acid or base solution to remove the nonexposed areas of photoresist. Once the exposed photoresist is removed, the wafer is “soft baked” at a low temperature to harden the remaining photoresist.
5. *Acid etching*—material is selectively removed from areas of the wafer that are not covered by photoresist. This is accomplished through the use of many different types of acid, base and caustic solutions as a function of the material that is to be removed. Much of the work with chemicals takes place at large wet benches where special solutions are prepared for specific tasks. Because of the dangerous nature of some of these solvents, safety and environmental impact is a primary concern.
6. *Spin, rinse, and dry*—a special tool (called SRD) cleans the wafer with deionized water and dries it with nitrogen. The microscopic scale of modern semiconductor devices means that even the smallest particle of dust or dirt can destroy the circuitry. To prevent this from happening, the processing steps are performed in ultraclean rooms where the number of dust particles per cubic foot of air ranges between 1 and 10. Automatic wafer handling and robotics are used whenever possible. This explains why the cost of a state-of-the-art fabrication facility easily reaches multiple billions of dollars. Even then, the wafers must be constantly cleaned to avoid contamination and to remove the leftover of the previous process steps.

7. *Various process steps*—the exposed area can now be subjected to a wide range of process steps, such as ion implantation, plasma etching, or metal deposition. These are the subjects of the subsequent section.
8. *Photoresist removal (or ashing)*—a high-temperature plasma is used to selectively remove the remaining photoresist without damaging device layers.

In Figure 2-5, we illustrate the use of the photolithographic process for one specific example, the patterning of a layer of  $\text{SiO}_2$ . The sequence of process steps shown in the figure patterns exactly one layer of the semiconductor material and may seem very complex. Yet, the reader has to bear in mind that the same sequence patterns the layer of **the complete surface of the wafer**. Hence, it is a very parallel process, transferring hundreds of millions of patterns to the semiconductor surface simultaneously. The concurrent and scalable nature of the photolithographical process is what makes the cheap manufacturing of complex semiconductor circuits possible, and lies at the core of the economic success of the semiconductor industry.

The continued scaling of the minimum feature sizes in integrated circuits puts an enormous burden on the developer of semiconductor manufacturing equipment. This is especially true for the photolithographical process. The dimensions of the features to be transcribed surpass the wavelengths of the optical light sources, so that achieving the necessary resolution and accuracy

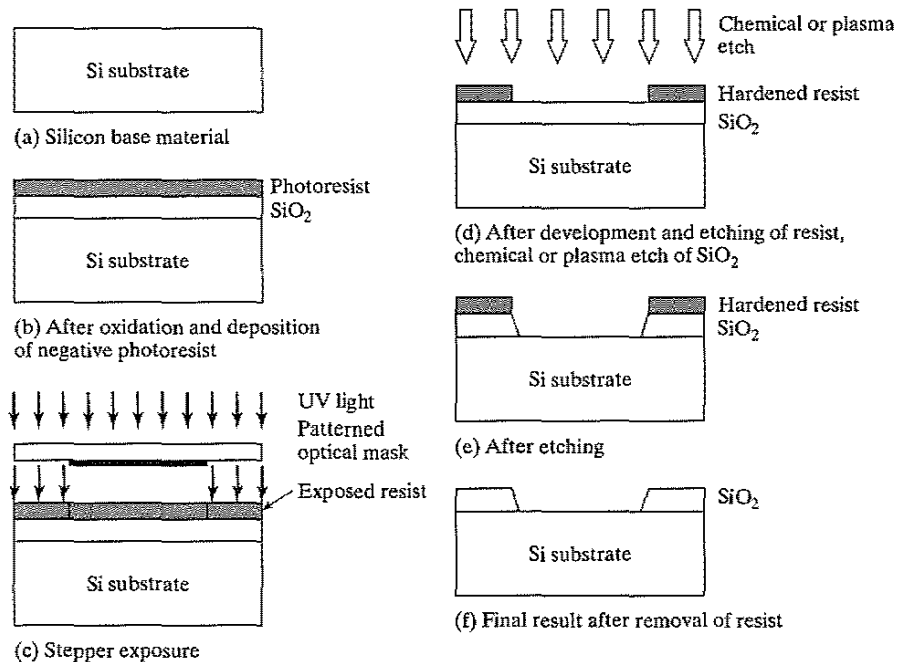


Figure 2-5 Process steps for patterning of  $\text{SiO}_2$ .

becomes more and more difficult. So far, electrical engineering has extended the lifetime of this process at least until the 100 nm (or 0.1  $\mu\text{m}$ ) process generation. Techniques such as *optical mask correction* (OPC) prewarp the drawn patterns to account for the diffraction phenomena, encountered when printing close to the wavelength of the available optical source. This adds substantially to the cost of mask making. In the foreseeable future, other solutions that offer a finer resolution, such as extreme ultraviolet (EUV), X ray, or electron beam, may be needed. These techniques, while fully functional, are currently less attractive from an economic viewpoint.

### 2.2.3 Some Recurring Process Steps

#### Diffusion and Ion Implantation

Many steps of the integrated circuit manufacturing process require a change in the dopant concentration of some parts of the material. Examples include the creation of the source and drain regions, well and substrate contacts, the doping of the polysilicon, and the adjustments of the device threshold. Two approaches exist for introducing these dopants—diffusion and ion implantation. In both techniques, the area to be doped is exposed, while the rest of the wafer is coated with a layer of buffer material, typically  $\text{SiO}_2$ .

In *diffusion implantation*, the wafers are placed in a quartz tube embedded in a heated furnace. A gas containing the dopant is introduced in the tube. The high temperatures of the furnace, typically 900 to 1100  $^{\circ}\text{C}$ , cause the dopants to diffuse into the exposed surface both vertically and horizontally. The final dopant concentration is the greatest at the surface and decreases in a gaussian profile deeper in the material.

In *ion implantation*, dopants are introduced as ions into the material. The ion implantation system directs and sweeps a beam of purified ions over the semiconductor surface. The acceleration of the ions determines how deep they will penetrate the material, while the beam current and the exposure time determine the dosage. The ion implantation method allows for an independent control of depth and dosage. This is the reason that ion implantation has largely displaced diffusion in modern semiconductor manufacturing.

Ion implantation has some unfortunate side effects, however, the most important one being lattice damage. Nuclear collisions during the high energy implantation cause the displacement of substrate atoms, leading to material defects. This problem is largely resolved by applying a subsequent *annealing* step, in which the wafer is heated to around 1000 $^{\circ}\text{C}$  for 15 to 30 minutes, and then allowed to cool slowly. The heating step thermally vibrates the atoms, which allows the bonds to reform.

#### Deposition

Any CMOS process requires the repetitive deposition of layers of a material over the complete wafer, to either act as buffers for a processing step, or as insulating or conducting layers. We have already discussed the oxidation process, which allows a layer of  $\text{SiO}_2$  to be grown. Other materials require different techniques. For instance, silicon nitride ( $\text{Si}_3\text{N}_4$ ) is used as a sacrificial buffer material during the formation of the field oxide and the introduction of the stopper

implants. This silicon nitride is deposited everywhere using a process called *chemical vapor deposition* or CVD. This process is based on a gas-phase reaction, with energy supplied by heat at around 850°C.

Polysilicon, on the other hand, is deposited using a chemical deposition process, which flows silane gas over the heated wafer coated with SiO<sub>2</sub> at a temperature of approximately 650°C. The resulting reaction produces a noncrystalline or amorphous material called *polysilicon*. To increase the conductivity of the material, the deposition has to be followed by an implantation step.

The Aluminum interconnect layers typically are deployed using a process known as *sputtering*. The aluminum is evaporated in a vacuum, with the heat for the evaporation delivered by electron-beam or ion-beam bombarding. Other metallic interconnect materials such as Copper require different deposition techniques.

### Etching

Once a material has been deposited, etching is used selectively to form patterns such as wires and contact holes. We already discussed the *wet etching* process, which makes use of acid or basic solutions. Hydrofluoric acid buffered with ammonium fluoride typically is used to etch SiO<sub>2</sub>, for example.


In recent years, *dry or plasma etching* has advanced substantially. A wafer is placed into the etch tool's processing chamber and given a negative electrical charge. The chamber is heated to 100°C and brought to a vacuum level of 7.5 Pa, then filled with a positively charged plasma (usually a mix of nitrogen, chlorine, and boron trichloride). The opposing electrical charges cause the rapidly moving plasma molecules to align themselves in a vertical direction, forming a microscopic chemical and physical "sandblasting" action which removes the exposed material. Plasma etching has the advantage of offering a well-defined directionality to the etching action, creating patterns with sharp vertical contours.

### Planarization

To reliably deposit a layer of material onto the semiconductor surface, it is essential that the surface be approximately flat. If special steps were not taken, this would definitely present problems in modern CMOS processes, where multiple patterned metal interconnect layers are superimposed onto each other. Therefore, a *chemical-mechanical planarization (CMP)* step is included before the deposition of an extra metal layer on top of the insulating SiO<sub>2</sub> layer. This process uses a slurry compound—a liquid carrier with a suspended abrasive component such as aluminum oxide or silica—to microscopically plane a device layer and to reduce the step heights.

#### 2.2.4 Simplified CMOS Process Flow


The gross outline of a potential CMOS process flow is given in Figure 2-6. The process starts with the definition of the *active regions*—these are the regions where transistors will be constructed. All other areas of the die will be covered with a thick layer of silicon dioxide (SiO<sub>2</sub>)

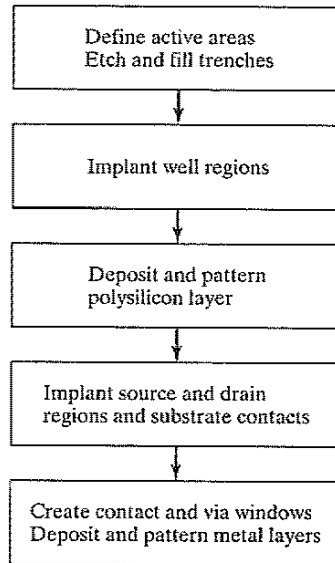

**Figure 2-6** Simplified process sequence for the manufacturing of a n-dual-well CMOS circuit.

called the *field oxide*. This oxide acts as the insulator between neighboring devices, and it is either grown (as in the process of Figure 2-1) or deposited in etched trenches (Figure 2-2)—hence, the name *trench insulation*. Further insulation is provided by the addition of a reverse-biased *np*-diode, formed by adding an extra  $p^+$  region called the *channel-stop implant* (or *field implant*) underneath the field oxide. Next, lightly doped *p*- and *n*-wells are formed through ion implantation. To construct an NMOS transistor in a *p*-well, heavily doped *n*-type *source* and *drain* regions are implanted (or diffused) into the lightly doped *p*-type substrate. A thin layer of  $\text{SiO}_2$  called the *gate oxide* separates the region between the source and drain, and is itself covered by conductive polycrystalline silicon (or *polysilicon*, for short). The conductive material forms the *gate* of the transistor. PMOS transistors are constructed in an *n*-well in a similar fashion (just reverse *n*'s and *p*'s). Multiple insulated layers of metallic (most often Aluminum) wires are deposited on top of these devices to provide for the necessary interconnections between the transistors.

A more detailed breakdown of the flow into individual process steps and their impact on the semiconductor material is shown graphically in Figure 2-7. While most of the operations should be self-explanatory in light of the previous descriptions, some comments on individual operations are worthwhile. The process starts with a *p*-substrate surfaced with a lightly doped *p*-epitaxial layer (a). A thin layer of  $\text{SiO}_2$  is then deposited, which will serve as the gate oxide for the transistors, followed by a deposition of a thicker sacrificial silicon nitride layer (b). A plasma etching step using the complementary of the active area mask creates the trenches used for insulating the devices (c). After providing the channel stop implant, the trenches are filled

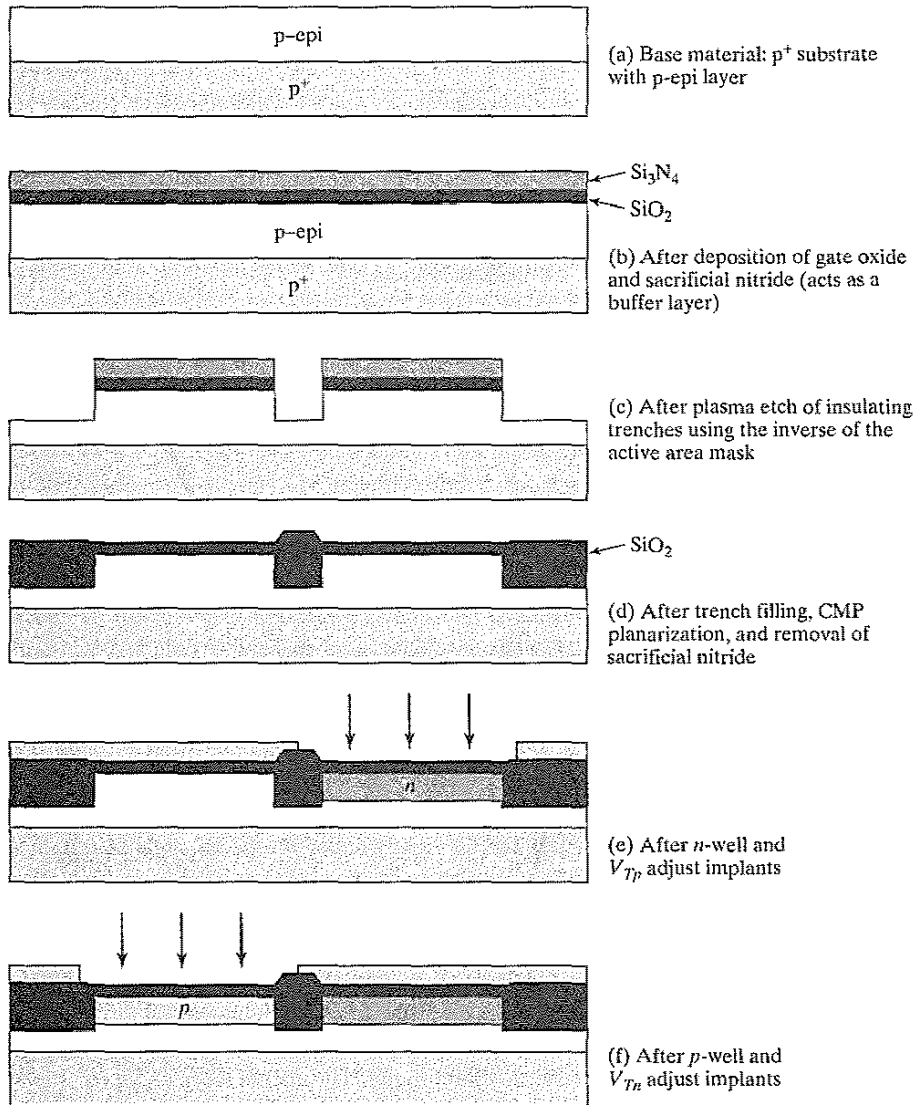

**Figure 2-7** Process flow for the fabrication of an NMOS and a PMOS transistor in a dual-well CMOS process. Be aware that the drawings are stylized for understanding and that the aspect ratios are not proportioned to reality.

with  $\text{SiO}_2$  followed by a number of steps to provide a flat surface (including inverse active pattern oxide etching, and chemical-mechanical planarization). At that point, the sacrificial nitride is removed (d). The  $n$ -well mask is used to expose only the  $n$ -well areas (the rest of the wafer is covered by a thick buffer material), after which an implant-annealing sequence is applied to

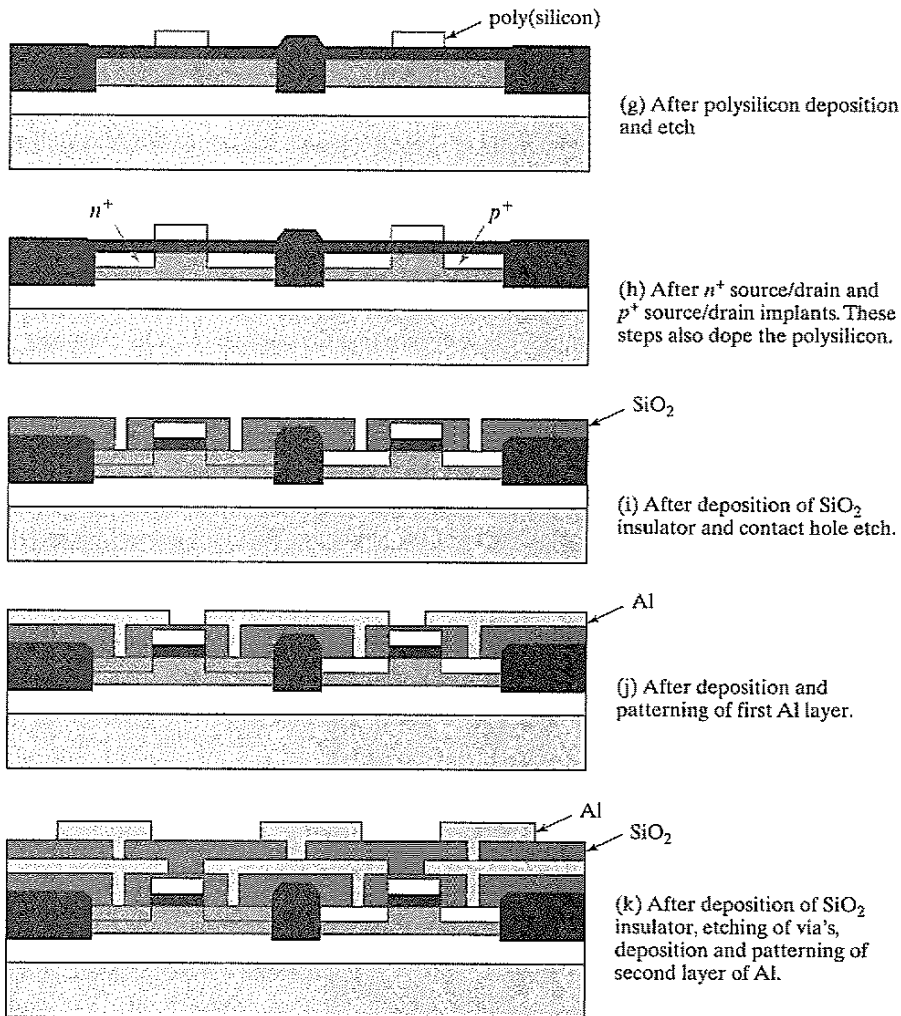


Figure 2-7 (cont.)

adjust the well-doping. This is followed by a second implant step to adjust the threshold voltages of the PMOS transistors. This implant only impacts the doping in the area just below the gate oxide (e). Similar operations (using other dopants) are performed to create the  $p$ -wells, and to adjust the thresholds of the NMOS transistors (f). A thin layer of polysilicon is chemically deposited and patterned with the aid of the polysilicon mask. Polysilicon is used both as gate electrode material for the transistors and as an interconnect medium (g). Consecutive ion implantations are used to dope the source and drain regions of the PMOS ( $p^+$ ) and NMOS ( $n^+$ ) transistors, respectively (h), after which the thin gate oxide not covered by the polysilicon is



etched away.<sup>1</sup> The same implants also are used to dope the polysilicon on the surface, reducing its resistivity. Undoped polysilicon has a very high resistivity. Note that the polysilicon gate, which is patterned before the doping, actually defines the precise location of the channel region, and thus the location of the source and drain regions. This procedure, called the *self-aligned process*, allows for a very precise positioning of the two regions relative to the gate. Self-alignment is instrumental in reducing parasitic capacitances in the transistor. The process continues with the deposition of the metallic interconnect layers. These consist of a repetition of the following steps (i–k): deposition of the insulating material (most often  $\text{SiO}_2$ ), etching of the contact or via holes, deposition of the metal (most often aluminum and copper, although tungsten often is used for the lower layers), and patterning of the metal. Intermediate planarization steps, using *chemical–mechanical polishing* or CMP, ensure that the surface remains reasonably flat, even in the presence of multiple interconnect layers. After the last level of metal is deposited, a final passivation or *overglass* is deposited for protection. This layer would be CVD  $\text{SiO}_2$ , although often an additional layer of nitride is deposited because it is more impervious to moisture. The final processing step etches openings to the pads used for bonding.

A cross section of the final artifact is shown in Figure 2-8. Observe how the transistors occupy only a small fraction of the total height of the structure. The interconnect layers take up the majority of the vertical dimension.

 


Figure 2-8 Cross section of state-of-the-art CMOS process.

<sup>1</sup>Most modern processes also include extra implants for the creation of the lightly doped drain regions (LDD), and the creation of gate spacers at this point. We have omitted these for the sake of simplicity.

### 2.3 Design Rules—Between the Designer and the Process Engineer

As processes become more complex, requiring the designer to understand the intricacies of the fabrication process and interpret the relations between the different masks is a sure road to trouble. The goal of defining a set of design rules is to allow for a ready translation of a circuit concept into an actual geometry in silicon. The design rules act as the interface or even the contract between the circuit designer and the process engineer.

Circuit designers generally want tighter, smaller designs, which lead to higher performance and higher circuit density. The process engineer, on the other hand, wants a reproducible and high-yield process. Consequently, design rules are a compromise that attempts to satisfy both sides.

The design rules provide a set of guidelines for constructing the various masks needed in the patterning process. They consist of minimum-width and minimum-spacing constraints and requirements between objects on the same or different layers.

The fundamental unity in the definition of a set of design rules is the *minimum line width*. It stands for the minimum mask dimension that can be safely transferred to the semiconductor material. In general, the minimum line width is set by the resolution of the patterning process, which is most commonly based on optical lithography. More advanced approaches use electron-beam EUV, or X-ray sources, all of which offer a finer resolution, but currently they are less attractive from an economical standpoint.

Even for the same minimum dimension, design rules tend to differ from company to company, and from process to process. This makes porting an existing design between different processes a time-consuming task. One approach to address this issue is to use advanced CAD techniques, which allow for migration between compatible processes. Another approach is to use *scalable design rules*. The latter approach, made popular by Mead and Conway [Mead80], defines all rules as a function of a single parameter, most often called  $\lambda$ . The rules are chosen so that a design is easily ported over a cross section of industrial processes. Scaling of the minimum dimension is accomplished by simply changing the value of  $\lambda$ . This results in a *linear scaling* of all dimensions. For a given process,  $\lambda$  is set to a specific value, and all design dimensions are consequently translated into absolute numbers. Typically, the minimum line width of a process is set to  $2\lambda$ . For instance, for a  $0.25\ \mu\text{m}$  process (i.e., a process with a minimum line width of  $0.25\ \mu\text{m}$ ),  $\lambda$  equals  $0.125\ \mu\text{m}$ .

This approach, while attractive, suffers from two disadvantages:

1. Linear scaling is possible only over a limited range of dimensions (for instance, between  $0.25\ \mu\text{m}$  and  $0.18\ \mu\text{m}$ ). When scaling over larger ranges, the relations between the different layers tend to vary in a nonlinear way that cannot be adequately covered by the linear scaling rules.
2. Scalable design rules are conservative: They represent a cross section over different technologies, and they must represent the worst case rules for the whole set. This results in overdimensioned and less dense designs.

For these and other reasons, scalable design rules normally are avoided by industry.<sup>2</sup> As circuit density is a prime goal in industrial designs, most semiconductor companies tend to use *micron rules*, which express the design rules in absolute dimensions and therefore can exploit the features of a given process to a maximum degree. Scaling and porting designs between technologies under these rules is more demanding and has to be performed either manually or using advanced CAD tools.

For this book, we have selected a “vanilla” 0.25  $\mu\text{m}$  CMOS process as our preferred implementation medium. The rest of this section is devoted to a short introduction and overview of the design rules of this process, which fall in the micron-rules class. A complete design-rule set consists of the following entities: a set of layers, relations between objects on the same layer, and relations between objects on different layers. We discuss each of them in sequence.

### Layer Representation

The layer concept translates the intractable set of masks currently used in CMOS into a simple set of conceptual layout levels that are easier to visualize by the circuit designer. From a designer’s viewpoint, all CMOS designs are based on the following entities:

- *Substrates and/or wells*, which are *p*-type (for NMOS devices) and *n*-type (for PMOS)
- *Diffusion regions* ( $n^+$  and  $p^+$ ), which define the areas where transistors can be formed. These regions are often called the *active areas*. Diffusions of an inverse type are needed to implement contacts to the wells or to the substrate. These are called *select regions*.
- One or more *polysilicon* layers, which are used to form the gate electrodes of the transistors (but serve as interconnect layers as well).
- A number of *metal interconnect* layers.
- *Contact and via* layers, which provide interlayer connections.

A layout consists of a combination of polygons, each of which is attached to a certain layer. The functionality of the circuit is determined by the choice of the layers, as well as the interplay between objects on different layers. For example, an MOS transistor is formed by the cross section of the diffusion layer and the polysilicon layer. An interconnection between two metal layers is formed by a cross section between the two metal layers and an additional contact layer. To visualize these relations, each layer is assigned a standard color (or stipple pattern for a black-and-white representation). The different layers used in our CMOS process are represented in Colorplate 1 (color insert).

### Intralayer Constraints

A first set of rules defines the minimum dimensions of objects on each layer, as well as the minimum spacings between objects on the same layer. All distances are expressed in  $\mu\text{m}$ . These constraints are presented in pictorial fashion in Colorplate 2.

<sup>2</sup>While not entirely accurate, lambda rules are still useful to estimate the impact of a technology scale on the area of a design.

### Interlayer Constraints

Interlayer rules tend to be more complex. Because multiple layers are involved, it is harder to visualize their meaning or functionality. Understanding layout requires the capability of translating the two-dimensional picture of the layout drawing into the three-dimensional reality of the actual device. This takes some practice.

We present these rules in a set of separate groupings:

1. *Transistor Rules* (Colorplate 3). A transistor is formed by the overlap of the active and the polysilicon layers. From the intralayer design rules, it is already clear that the minimum length of a transistor equals  $0.24\ \mu\text{m}$  (the minimum width of polysilicon), while its width is at least  $0.3\ \mu\text{m}$  (the minimum width of diffusion). Extra rules include the spacing between the active area and the well boundary, the gate overlap of the active area, and the active overlap of the gate.
2. *Contact and Via Rules* (Colorplates 2 and 4). A contact (which forms an interconnection between metal and active or polysilicon) or a via (which connects two metal layers) is formed by overlapping the two interconnecting layers and providing a contact hole, filled with metal, between the two. In our process, the minimum size of the contact hole is  $0.3\ \mu\text{m}$ , while the polysilicon and diffusion layers have to extend at least  $0.14\ \mu\text{m}$  beyond the area of the contact hole. This sets the minimum area of a contact to  $0.44\ \mu\text{m} \times 0.44\ \mu\text{m}$ . This is larger than the dimensions of a minimum-size transistor! Excessive changes between interconnect layers in routing should therefore be avoided. The figure, furthermore, points out the minimum spacings between contact and via holes, as well as their relationship with the surrounding layers.
3. *Well and Substrate Contacts* (Colorplate 5). For robust digital circuit design, it is important for the well and substrate regions to be adequately connected to the supply voltages. Failing to do so results in a resistive path between the substrate contact of the transistors and the supply rails, and can lead to possibly devastating parasitic effects, such as latchup. It is therefore advisable to provide numerous substrate (well) contacts spread over the complete region. To establish an ohmic contact between a supply rail, implemented in metal, and a  $p$ -type material, a  $p^+$  diffusion region must be provided. This is enabled by the *select* layer, which reverses the type of diffusion. A number of rules regarding the use of the *select* layer are illustrated in Colorplate 5.

Consider an  $n$ -well process, which implements the PMOS transistors into an  $n$ -type well diffused in a  $p$ -type material. The nominal diffusion is  $p^+$ . To invert the polarity of the diffusion, an  $n$ -select layer is provided that helps to establish the  $n^+$  diffusions for the well contacts in the  $n$ -region, as well as the  $n^+$  source and drain regions for the NMOS transistors in the substrate.


### Verifying the Layout

Ensuring that none of the design rules are violated is a fundamental requirement of the design process. Failing to do so will almost surely lead to a nonfunctional design. Doing so for a complex design that can contain millions of transistors is no simple task either, especially given the complexity of some design-rule sets. While design teams in the past used to spend numerous

hours staring at room-size layout plots, most of this work is now done by computers. Computer-aided *Design-Rule Checking* (called *DRC*) is an integral part of the design cycle for virtually every chip produced today. A number of layout tools even perform *on-line DRC* and check the design in the background during the time of conception.

### Example 2.1 Layout Example

An example of a complete layout containing an inverter is shown in Figure 2-9. To help the visualization process, a vertical cross section of the process along the design center is included, as well as a circuit schematic.

 

**Figure 2-9** A detailed layout example, including vertical process cross section and circuit diagram.

It is left as an exercise for the reader to determine the sizes of both the NMOS and the PMOS transistors.

## 2.4 Packaging Integrated Circuits

The IC package plays a fundamental role in the operation and performance of a component. Besides providing a means of bringing signal and supply wires in and out of the silicon die, it also removes the heat generated by the circuit and provides mechanical support. Finally, it also protects the die against environmental conditions such as humidity.

In addition, the packaging technology has a major impact on the performance and power dissipation of a microprocessor or signal processor. This influence is getting more pronounced as time progresses due to the reduction in internal signal delays and on-chip capacitance resulting from technology scaling. Currently, up to 50% of the delay of a high-performance computer is due to packaging delays, and this number is expected to rise. The search for higher performance packages with fewer inductive or capacitive parasitics has accelerated in recent years. The increasing complexity of what can be integrated on a single die also translates into a need for ever more input/output pins, as the number of connections going off-chip tends to be roughly proportional to the complexity of the circuitry on the chip. This relationship was first observed by E. Rent of IBM (published in [Landman71]), who translated it into an empirical formula that, appropriately, is called *Rent's rule*. This formula relates the number of input/output pins to the complexity of the circuit, as measured by the number of gates. It is written as

$$P = K \times G^\beta \quad (2.1)$$

where  $K$  is the average number of I/Os per gate,  $G$  the number of gates,  $\beta$  the Rent exponent, and  $P$  the number of I/O pins to the chip.  $\beta$  varies between 0.1 and 0.7. Its value depends strongly upon the application area, architecture, and organization of the circuit, as demonstrated in Table 2-1. Clearly, microprocessors display a very different input/output behavior compared to memories.

The observed rate of pin-count increase for integrated circuits varies from 8% to 11% per year, and it has been projected that packages with more than 2000 pins will be required by 2010. For all these reasons, traditional dual-in-line, through-hole mounted packages have been replaced by other approaches, such as surface-mount, ball-grid array, and multichip module

**Table 2-1** Rent's constant for various classes of systems ([Bakoglu90])

Application	$\beta$	$K$
Static memory	0.12	6
Microprocessor	0.45	0.82
Gate array	0.5	1.9
High-speed computer (chip)	0.63	1.4
High-speed computer (board)	0.25	82

techniques. It is useful for the circuit designer to be aware of the available options and their pros and cons.

Due to its multifunctionality, a good package must comply with a large variety of requirements:

- **Electrical requirements**—Pins should exhibit low capacitance (both interwire and to the substrate), resistance, and inductance. A large characteristic impedance should be tuned to optimize transmission line behavior. Observe that intrinsic integrated-circuit impedances are high.
- **Mechanical and thermal properties**—The heat removal rate should be as high as possible. Mechanical reliability requires a good matching between the thermal properties of the die and the chip carrier. Long-term reliability requires a strong connection from die to package, as well as from package to board.
- **Low Cost**—Cost is one of the more important properties to consider in any project. For example, while ceramics have a superior performance over plastic packages, they are also substantially more expensive. Increasing the heat removal capacity of a package also tends to raise the package cost. The least expensive plastic packaging can dissipate up to 1 W. Slightly more expensive, but still of somewhat low quality, plastic packages can dissipate up to 2 W. Higher dissipation requires more expensive ceramic packaging. Chips dissipating over 20 W require special heat sink attachments. Even more extreme techniques such as fans and blowers, liquid cooling hardware, or heat pipes are needed for higher dissipation levels.

Packing density is a major factor in reducing board cost. The increasing pin count either requires an increase in the package size or a reduction in the pitch between the pins. Both have a profound effect on the packaging economics.

Packages can be classified in many different ways: by their main material, the number of interconnection levels, and the means used to remove heat. In this brief section, we provide only sketches of each of those issues.

### 2.4.1 Package Materials

The most common materials used for the package body are ceramic and polymers (plastics). The latter have the advantage of being substantially cheaper, but they suffer from inferior thermal properties. For example, the ceramic  $\text{Al}_2\text{O}_3$  (alumina) conducts heat better than  $\text{SiO}_2$  and the polyimide plastic by factors of 30 and 100, respectively. Furthermore, its thermal expansion coefficient is substantially closer to the typical interconnect metals. The disadvantage of alumina and other ceramics is their high dielectric constant, which results in large interconnect capacitances.

### 2.4.2 Interconnect Levels

The traditional packaging approach uses a two-level interconnection strategy. The die is first attached to an individual chip carrier or substrate. The package body contains an internal cavity where the chip is mounted. These cavities provide ample room for many connections to the chip leads (or pins). The leads compose the second interconnect level and connect the chip to the global interconnect medium, which normally is a PC board. Complex systems contain even more interconnect levels, since boards are connected together using backplanes or ribbon cables. The first two layers of the interconnect hierarchy are illustrated in the drawing of Figure 2-10. The sections that follow provide a brief overview of the interconnect techniques used at levels one and two of the interconnect hierarchy, and a brief discussion of some more advanced packaging approaches.

#### Interconnect Level 1—Die-to-Package Substrate

For a long time, *wire bonding* was the technique of choice to provide an electrical connection between die and package. In this approach, the backside of the die is attached to the substrate using glue with a good thermal conductance. Next, the chip pads are individually connected to the lead frame with aluminum or gold wires. The wire-bonding machine used for this purpose operates much like a sewing machine. An example of wire bonding is shown in Figure 2-11. Although the wire-bonding process is automated to a large degree, it has some major disadvantages:

1. Wires must be attached serially, one after the other. This leads to longer manufacturing times with increasing pin counts.
2. Larger pin counts make it substantially more challenging to find bonding patterns that avoid shorts between the wires.
3. The exact value of the parasitics is hard to predict because of the manufacturing approach and irregular outlay.


 


Figure 2-10 Interconnect hierarchy in traditional IC packaging.

 



**Figure 2-11** Wire bonding.

Bonding wires have inferior electrical properties, such as a high individual inductance (5 nH or more) and mutual inductance with neighboring signals. The inductance of a bonding wire is typically about 1 nH/mm, while the inductance per package pin ranges between 7 and 40 nH per pin, depending on the type of package as well as the positioning of the pin on the package boundary [Steidel83]. Typical values of the parasitic inductances and capacitances for a number of commonly used packages are summarized in Table 2-2.

New attachment techniques are being explored as a result of these deficiencies. In one approach, called *Tape Automated Bonding* (or TAB), the die is attached to a metal lead frame that is printed on a polymer film, typically polyimide (see Figure 2-12a). The connection between chip pads and polymer film wires is made using solder bumps (Figure 2-12b). The tape can then be connected to the package body using a number of techniques. One possible approach is to use pressure connectors.

The advantage of the TAB process is that it is highly automated. The sprockets in the film are used for automatic transport. All connections are made simultaneously. The printed approach helps to reduce the wiring pitch, which results in higher lead counts. Elimination of the long bonding wires improves the electrical performance. For instance, for a two-conductor layer, 48 mm

**Table 2-2** Typical capacitance and inductance values of package and bonding styles (from [Steidel83], [Franzon93], and [Harper00]).

Package Type	Capacitance (pF)	Inductance (nH)
68-pin plastic DIP	4	35
68-pin ceramic DIP	7	20
300 pin Ball Grid Array	1-5	2-15
Wire bond	0.5-1	1-2
Solder bump	0.1-0.5	0.01-0.1

 


Figure 2-12 Tape-automated bonding (TAB).

 


Figure 2-13 Flip-chip bonding.

TAB Circuit, the following electrical parameters hold:  $L = 0.3\text{--}0.5$  nH,  $C \approx 0.2\text{--}0.3$  pF, and  $R \approx 50\text{--}200$   $\Omega$  [Doane93, p. 420].

Another approach is to flip the die upside down and attach it directly to the substrate using solder bumps. This technique, called *flip-chip* mounting, has the advantage of a superior electrical performance (see Figure 2-13.) Instead of making all the I/O connections on the die boundary, pads can be placed at any position on the chip. This can help address the power- and clock-distribution problems, since the interconnect materials on the substrate (e.g., Cu or Au) typically are of better quality than the Al on the chip.

#### Interconnect Level 2—Package Substrate to Board

When connecting the package to the PC board, *through-hole mounting* has been the packaging style of choice. A PC board is manufactured by stacking layers of copper and insulating epoxy glass. In the through-hole mounting approach, holes are drilled through the board and plated with copper. The package pins are inserted and electrical connection is made with solder (see Figure 2-14a). The favored package in this class was the *dual-in-line* package or DIP, as in Figure 2-15-2. The packaging density of the DIP degrades rapidly when the number of pins exceeds 64. This problem can be alleviated by using the *pin-grid-array* (PGA) package that has

 


Figure 2-14 Board-mounting approaches.

leads on the entire bottom surface instead of only on the periphery (Figure 2-15-3). PGAs can extend to large pin counts (over 400 pins are possible).

The through-hole mounting approach offers a mechanically reliable and sturdy connection. However, this comes at the expense of packaging density. For mechanical reasons, a minimum pitch of 2.54 mm between the through holes is required. Even under those circumstances, PGAs with large numbers of pins tend to substantially weaken the board. In addition, through holes limit the board packing density by blocking lines that might otherwise have been routed below them, which results in longer interconnections. PGAs with large pin counts therefore require extra routing layers to connect to the multitudes of pins. Finally, while the parasitic capacitance and inductance of the PGA are slightly lower than that of the DIP, their values are still substantial.

Many of the shortcomings of the through-hole mounting approach are solved by using the *surface-mount* technique. A chip is attached to the surface of the board with a solder connection without requiring any through holes (Figure 2-14b). Packing density is increased for the following reasons: (1) through holes are eliminated, which provides more wiring space; (2) the lead pitch is reduced; and (3) chips can be mounted on both sides of the board. In addition, the elimination of the through holes improves the mechanical strength of the board. On the negative side, the on-the-surface connection makes the chip-board connection weaker. Not only is it cumbersome to mount a component on a board, but also more expensive equipment is needed, since a simple soldering iron will no longer suffice. Finally, testing of the board is more complex, because the package pins are no longer accessible at the backside of the board. Signal probing becomes difficult or almost impossible.

A variety of surface-mount packages are currently in use with different pitch and pin-count parameters. Three of these packages are shown in Figure 2-15: the *small-outline package* with gull wings, the *plastic leaded package* (PLCC) with J-shaped leads, and the *leadless chip carrier*. An overview of the most important parameters for a number of packages is given in Table 2-3.

Even surface-mount packaging is unable to satisfy the quest for ever higher pin counts. This is worsened by the demand for power connections: today's high performance chips, operating at low supply voltages, require as many power and ground pins as signal I/Os! When more than 300 I/O connections are needed, solder balls replace pins as the preferred interconnect medium between package and board. An example of such a packaging approach, called ceramic

 


Figure 2-15 An overview of commonly used package types.


Table 2-3 Parameters of various types of chip carriers.

Package Type	Lead Spacing (Typical)	Lead Count (Maximum)
Dual in line	2.54 mm	64
Pin grid array	2.54 mm	> 300
Small-outline IC	1.27 mm	28
Leaded chip carrier (PLCC)	1.27 mm	124
Leadless chip carrier	0.75 mm	124

*ball grid array* (BGA), is shown in Figure 2-16. Solder bumps are used to connect both the die to the package substrate, and the package to the board. The area array interconnect of the BGA provides constant input/output density regardless of the number of total package I/O pins. A minimum pitch between solder balls of as low as 0.8 mm can be obtained, and packages with multiple thousands of I/O signals are feasible.

#### Multichip Modules—Die-to-Board

The deep hierarchy of interconnect levels in the package is becoming unacceptable in today's complex designs due to their higher levels of integration, large signal counts, and increased performance requirements. The trend, therefore, is toward reducing the number of levels. For the time being, attention is focused on the elimination of the first level in the packaging hierarchy. Removing one layer in the packaging hierarchy by mounting the die directly on the

 

**Figure 2-16** Ball grid array packaging; (a) cross section, (b) photo of package bottom.

wiring backplanes—board or substrate—offers a substantial benefit when performance or density is a major issue. This packaging approach is called the multichip module technique (or MCM), and results in a substantial increase in packing density, as well as improved performance overall.

A number of the previously mentioned die-mounting techniques can be adapted to mount dies directly on the substrate, including wire bonding, TAB, and flip-chip, although the latter two are preferable. The substrate itself can vary over a wide range of materials, depending upon the required mechanical, electrical, thermal, and economical requirements. Materials of choice are epoxy substrates (similar to PC boards), metal, ceramics, and silicon. Silicon has the advantage of presenting a perfect match in mechanical and thermal properties with respect to the die material.

The main advantages of the MCM approach are the increased packaging density and performance. An example of an MCM module implemented using a silicon substrate (commonly dubbed *silicon on silicon*) is shown in Figure 2-17. The module, which implements an avionics processor module and is fabricated by Rockwell International, contains 53 ICs and 40 discrete devices on a 2.2" × 2.2" substrate with aluminum polyimide interconnect. The interconnect wires are only an order of magnitude wider than what is typical for on-chip wires, since similar patterning approaches are used. The module itself has 180 I/O pins. Performance is improved by the elimination of the chip-carrier layer with its assorted parasitics, and through a reduction of the global wiring lengths on the die, a result of the increased packaging density. For instance, a solder bump has an assorted capacitance and inductance of only 0.1 pF and 0.01 nH, respectively. The MCM technology can also reduce power consumption significantly, since large output drivers—and associated dissipation—become superfluous due to the reduced load capacitance of the output pads. The dynamic power associated with the switching of the large load capacitances is simultaneously reduced.

While MCM technology offers some clear benefits, its main disadvantage is economic. This technology requires some advanced manufacturing steps that make the process expensive. The approach was until recently only justifiable when either dense housing or extreme performance is essential. In recent years, the economics have been shifting, and advanced multichip

 


Figure 2-17 Avionics processor module. Courtesy of Rockwell Collins, Inc.

packaging approaches have made inroad in several low-cost high-density applications as well. This trend is called the *system-in-a-package* (SIP) strategy.

### 2.4.3 Thermal Considerations in Packaging

As the power consumption of integrated circuits rises, it becomes increasingly important to efficiently remove the heat generated by the chips. A large number of failure mechanisms in ICs are accentuated by increased temperatures. Examples are leakage in reverse-biased diodes, electromigration, and hot-electron trapping. To prevent failure, the temperature of the die must be kept within certain ranges. The supported temperature range for commercial devices during operation equals 0° to 70°C. Military parts are more demanding and require a temperature range varying from -55° to 125°C.

The cooling effectiveness of a package depends on the thermal conduction (resistance) of the package material, which consists of the package substrate and body, the package composition, and the effectiveness of the heat transfer between package and cooling medium. Standard packaging approaches use still or circulating air as the cooling medium. The transfer efficiency can be improved by adding finned metal heat sinks to the package. More expensive packaging approaches, such as those used in mainframes or supercomputers, force air, liquids, or inert gases through tiny ducts in the package to achieve even greater cooling efficiencies.

Given the thermal resistance  $\theta$  of the package, expressed in °C/W, we can derive the chip temperature by using the *heat flow equation*

$$\Delta T = T_{chip} - T_{env} = \theta Q, \quad (2.2)$$

with  $T_{chip}$  and  $T_{env}$ , the chip and environment temperatures, respectively.  $Q$  represents the heat flow (in Watt). Observe how closely the heat flow equation resembles Ohm's Law. The heat flow and temperature differential are the equivalents of current and voltage difference, respectively. Thermal modeling of a chip, its package, and its environment is a complex task. We refer the reader to [Lau98 – Chapter 3] for a more detailed discussion on the topic.

---

### Example 2.2 Thermal Conduction of Package

As an example, a 40-pin DIP has a thermal resistance of 38°C/W and 25°C/W for natural and forced convection of air. This means that a DIP can dissipate 2 watts (3 watts) of power with natural (forced) air convection, and still keep the temperature difference between the die and the environment below 75°C. For comparison, the thermal resistance of a ceramic PGA ranges from 15° to 30°C/W.

Since packaging approaches with decreased thermal resistance are prohibitively expensive, keeping the power dissipation of an integrated circuit within bounds is an economic necessity. The increasing integration levels and circuit performance make this task nontrivial. An interesting relationship in this context has been derived by Nagata [Nagata92]. It provides a bound on the integration complexity and performance as a function of the thermal parameters. We write

$$\frac{N_G}{t_p} \leq \frac{\Delta T}{\theta E} \quad (2.3)$$

where  $N_G$  is the number of gates on the chip,  $t_p$  the propagation delay,  $\Delta T$  the maximum temperature difference between chip and environment,  $\theta$  the thermal resistance between them, and  $E$  the switching energy of each gate.

---

### Example 2.3 Thermal Bounds on Integration

For  $\Delta T = 100^\circ\text{C}$ ,  $\theta = 2.5^\circ\text{C/W}$  and  $E = 0.1$  pJ, this results in  $N_G/t_p \leq 4 \times 10^5$  (gates/nsec). In other words, the maximum number of gates on a chip, when all gates are operating simultaneously, must be less than 400,000 if the switching speed of each gate is 1 nsec. This is equivalent to a power dissipation of 40 W.

Fortunately, not all gates are operating simultaneously in real systems. The maximum number of gates can be substantially larger, based on the activity in the circuit. For example, it has been experimentally derived that the ratio between the average switching period and the propagation delay ranges from 20 to 200 in mini- and large-scale computers [Masaki92].

Nevertheless, Eq. (2.3) demonstrates that heat dissipation and thermal concerns present an important limitation on circuit integration. Design approaches for low power that reduce either  $E$  or the activity factor are rapidly gaining importance.

## 2.5 Perspective—Trends in Process Technology

Modern CMOS processes pretty much track the flow described in the previous sections, although a number of the steps might be reversed, a single well approach might be followed, a grown field oxide instead of the trench approach might be used, or extra steps such as LDD (*Lightly Doped Drain*) might be introduced. Also, it is quite common to cover the polysilicon interconnections as well as the drain and source regions with a *silicide* such as  $\text{TiSi}_2$  to improve the conductivity (see Figure 2-2). This extra operation is inserted between steps  $i$  and  $j$  of our process. Some important modifications or improvements to the technology are currently under way or are on the horizon, and deserve some attention. Beyond these, we expect no dramatic changes from the described CMOS technology in the next decade.

### 2.5.1 Short-Term Developments

#### Copper and Low- $k$ Dielectrics


A recurring theme throughout this book will be the increasing impact of interconnect on the overall design performance. Process engineers are continuously evaluating alternative options for the traditional Aluminum-conductor- $\text{SiO}_2$ -insulator combination that has been the norm for the last several decades. In 1998, engineers at IBM introduced an approach that finally made the use of copper as an interconnect material in a CMOS process viable and economical [Geppert98]. Copper has a resistivity that is substantially lower than aluminum. It has the disadvantage of easy diffusion into silicon, which degrades the characteristics of the devices. Coating the copper with a buffer material such as titanium-nitride, preventing the diffusion, addresses this problem, but requires a special deposition process. The Dual Damascene process, introduced by IBM, (Figure 2-18) uses a metallization approach that fills trenches etched into the insulator, followed by a chemical-mechanical polishing step. This is in contrast with the traditional approach that first deposits a full metal layer, and removes the redundant material through etching.

In addition to the lower resistivity interconnections, insulator materials with a lower dielectric constant than  $\text{SiO}_2$ , and hence, lower capacitance have also found their way into the production process, starting with the 0.18- $\mu\text{m}$  CMOS process generation.
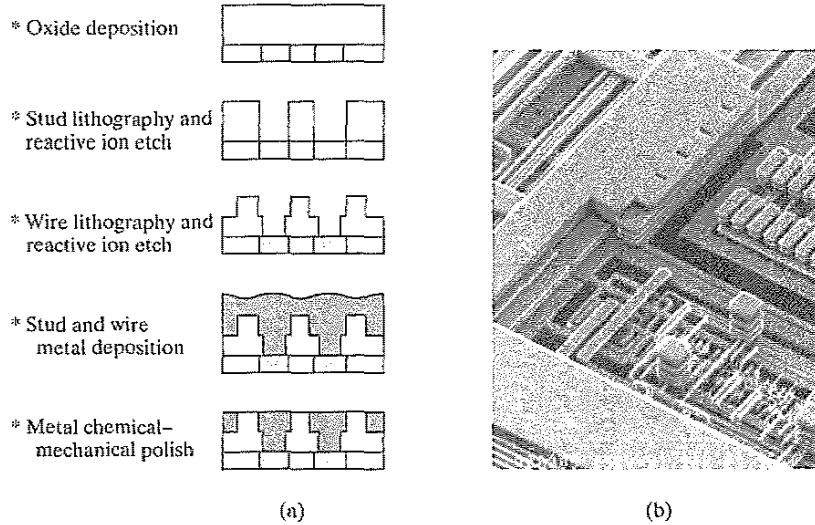
#### Silicon on Insulator


Although it has been around a long time, there seems to be a good chance that Silicon-on-Insulator (SOI) CMOS might replace the traditional CMOS process, described in the previous sections (also known as the *bulk CMOS process*). The main difference lies in the start material: the SOI transistors are constructed in a very thin layer of silicon, deposited on top of a thick layer of insulating  $\text{SiO}_2$  (see Figure 2-19). The primary advantages of the SOI process are reduced



**Dual damascene IC process**

**Figure 2-18** The damascene process (from [Geppert98]): process steps (a), and microphotograph of interconnect after removal of insulator (b).

parasitics and better transistor on-off characteristics. It has, for example, been demonstrated by researchers at IBM, that the porting of a design from a bulk CMOS to an SOI process—leaving all other design and process parameters such as channel length and oxide thickness identical—yields a performance improvement of 22% [Allen99]. Preparing a high quality SOI substrate at an economical cost was long the main hindrance against a large-scale introduction of the process. This picture had changed by the end of the 1990s, and SOI is steadily moving into the mainstream.

 

**Figure 2-19** Silicon-on-insulator process—schematic diagram (a) and SEM cross section (b). [Eaglesham99].


### 2.5.2 In the Longer Term

Extending the life of CMOS technology beyond the next decade, and going deeply below the 100 nm channel length region, however, will require redeveloping the process technology and the device structure. Already we are witnessing the emergence of a wide range of new devices (such as organic transistors, molecular switches, and quantum devices). While we cannot project what approaches will dominate in the next era, one interesting development is worth mentioning.

#### Truly Three-Dimensional Integrated Circuits

Getting signals in and out of the computation elements in a timely fashion is one of the main challenges presented by the continued increase in integration density. One way to address this problem is to introduce extra active layers, and to sandwich them between the metal interconnect layers, as shown in Figure 2-20. This enables us to position high density memory on top of the logic processors implemented in the bulk CMOS, reducing the distance between computation and storage, and thus also the delay [Souri00]. In addition, devices with different voltage, performance, or substrate material requirements can be placed in different layers. For instance, the top active layer can be reserved for the realization of optical transceivers, which may help to address the input/output requirements, or MEMS (Micro Electro-Mechanical Systems) devices providing sensing functions or radio frequency (RF) interfaces.

While this approach may seem to be promising, a number of major challenges and hindrances have to be resolved to make it truly viable. How to remove the dissipated heat is one of the more compelling questions, ensuring yield is another. Researchers are demonstrating major progress on these issues, and 3D integration might well be on the horizon. Before the true solution arrives, we might have to rely on some intermediate approaches. One alternative, called *2.5D integration*, is to bond two fully processed wafers, on which circuits are fabricated on the

 

**Figure 2-20** Example of true 3D integration. Extra active layers (T\*), implementing high-density memory and I/O, are sandwiched between the metal interconnect layers (M\*).

surface such that the chips completely overlap. Vias are etched to electrically connect both chips after metallization. The advantages of this technology lie in the similar electrical properties of devices on all active levels and the independence of processing temperature since all chips can be fabricated separately and later bonded. The major limitation of this technique is its lack of precision (best case alignment:  $\pm 2 \mu\text{m}$ ), which restricts the interchip communication to global metal lines.

One picture that strongly emerges from these futuristic devices is that the line between chip, substrate, package, and board is blurring. Designers of these *systems on a die* or *systems in a package* will have to consider all these aspects simultaneously.

## 2.6 Summary

This chapter has presented a bird's-eye view of the manufacturing and packaging process of CMOS integrated circuits:

- The manufacturing process of integrated circuits requires many steps, each of which consists of a sequence of basic operations. A number of these steps and/or operations, such as photolithographical exposure and development, material deposition, and etching, are executed very repetitively in the course of the manufacturing process.
- The *optical masks* forms the central interface between the intrinsics of the manufacturing process and the design that the user wants to see transferred to the silicon fabric.
- The *design-rules set* defines the constraints in terms of minimum width and separation that the IC design has to adhere to if the resulting circuit is to be fully functional. These design rules act as the contract between the circuit designer and the process engineer.
- The *package* forms the interface between the circuit implemented on the silicon die and the outside world, and as such has a major impact on the performance, reliability, longevity, and cost of the integrated circuit.

## 2.7 To Probe Further

Many books on semiconductor manufacturing have been published in the last few decades. An excellent overview of the state of the-art in CMOS manufacturing is *Silicon VLSI Technology* by J. Plummer, M. Deal, and P. Griffin [Plummer00]. A visual overview of the different steps in the manufacturing process can be found on the Web at [Fullman99]. Other sources for information are the IEEE Transactions on Electron Devices, and the Technical Digest of the IEDM conference. A number of great compendia are available for up-to-date and in-depth information about electronic packaging. [Doane93], [Harper00], and [Lau98] are good examples of such.

## References

- [Allen99] D. Allen, et al., "A 0.2  $\mu\text{m}$  1.8 V SOI 550 MHz PowerPC Microprocessor with Copper Interconnects," *Proceedings IEEE ISSCC Conference*, vol. XLII, pp. 438-439, February 1999.
- [Bakoglu90] H. Bakoglu, *Circuits, Interconnections and Packaging for VLSI*, Addison-Wesley, 1990.

- [Doane93] D. Doane, ed., *Multichip Module Technologies and Alternatives*, Van Nostrand-Reinhold, 1993.
- [Eaglesham 99] D. Eaglesham, "0.18  $\mu\text{m}$  CMOS and Beyond," *Proceedings 1999 Design Automation Conference*, pp. 703–708, June 1999.
- [Franzon93] P. Franzon, "Electrical Design of Digital Multichip Modules," in [Doane93], pp 525–568, 1993.
- [Fullman99] Fullman Kinetics, "The Semiconductor Manufacturing Process," <http://www.fullman-kinetics.com/semiconductors/semiconductors.html>, 1999.
- [Geppert98] L. Geppert, "Technology—1998 Analysis and Forecast," *IEEE Spectrum*, vol. 35, no. 1, p. 23, January 1998.
- [Harper00] C. Harper, Ed., *Electronic Packaging and Interconnection Handbook*, McGraw-Hill, 2000.
- [Landman71] B. Landman and R. Russo, "On a Pin versus Block Relationship for Partitions of Logic Graphs," *IEEE Trans. on Computers*, vol. C-20, pp. 1469–1479, December 1971.
- [Lau98] J. Lau et al., *Electronic Packaging—Design, Materials, Process, and Reliability*, McGraw-Hill, 1998.
- [Masaki92] A. Masaki, "Deep-Submicron CMOS Warms Up to High-Speed Logic," *Circuits and Devices Magazine*, November 1992.
- [Mead80] C. Mead and L. Conway, *Introduction to VLSI Systems*, Addison-Wesley, 1980.
- [Nagata92] M. Nagata, "Limitations, Innovations, and Challenges of Circuits and Devices into a Half Micrometer and Beyond," *IEEE Journal of Solid State Circuits*, vol. 27, no. 4, pp. 465–472, April 1992.
- [Plummer00] J. Plummer, M. Deal, and P. Griffin, *Silicon VLSI Technology*, Prentice Hall, 2000.
- [Steidel83] C. Steidel, *Assembly Techniques and Packaging*, in [Sze83], pp. 551–598, 1983.
- [Souri00] S. J. Souri, K. Banerjee, A. Mehrotra and K. C. Saraswat, "Multiple Si Layer ICs: Motivation, Performance Analysis, and Design Implications," *Proceedings 37th Design Automation Conference*, pp. 213–220, June 2000.



## DESIGN METHODOLOGY INSERT

A

### IC LAYOUT

*Creating a manufacturable layout*  
*Verifying the layout*

The increasing complexity of the integrated circuit has made the role of design-automation tools indispensable, and raises the abstractions the designer is working with to ever higher levels. Yet, when performance or design density is of primary importance, the designer has no other choice than to return to handcrafting the circuit topology and physical design. The labor-intensive nature of this approach, called *custom design*, translates into a high cost and a long time to market. Therefore, it can only be justified economically under the following conditions:

- The custom block can be reused many times, as a library cell, for instance.
- The cost can be amortized over a large volume. Microprocessors and semiconductor memories are examples of applications in this class.
- Cost is not among the prime design criteria.<sup>1</sup> Examples include space applications and scientific instrumentation.

With continuous progress in the design-automation arena, the share of custom design reduces from year to year. Even in high-performance microprocessors, large portions are

---


<sup>1</sup>This is becoming increasingly rare.

designed automatically using semicustom design approaches. Only the most performance-critical modules—such as the integer and floating-point execution units—are handcrafted.

Although the amount of design automation in the custom design process is minimal, some design tools have proven to be indispensable. Together with circuit simulators, these programs form the core of every design-automation environment, and they are the first tools an aspiring circuit designer will encounter.

### Layout Editor

The layout editor is the premier working tool of the designer and exists primarily for the generation of a physical representation of a design, given a circuit topology. Virtually every design-automation vendor offers an entry in this field. The most well known is the MAGIC tool developed at the University of California at Berkeley [Ousterhout84], which has been widely distributed. Even though MAGIC did not withstand the evolution of software technology and user interface, some of its offspring did. Throughout this book, we will be using a layout tool called **max**, a MAGIC descendant developed by a company called MicroMagic [mmi00]. A typical **max** display is shown in Figure A-1 and illustrates the basic function of the layout editor—placing polygons on

 

**Figure A-1** View of a **max** display window. It plots the layout of two stacked NMOS transistor. The menu on the left side allows for the selection of the layer a particular polygon will be placed on.


different mask layers so that a functional physical design is obtained (scathingly called *polygon pushing*).

### Symbolic Layout

Since physical design occupies a major fraction of the design time for a new cell or component, techniques to expedite this process have been in continual demand. The *symbolic-layout* approach has gained popularity over the years. In this design methodology, the designer only draws a shorthand notation for the layout structure. This notation indicates only the *relative* positioning of the various design components (transistors, contacts, wires). The *absolute* coordinates of these elements are determined automatically by the editor using a *compactor* [Hsueh79, Weste93]. The compactor translates the design rules into a set of constraints on the component positions, and solves a constrained optimization problem that attempts to minimize the area or another cost function.

An example of a symbolic notation for a circuit topology called a *sticks diagram* is shown in Figure A-2. The different layout entities are dimensionless, since only positioning is important. The advantage of this approach is that the designer does not have to worry about design rules, because the compactor ensures that the final layout is physically correct. Thus, she can avoid cumbersome polygon manipulations. Another plus of the symbolic approach is that cells can adjust themselves automatically to the environment. For example, automatic pitch matching of cells is an attractive feature in module generators. Consider the case of Figure A-3 (from [Croes88]), in which the original cells have different heights, and the terminal positions do not match. Connecting the cells would require extra wiring. The symbolic approach allows the cells to adjust themselves and connect without any overhead.

The disadvantage of the symbolic approach is that the outcome of the compaction phase often is unpredictable. The resulting layout can be less dense than what is obtained with the manual approach. This has prevented it from becoming a mainstream layout tool. Nonetheless, symbolic layout techniques have improved considerably over the years, and they have become very useful as a first-order drafting tool for new cells. More important, they form the solid underpinning of the automatic cell-generation techniques, described later, in Chapter 8.

 

**Figure A-2** Sticks representation of CMOS inverter. The numbers represent the (*Width/Length*)-ratios of the transistors.



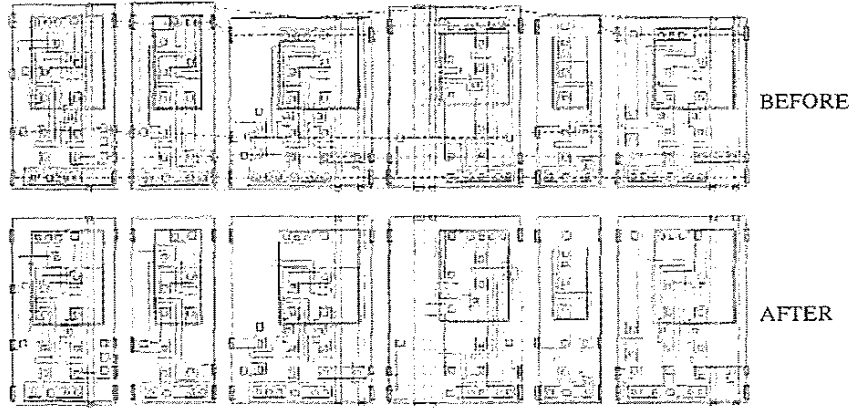


Figure A-3 Automatic pitch matching of data path cells based on symbolic layout.


### Design-Rule Checking

Design rules were introduced in Chapter 2 as a set of layout restrictions that ensure the manufactured design will operate as desired with no short or open circuits. A prime requirement of the physical layout of a design is that it adhere to these rules. This can be verified with the aid of a *design-rule checker (DRC)*, which uses as inputs the physical layout of a design and a description of the design rules presented in the form of a *technology file*. Since a complex circuit can contain millions of polygons that must be checked against each other, efficiency is the most important property of a good DRC tool. The verification of a large chip can take hours or days of computation time. One way of expediting the process is to preserve the design hierarchy at the physical level. For example, if a cell is used multiple times in a design, it should be checked only once. Besides speeding up the process, the use of hierarchy can make error messages more informative by retaining knowledge of the circuit structure.

DRC tools come in two formats: (1) The *on-line DRC* runs concurrent with the layout editor and flags design violations during the cell layout. For instance, **max** has a built-in design-rule checking facility. An example of on-line DRC is shown in Figure A-4. (2) *Batch DRC* is used as a postdesign verifier; it is run on a complete chip prior to shipping the mask descriptions to the manufacturer.

### Circuit Extraction

Another important tool in the custom-design methodology is the circuit extractor, which derives a circuit schematic from a physical layout. By scanning the various layers and their interactions, the extractor reconstructs the transistor network, including the sizes of the devices and the interconnections. The schematic produced can be used to verify that the artwork implements the intended function. Furthermore, the resulting circuit diagram contains precise information on the parasitics, such as the diffusion and wiring capacitances and resistances. This allows for a

 

**Figure A-4** On-line design rule checking. The white dots indicate a design rule violation. The violated rule can be obtained with a simple mouse click.

more accurate simulation and analysis. The complexity of the extraction depends greatly upon the desired information. Most extractors extract the transistor network and the capacitances of the interconnect with respect to *GND* or other network nodes. Extraction of the wiring resistances already comes at a greater cost, yet it has become a necessity for virtually all high-performance circuits. Clever algorithms have helped to reduce the complexity of the resulting circuit diagrams. For very high-speed circuits, extraction of the inductance would be desirable as well. Unfortunately, this requires a three-dimensional analysis and is only feasible for small-sized circuits at present.

### A.1 To Probe Further

More detailed information regarding the *MAGIC* and *max* layout editors can be found on the web site of this book. In-depth textbooks on layout generation and verification have been published, and can be of great help to the novice designer. To mention a few of them, [Clein00], [Uyemura95], and [Wolf94] offer some comprehensive and well-illustrated treatment and discussion.

### References

- [Clein00] D. Clein, *CMOS IC Layout—Concepts, Methodologies, and Tools*, Newnes, 2000.
- [Croes88] K. Croes, H. De Man, and P. Six, "CAMELEON: A Process-Tolerant Symbolic Layout System," *Journal of Solid State Circuits*, vol. 23 no. 3, pp. 705–713, June 1988.
- [Hsueh79] M. Hsueh and D. Pederson, "Computer-Aided Layout of LSI Building Blocks," *Proceedings ISCAS Conf.*, pp. 474–477, Tokyo, 1979.
- [mmi00] MicroMagic, Inc, <http://www.micromagic.com>.

- [Ousterhout84] J. Ousterhout, G. Hamachi, R. Mayo, W. Scott, and G. Taylor, "Magic: A VLSI Layout System," *Proc. 21st Design Automation Conference*, pp. 152–159, 1984.
- [Uyemura95] J. Uyemura, *Physical Design of CMOS Integrated Circuits Using L-EDIT*, PWS Publishing Company, 1995.
- [Weste93] N. Weste and K. Eshraghian, *Principles of CMOS VLSI Design—A Systems Perspective*, Addison-Wesley, 1993.
- [Wolf94] W. Wolf, *Modern VLSI Design—A Systems Approach*, Prentice Hall, 1994.

## CHAPTER

# 5

## The CMOS Inverter

*Quantification of integrity, performance, and energy metrics of an inverter  
Optimization of an inverter design*

- 5.1 Introduction
- 5.2 The Static CMOS Inverter—An Intuitive Perspective
- 5.3 Evaluating the Robustness of the CMOS Inverter—The Static Behavior
  - 5.3.1 Switching Threshold
  - 5.3.2 Noise Margins
  - 5.3.3 Robustness Revisited
- 5.4 Performance of CMOS Inverter: The Dynamic Behavior
  - 5.4.1 Computing the Capacitances
  - 5.4.2 Propagation Delay: First-Order Analysis
  - 5.4.3 Propagation Delay from a Design Perspective
- 5.5 Power, Energy, and Energy Delay
  - 5.5.1 Dynamic Power Consumption
  - 5.5.2 Static Consumption
  - 5.5.3 Putting It All Together
  - 5.5.4 Analyzing Power Consumption by Using SPICE
- 5.6 Perspective: Technology Scaling and its Impact on the Inverter Metrics
- 5.7 Summary
- 5.8 To Probe Further

## 5.1 Introduction

The inverter is truly the nucleus of all digital designs. Once its operation and properties are clearly understood, designing more intricate structures such as logic gates, adders, multipliers, and microprocessors is greatly simplified. The electrical behavior of these complex circuits can be almost completely derived by extrapolating the results obtained for inverters. The analysis of inverters can be extended to explain the behavior of more complex gates such as NAND, NOR, or XOR, which in turn form the building blocks for modules such as multipliers and processors.

In this chapter, we focus on a single incarnation of the inverter gate—the static CMOS inverter. This is certainly the most popular inverter at present, and therefore deserves special attention. We analyze the gate with respect to the different design metrics that were outlined in Chapter 1:

- *cost*, expressed by the complexity and area
- *integrity and robustness*, expressed by the static (or steady-state) behavior
- *performance*, determined by the dynamic (or transient) response
- *energy efficiency*, set by the energy and power consumption

Using this analysis, we develop a model of the gate and identify its design parameters. We develop methods to choose the parameter values so that the resulting design meets the desired specifications. While each of these parameters can easily be quantified for a given technology, we also discuss how they are affected by *scaling of the technology*.

While the chapter focuses uniquely on the CMOS inverter, in the next chapter, we see that the same methodology also applies to other gate topologies.

## 5.2 The Static CMOS Inverter—An Intuitive Perspective

Figure 5-1 shows the circuit diagram of a static CMOS inverter. Its operation is readily understood with the aid of the simple switch model of the MOS transistor that we introduced in Chapter 3 (see Figure 3-26). The transistor is nothing more than a switch with an infinite off-

 


Figure 5-1 Static CMOS inverter.  $V_{DD}$  stands for the supply voltage.

 


Figure 5-2 Switch models of CMOS inverter.

resistance (for  $|V_{GS}| < |V_T|$ ) and a finite on-resistance (for  $|V_{GS}| > |V_T|$ ). This leads to the following interpretation of the inverter. When  $V_{in}$  is high and equal to  $V_{DD}$ , the NMOS transistor is on and the PMOS is off. This yields the equivalent circuit of Figure 5-2a. A direct path exists between  $V_{out}$  and the ground node, resulting in a steady-state value of 0 V. On the other hand, when the input voltage is low (0 V), NMOS and PMOS transistors are off and on, respectively. The equivalent circuit of Figure 5-2b shows that a path exists between  $V_{DD}$  and  $V_{out}$ , yielding a high output voltage. The gate clearly functions as an inverter.

A number of other important properties of static CMOS can be derived from this switch level view:

- The high and low output levels equal  $V_{DD}$  and  $GND$ , respectively; in other words, the voltage swing is equal to the supply voltage. This results in high noise margins.
- The logic levels are not dependent upon the relative device sizes, so that the transistors can be minimum size. Gates with this property are called *ratioless*. This is in contrast with *ratioed logic*, where logic levels are determined by the relative dimensions of the composing transistors.
- In steady state, there always exists a path with finite resistance between the output and either  $V_{DD}$  or  $GND$ . A well-designed CMOS inverter, therefore, has a *low output impedance*, which makes it less sensitive to noise and disturbances. Typical values of the output resistance are in  $k\Omega$  range.
- The *input resistance* of the CMOS inverter is extremely high, as the gate of an MOS transistor is a virtually perfect insulator and draws no dc input current. Since the input node of the inverter only connects to transistor gates, the steady-state input current is nearly zero. A single inverter can theoretically drive an infinite number of gates (or have an infinite fan-out) and still be functionally operational; however, increasing the fan-out also increases the propagation delay, as will become clear shortly. Although fan-out does not have any effect on the steady-state behavior, it degrades the transient response.


- No direct path exists between the supply and ground rails under steady-state operating conditions (i.e., when the input and outputs remain constant). The absence of current flow (ignoring leakage currents) means that the gate does not consume any static power.

**SIDELINE:** The preceding observation, while seemingly obvious, is of crucial importance, and is one of the primary reasons CMOS is the digital technology of choice at present. The situation was very different in the 1970s and early 1980s. All early microprocessors—such as the Intel 4004—were implemented in a pure NMOS technology. The lack of complementary devices (such as the NMOS and PMOS transistor) in such a technology makes the realization of inverters with zero static power nontrivial. The resulting static power consumption puts a firm upper bound on the number of gates that can be integrated on a single die; hence, the forced move to CMOS in the 1980s, when scaling of the technology allowed for higher integration densities.


The nature and the form of the voltage-transfer characteristic (VTC) can be graphically deduced by superimposing the current characteristics of the NMOS and the PMOS devices. Such a graphical construction is traditionally called a *load-line plot*. It requires that the  $I$ - $V$  curves of the NMOS and PMOS devices are transformed onto a common coordinate set. We have selected the input voltage  $V_{in}$ , the output voltage  $V_{out}$  and the NMOS drain current  $I_{DN}$  as the variables of choice. The PMOS  $I$ - $V$  relations can be translated into this variable space by the following relations (the subscripts  $n$  and  $p$  denote the NMOS and PMOS devices, respectively):

$$\begin{aligned}
 I_{DSp} &= -I_{DSn} \\
 V_{GSn} &= V_{in}; \quad V_{GSp} = V_{in} - V_{DD} \\
 V_{DSn} &= V_{out}; \quad V_{DSp} = V_{out} - V_{DD}
 \end{aligned}
 \tag{5.1}$$

The load-line curves of the PMOS device are obtained by a mirroring around the  $x$ -axis and a horizontal shift over  $V_{DD}$ . This procedure is outlined in Figure 5-3, where the subsequent steps to adjust the original PMOS  $I$ - $V$  curves to the common coordinate set  $V_{in}$ ,  $V_{out}$ , and  $I_{DN}$  are illustrated.

 


**Figure 5-3** Transforming PMOS  $I$ - $V$  characteristic to a common coordinate set (assuming  $V_{DD} = 2.5$  V).

 

**Figure 5-4** Load curves for NMOS and PMOS transistors of the static CMOS inverter ( $V_{DD} = 2.5$  V). The dots represent the dc operation points for various input voltages.

The resulting load lines are plotted in Figure 5-4. For a dc operating point to be valid, the currents through the NMOS and PMOS devices must be equal. Graphically, this means that the dc points must be located at the intersection of corresponding load lines. A number of those points (for  $V_{in} = 0, 0.5, 1, 1.5, 2,$  and  $2.5$  V) are marked on the graph. As can be seen, all operating points are located either at the high or low output levels. The VTC of the inverter thus exhibits a very narrow transition zone. This results from the high gain during the switching transient, when both NMOS and PMOS are simultaneously on and in saturation. In that operation region, a small change in the input voltage results in a large output variation. All these observations translate into the VTC shown in Figure 5-5.

 

**Figure 5-5** VTC of static CMOS inverter, derived from Figure 5-4 ( $V_{DD} = 2.5$  V). For each operation region, the modes of the transistors are annotated—off, res(istive), or sat(urated).



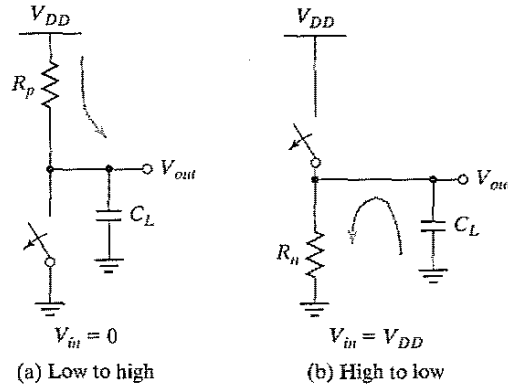


Figure 5-6 Switch model of dynamic behavior of static CMOS inverter.

Before going into the analytical details of the operation of the CMOS inverter, a qualitative analysis of the transient behavior of the gate is appropriate. This response is dominated mainly by the output capacitance of the gate,  $C_L$ , which is composed of the drain diffusion capacitances of the NMOS and PMOS transistors, the capacitance of the connecting wires, and the input capacitance of the fan-out gates. Assuming temporarily that the transistors switch instantaneously, we can get an approximate idea of the transient response by using the simplified switch model again. Let us first consider the low-to-high transition (see Figure 5-6a). The gate response time is simply determined by the time it takes to charge the capacitor  $C_L$  through the resistor  $R_p$ . In Example 4.5, we learned that the propagation delay of such a network is proportional to the time constant  $R_p C_L$ . Hence, a fast gate is built either by keeping the output capacitance small or by decreasing the on-resistance of the transistor. The latter is achieved by increasing the  $W/L$  ratio of the device. Similar considerations are valid for the high-to-low transition (Figure 5-6b), which is dominated by the  $R_n C_L$  time constant. The reader should be aware that the on-resistance of the NMOS and PMOS transistor is not constant; rather, it is a nonlinear function of the voltage across the transistor. This complicates the exact determination of the propagation delay. (An in-depth analysis of how to analyze and optimize the performance of the static CMOS inverter is offered in Section 5.4.)

### 5.3 Evaluating the Robustness of the CMOS Inverter—The Static Behavior

In the preceding qualitative discussion, the overall shape of the voltage-transfer characteristic of the static CMOS inverter was sketched, and the values of  $V_{OH}$  and  $V_{OL}$ —which are evaluated to  $V_{DD}$  and  $GND$ , respectively—were derived. It remains to determine the precise values of  $V_M$ ,  $V_{IH}$ , and  $V_{IL}$ , as well as the noise margins.

### 5.3.1 Switching Threshold

The switching threshold  $V_M$  is defined as the point where  $V_{in} = V_{out}$ . Its value can be obtained graphically from the intersection of the VTC with the line given by  $V_{in} = V_{out}$  (see Figure 5-5). In this region, both PMOS and NMOS are always saturated, since  $V_{DS} = V_{GS}$ . An analytical expression for  $V_M$  is obtained by equating the currents through the transistors. We solve for the case in which the supply voltage is high enough so that the devices can be assumed to be velocity-saturated (or  $V_{DSAT} < V_M - V_T$ ). Furthermore, we ignore the channel length modulation effects. We have

$$k_n V_{DSATn} \left( V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) + k_p V_{DSATp} \left( V_M - V_{DD} - V_{Tp} \frac{V_{DSATp}}{2} \right) = 0 \quad (5.2)$$

Solving for  $V_M$  yields

$$V_M = \frac{\left( V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left( V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r} \quad \text{with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{\mu_{satp} W_p}{\mu_{satn} W_n} \quad (5.3)$$

assuming identical oxide thicknesses for PMOS and NMOS transistors. For large values of  $V_{DD}$  (compared with threshold and saturation voltages), Eq. (5.3) can be simplified:

$$V_M \approx \frac{r V_{DD}}{1 + r} \quad (5.4)$$

Equation (5.4) states that the switching threshold is set by the ratio  $r$ , which compares the relative driving strengths of the PMOS and NMOS transistors. It is generally desirable for  $V_M$  to be located around the middle of the available voltage swing (or at  $V_{DD}/2$ ), since this results in comparable values for the low and high noise margins. This requires  $r$  to be approximately 1, which is equivalent to sizing the PMOS device so that  $(W/L)_p = (W/L)_n \times (V_{DSATn} k'_n) / (V_{DSATp} k'_p)$ . To move  $V_M$  upwards, a larger value of  $r$  is required, which means making the PMOS wider. Increasing the strength of the NMOS, on the other hand, moves the switching threshold closer to GND.

From Eq. (5.2), we derive the required ratio of PMOS to NMOS transistor sizes such that the switching threshold is set to a desired value  $V_M$ :

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)} \quad (5.5)$$

When using this expression, make sure that the assumption that both devices are velocity saturated still holds for the chosen operation point.

---

#### Problem 5.1 Inverter Switching Threshold for Long-Channel Devices, or Low-Supply Voltages

The preceding expressions were derived under the assumption that the transistors are velocity saturated. When the PMOS and NMOS are long-channel devices, or when the supply voltage is low,

velocity saturation does not occur ( $V_M - V_T < V_{DSAT}$ ). Under these circumstances, the following equation holds for  $V_M$ :

$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r} \quad \text{with } r = \sqrt{\frac{-k_p}{k_n}} \quad (5.6)$$

Derive this equation.

#### Design Technique—Maximizing the Noise Margins

When designing static CMOS circuits, it is advisable to balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section if maximizing the noise margins and obtaining symmetrical characteristics are desired. The required ratio is given by Eq. (5.5). ■

#### Example 5.1 Switching Threshold of CMOS Inverter

We derive the sizes of PMOS and NMOS transistors such that the switching threshold of a CMOS inverter, implemented in our generic 0.25  $\mu\text{m}$  CMOS process, is located in the middle between the supply rails. We use the process parameters presented in Example 3.7, and assume a supply voltage of 2.5 V. The minimum size device has a width-to-length ratio of 1.5. With the aid of Eq. (5.5), we find that

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{30 \times 10^{-6}} \times \frac{0.63}{1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$

Figure 5-7 plots the values of switching threshold as a function of the PMOS-to-NMOS ratio, as obtained by circuit simulation. The simulated PMOS-to-NMOS ratio of 3.4 for a 1.25-V switching threshold confirms the value predicted by Eq. (5.5).


 


Figure 5-7 Simulated inverter switching threshold versus PMOS-to-NMOS ratio (0.25- $\mu\text{m}$  CMOS,  $V_{DD} = 2.5$  V).

An analysis of the curve of Figure 5-7 leads to some interesting observations:

1.  $V_M$  is relatively insensitive to variations in the device ratio. This means that small variations of the ratio (e.g., making it 3 or 2.5) do not disturb the transfer characteristic that much. It is therefore an accepted practice in industrial designs to set the width of the PMOS transistor to values smaller than those required for exact symmetry. For the preceding example, setting the ratio to 3, 2.5, and 2 yields switching thresholds of 1.22 V, 1.18 V, and 1.13 V, respectively.
2. The effect of changing the  $W_p$ -to- $W_n$  ratio is to shift the transient region of the VTC. Increasing the width of the PMOS or the NMOS moves  $V_M$  toward  $V_{DD}$  or  $GND$ , respectively. This property can be very useful, as asymmetrical transfer characteristics are actually desirable in some designs. This is demonstrated by the example of Figure 5-8. The incoming signal  $V_{in}$  has a very noisy zero value. Passing this signal through a symmetrical inverter would lead to erroneous values (Figure 5-8a). This can be addressed by raising the threshold of the inverter, which results in a correct response (Figure 5-8b). Later in the text we will see other circuit instances in which inverters with asymmetrical switching thresholds are desirable. Changing the switching threshold by a considerable amount, however, is not easy, especially when the ratio of supply voltage to transistor threshold is relatively small ( $2.5/0.4 = 6$ , for our particular example). To move the threshold to 1.5 V requires a transistor ratio of 11, and further increases are prohibitively expensive. Observe that Figure 5-7 is plotted in a semilog format.

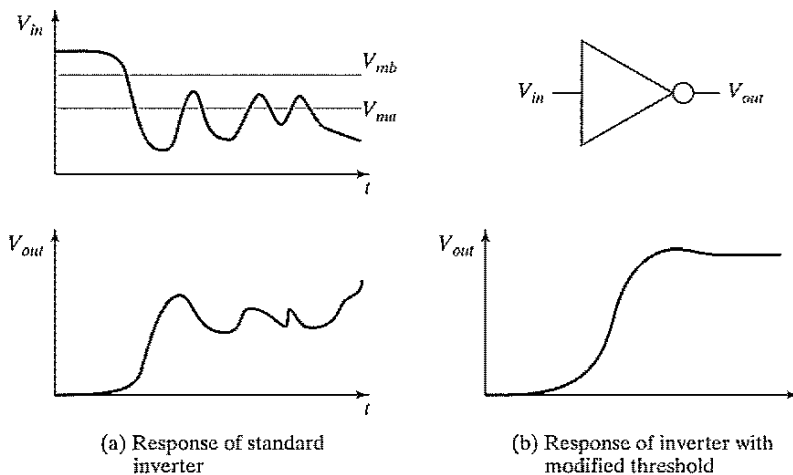

**Figure 5-8** Changing the inverter threshold can improve the circuit reliability.

### 5.3.2 Noise Margins


By definition,  $V_{IH}$  and  $V_{IL}$  are the operational points of the inverter where  $\frac{dV_{out}}{dV_{in}} = -1$ . In the terminology of the analog circuit designer, these are the points where the gain  $g$  of the amplifier, formed by the inverter, is equal to  $-1$ . While it is indeed possible to derive analytical expressions for  $V_{IH}$  and  $V_{IL}$ , these tend to be unwieldy and provide little insight in what parameters are instrumental in setting the noise margins.

A simpler approach is to use a piece-wise linear approximation for the VTC, as shown in Figure 5-9. The transition region is approximated by a straight line, the gain of which equals the gain  $g$  at the switching threshold  $V_M$ . The crossover with the  $V_{OH}$  and the  $V_{OL}$  lines is used to define  $V_{IH}$  and  $V_{IL}$  points. The error introduced is small and well within the range of what is required for an initial design. This approach yields the following expressions for the width of the transition region  $V_{IH} - V_{IL}$ ,  $V_{IH}$ ,  $V_{IL}$ , and the noise margins  $NM_H$  and  $NM_L$ :

$$\begin{aligned} V_{IH} - V_{IL} &= -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g} \\ V_{IH} &= V_M - \frac{V_M}{g} & V_{IL} &= V_M + \frac{V_{DD} - V_M}{g} \\ NM_H &= V_{DD} - V_{IH} & NM_L &= V_{IL} \end{aligned} \quad (5.7)$$

These expressions make it increasingly clear that a high gain in the transition region is very desirable. In the extreme case of an infinite gain, the noise margins simplify to  $V_{OH} - V_M$  and  $V_M - V_{OL}$  for  $NM_H$  and  $NM_L$ , respectively, and span the complete voltage swing.

It remains for us to determine the midpoint gain of the static CMOS inverter. We assume once again that both PMOS and NMOS are velocity saturated. It is apparent from Figure 5-4 that the gain is a strong function of the slopes of the currents in the saturation region. The channel-

 

**Figure 5-9** A piecewise linear approximation of the VTC simplifies the derivation of  $V_{IL}$  and  $V_{IH}$ .

length modulation factor therefore cannot be ignored in this analysis—doing so would lead to an infinite gain. The gain can now be derived by differentiating the current Eq. (5.8), which is valid around the switching threshold, with respect to  $V_{in}$ :

$$\begin{aligned} k_n V_{DSATn} \left( V_{in} - V_{Tn} - \frac{V_{DSATn}}{2} \right) (1 + \lambda_n V_{out}) + \\ k_p V_{DSATp} \left( V_{in} - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) (1 + \lambda_p V_{out} - \lambda_p V_{DD}) = 0 \end{aligned} \quad (5.8)$$

Differentiating and solving for  $dV_{out}/dV_{in}$ , yields

$$\frac{dV_{out}}{dV_{in}} = \frac{k_n V_{DSATn} (1 + \lambda_n V_{out}) + k_p V_{DSATp} (1 + \lambda_p V_{out} - \lambda_p V_{DD})}{\lambda_n k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn}/2) + \lambda_p k_p V_{DSATp} (V_{in} - V_{DD} - V_{Tp} - V_{DSATp}/2)} \quad (5.9)$$

Ignoring some second-order terms and setting  $V_{in} = V_M$  produces the gain expression,

$$\begin{aligned} g &= \frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p} \\ &\approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)} \end{aligned} \quad (5.10)$$

with  $I_D(V_M)$  the current flowing through the inverter for  $V_{in} = V_M$ . The gain is almost purely determined by technology parameters, especially the channel-length modulation. It can only be influenced in a minor way by the designer through the choice of the supply voltage and the transistor sizes.

### Example 5.2 Voltage Transfer Characteristic and Noise Margins of CMOS Inverter

Assume an inverter in the generic 0.25- $\mu\text{m}$  CMOS technology designed with a PMOS-to-NMOS ratio of 3.4 and with the NMOS transistor minimum size ( $W = 0.375 \mu\text{m}$ ,  $L = 0.25 \mu\text{m}$ ,  $W/L = 1.5$ ). We first compute the gain at  $V_M (= 1.25 \text{ V})$ :

$$I_D(V_M) = 1.5 \times 115 \times 10^{-6} \times 0.63 \times (1.25 - 0.43 - 0.63/2) \times (1 + 0.06 \times 1.25) = 59 \times 10^{-6} \text{ A}$$

$$g = \frac{1}{59 \times 10^{-6}} \frac{1.5 \times 115 \times 10^{-6} \times 0.63 + 1.5 \times 3.4 \times 30 \times 10^{-6} \times 1.0}{0.06 + 0.1} = -27.5 \text{ (Eq. 5.10a)}$$


This yields the following values for  $V_{IL}$ ,  $V_{IH}$ ,  $NM_L$ ,  $NM_H$ :

$$V_{IL} = 1.2 \text{ V}, V_{IH} = 1.3 \text{ V}, NM_L = NM_H = 1.2$$

Figure 5-10 plots the simulated VTC of the inverter, as well as its derivative, the gain. A close to ideal characteristic is obtained. The actual values of  $V_{IL}$  and  $V_{IH}$  are 1.03 V and 1.45 V, respectively, which leads to noise margins of 1.03 V and 1.05 V. These values are lower than those predicted, for two reasons:

- Eq. (5.10) overestimates the gain. As observed in Figure 5-10b, the maximum gain (at  $V_M$ ) equals only 17. This reduced gain would yield values for  $V_{IL}$  and  $V_{IH}$  of 1.17 V, and 1.33 V, respectively<sup>1</sup>.
- The most important deviation is due to the piecewise linear approximation of the VTC, which is optimistic with respect to the actual noise margins. The expressions obtained are, however, perfectly useful as first-order estimations, as well as means of identifying the relevant parameters and their impact.

To conclude this example, we also extracted from simulations the output resistance of the inverter in the low- and high-output states. Low values of 2.4 k $\Omega$  and 3.3 k $\Omega$ , respectively, were observed. The output resistance is a good measure of the sensitivity of the gate with respect to noise induced at the output, and is preferably as low as possible.

 

**Figure 5-10** Simulated Voltage Transfer Characteristic (a) and voltage gain (b) of CMOS inverter (0.25- $\mu$ m CMOS,  $V_{DD} = 2.5$  V).

**SIDELINE:** Surprisingly (or perhaps not so surprisingly), the static CMOS inverter can also be used as an analog amplifier, as it has a fairly high gain in its transition region. This region is very narrow, however, as is apparent in the graph of Figure 5-10b. It also receives poor marks on other amplifier properties such as supply noise rejection. Still, this observation can be used to demonstrate one of the major differences between analog and digital design. Where the analog designer would bias the amplifier in the middle of the transient region so that a maximum linearity is obtained, the digital designer will operate the device in the regions of extreme nonlinearity, resulting in well-defined and well-separated high and low signals.


<sup>1</sup>In addition, Eq. (5.10) is not entirely valid for this particular example. The attentive reader will observe that for the operating conditions at hand, the PMOS operates in saturation mode, not velocity saturation. The impact on the result is minor, however.

**Problem 5.2 Inverter Noise Margins for Long-Channel Devices**

Derive expressions for the gain and noise margins assuming that PMOS and NMOS are long-channel devices (or that the supply voltage is low), so that velocity saturation does not occur.

**5.3.3 Robustness Revisited****Device Variations**

While we design a gate for nominal operation conditions and typical device parameters, we should always be aware that the actual operating temperature might vary over a large range, and that the device parameters after fabrication probably will deviate from the nominal values we used in our design optimization process. Fortunately, the dc characteristics of the static CMOS inverter turn out to be rather insensitive to these variations, and the gate remains functional over a wide range of operating conditions. This already became apparent in Figure 5-7, which shows that variations in the device sizes have only a minor impact on the switching threshold of the inverter. To further confirm the assumed robustness of the gate, we have resimulated the voltage transfer characteristic by replacing the nominal devices by their worst or best case incarnations. Two corner cases are plotted in Figure 5-11: a better-than-expected NMOS, combined with an inferior PMOS, and the opposite scenario. Comparing the resulting curves with the nominal response shows that the operation of the gate is by no means affected, and that the variations mainly cause a shift in the switching threshold. This robust behavior, which ensures functionality of the gate over a wide range of conditions, has contributed in a big way to the popularity of the static CMOS gate.

 

**Figure 5-11** Impact of device variations on static CMOS inverter VTC. The “good” device has a smaller oxide thickness (– 3 nm), a smaller length (– 25 nm), a higher width (+ 30 nm), and a smaller threshold (– 60 mV). The opposite is true for the “bad” transistor.



### Scaling the Supply Voltage

In Chapter 3, we observed that continuing technology scaling forces the supply voltages to reduce at rates similar to the device dimensions. At the same time, device threshold voltages are virtually kept constant. You may wonder about the impact of this trend on the integrity parameters of the CMOS inverter. Do inverters keep on working when the voltages are scaled, and are there potential limits to the supply scaling?

A first hint on what might happen was offered in Eq. (5.10), which indicates that the gain of the inverter in the transition region actually increases with a reduction of the supply voltage! Note that for a fixed transistor ratio  $r$ ,  $V_M$  is approximately proportional to  $V_{DD}$ . Plotting the (normalized) VTC for different supply voltages not only confirms this conjecture, but even shows that the inverter is well and alive for supply voltages close to the threshold voltage of the composing transistors (see Figure 5-12a). At a voltage of 0.5 V—which is just 100 mV above the threshold of the transistors—the width of the transition region measures only 10% of the supply voltage (for a maximum gain of 35), while it widens to 17% for 2.5 V. So, given this improvement in dc characteristics, why do we not choose to operate all of our digital circuits at these low supply voltages? Three important reasons come to mind:

- Reducing the supply voltage indiscriminately has a positive impact on the energy dissipation, but is absolutely detrimental to the delay of the gate, as we will learn in the next sections.
- The dc characteristic becomes increasingly sensitive to variations in the device parameters, such as the transistor threshold, once supply voltages and intrinsic voltages become comparable.
- Scaling the supply voltage means reducing the signal swing. While this typically helps to reduce the internal noise in the system (such as caused by crosstalk), it makes the design more sensitive to external noise sources that do not scale.

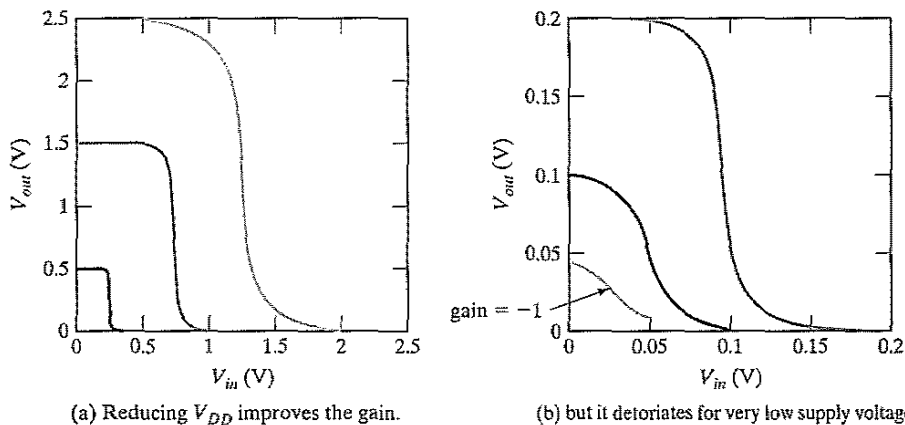


Figure 5-12 VTC of CMOS inverter as a function of supply voltage (0.25- $\mu\text{m}$  CMOS technology).

To provide an insight into the question on potential limits to the voltage scaling, we have plotted the voltage transfer characteristic of the same inverter for the even lower supply voltages of 200 mV, 100 mV, and 50 mV in Figure 5-12b. The transistor thresholds are kept at the same level. Amazingly enough, we still obtain an inverter characteristic, even though the supply voltage is not large enough to turn the transistors on! The explanation can be found in the subthreshold operation of the transistors. The subthreshold currents are sufficient to switch the gate between low and high levels, as well as to provide enough gain to produce acceptable VTCs. The low value of the switching currents ensures a very slow operation, but this might be acceptable for some applications (such as watches, for example).

At around 100 mV, we start observing a major deterioration of the gate characteristic.  $V_{OL}$  and  $V_{OH}$  are no longer at the supply rails and the transition region gain approaches 1. The latter turns out to be a fundamental showstopper. To achieve sufficient gain for use in a digital circuit, it is necessary that the supply be at least two times  $\phi_T = kT/q$  ( $= 25$  mV at room temperature), the thermal voltage introduced in Chapter 3 [Swanson72]. It turns out that below this same voltage, thermal noise becomes an issue as well, potentially resulting in unreliable operation. We express this relation as

$$V_{DDmin} > 2 \dots 4 \frac{kT}{q} \quad (5.11)$$

Equation (5.11) presents a true lower bound on supply scaling. It suggests that the only way to get CMOS inverters to operate below 100 mV is to reduce the ambient temperature—or in other words, to cool the circuit.

---

#### Problem 5.3 Minimum Supply Voltage of CMOS Inverter

Once the supply voltage drops below the threshold voltage, the transistors operate in the subthreshold region, and display an exponential current–voltage relationship (as expressed in Eq. (3.39)). Derive an expression for the gain of the inverter under these circumstances (assume symmetrical NMOS and PMOS transistors, and a maximum gain at  $V_M = V_{DD}/2$ ). The resulting expression demonstrates that the minimum voltage is a function of the slope factor  $n$  of the transistor:

$$g = - \left( \frac{1}{n} \right) \left( e^{V_{DD}/2\phi_T} - 1 \right) \quad (5.12)$$

According to this expression, the gain drops to  $-1$  at  $V_{DD} = 48$  mV (for  $n = 1.5$  and  $\phi_T = 25$  mV).

---

#### 5.4 Performance of CMOS Inverter: The Dynamic Behavior

The qualitative analysis presented earlier concluded that the propagation delay of the CMOS inverter is determined by the time it takes to charge and discharge the load capacitor  $C_L$  through the PMOS and NMOS transistors, respectively. This observation suggests that **getting  $C_L$  as small as possible is crucial to the realization of high-performance CMOS circuits.** It is thus

worthwhile to first study the major components of the load capacitance before embarking on an in-depth analysis of the propagation delay of the gate. In addition to this detailed analysis, this section also presents a summary of techniques that a designer might use to optimize the performance of the inverter.

### 5.4.1 Computing the Capacitances


Manual analysis of MOS circuits where each capacitor is considered individually is virtually impossible. The problem is exacerbated by the many nonlinear capacitances in the MOS transistor model. To make the analysis tractable, we assume that all capacitances are lumped together into one single capacitor  $C_L$ , located between  $V_{out}$  and  $GND$ . Be aware that this is a considerable simplification of the actual situation, even in the case of a simple inverter.

Figure 5-13 shows the schematic of a cascaded inverter pair. It includes all the capacitances influencing the transient response of node  $V_{out}$ . It is initially assumed that the input  $V_{in}$  is driven by an *ideal voltage source with zero rise and fall times*. Accounting only for capacitances connected to the output node,  $C_L$  breaks down into the following components.


#### Gate-Drain Capacitance $C_{gd12}$

$M_1$  and  $M_2$  are either in cut-off or in the saturation mode during the first half (up to 50% point) of the output transient. Under these circumstances, the only contributions to  $C_{gd12}$  are the overlap capacitances of both  $M_1$  and  $M_2$ . The channel capacitance of the MOS transistors does not play a role here, as it is located either completely between gate and bulk (cut-off) or gate and source (saturation) (see Chapter 3).

The lumped capacitor model now requires that this floating gate-drain capacitor be replaced by a capacitance to ground. This is accomplished by taking the so-called Miller effect into account. During a low-high or high-low transition, the terminals of the gate-drain capacitor are moving in opposite directions (see Figure 5-14). The voltage change over the floating capacitor is thus twice the actual output voltage swing. To present an identical load to the out-

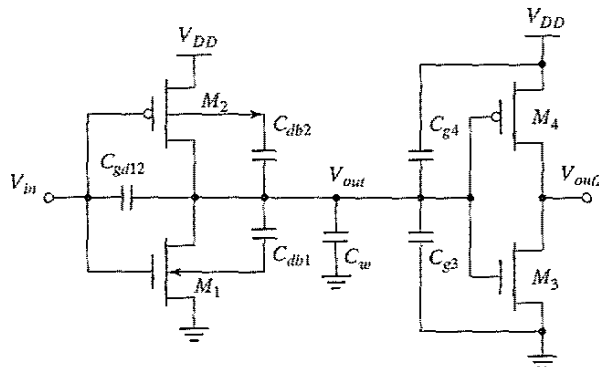

**Figure 5-13** Parasitic capacitances, influencing the transient behavior of the cascaded inverter pair.

 

**Figure 5-14** The Miller effect—A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.

put node, the capacitance to ground must have a value that is twice as large as the floating capacitance.

We use the following equation for the gate-drain capacitors:  $C_{gd} = 2 C_{GD0}W$  (with  $C_{GD0}$  the overlap capacitance per unit width as used in the SPICE model). For an in-depth discussion of the Miller effect, please refer to textbooks such as [Sedra87, p. 57].<sup>2</sup>

#### Diffusion Capacitances $C_{db1}$ and $C_{db2}$

The capacitance between drain and bulk is due to the reverse-biased  $pn$ -junction. Such a capacitor is, unfortunately, quite nonlinear and depends heavily on the applied voltage. We argued in Chapter 3 that the best approach to simplifying the analysis is to replace the nonlinear capacitor by a linear one with the same change in charge for the voltage range of interest. A multiplication factor  $K_{eq}$  is introduced to relate the linearized capacitor to the value of the junction capacitance under zero-bias conditions.

$$C_{eq} = K_{eq}C_{j0} \quad (5.13)$$

with  $C_{j0}$  the junction capacitance per unit area under zero-bias conditions. For convenience, we repeat Eq. (3.11) here, written as

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}] \quad (5.14)$$

with  $\phi_0$  the built-in junction potential and  $m$  the grading coefficient of the junction. Observe that the junction voltage is defined to be negative for reverse-biased junctions.

#### Example 5.3 $K_{eq}$ for a 2.5-V CMOS Inverter

Consider the inverter of Figure 5-13 designed in the generic 0.25- $\mu\text{m}$  CMOS technology. The relevant capacitance parameters for this process were summarized in Table 3-5.

Let us first analyze the NMOS transistor ( $C_{db1}$  in Figure 5-13). The propagation delay is defined by the time between the 50% transitions of the input and the output. For the CMOS inverter, this is the time instance where  $V_{out}$  reaches 1.25-V, as the output

<sup>2</sup>The Miller effect discussed in this context is a simplified version of the general analog case. In a digital inverter, the large-scale gain between input and output always equals  $-1$ .

voltage swing goes from rail to rail or equals 2.5 V. We therefore linearize the junction capacitance over the interval {2.5 V, 1.25 V} for the high-to-low transition, and {0, 1.25 V} for the low-to-high transition.

During the high-to-low transition at the output,  $V_{out}$  initially equals 2.5 V. Because the bulk of the NMOS device is connected to  $GND$ , this translates into a reverse voltage of 2.5 V over the drain junction or  $V_{high} = -2.5$  V. At the 50% point,  $V_{out} = 1.25$  V or  $V_{low} = -1.25$  V. Evaluating Eq. (5.14) for the bottom plate and sidewall components of the diffusion capacitance yields the following data:

$$\text{Bottom plate: } K_{eq} (m = 0.5, \phi_0 = 0.9) = 0.57$$

$$\text{Sidewall: } K_{eqsw} (m = 0.44, \phi_0 = 0.9) = 0.61$$

During the low-to-high transition,  $V_{low}$  and  $V_{high}$  equal 0 V and  $-1.25$  V, respectively, resulting in higher values for  $K_{eq}$ :

$$\text{Bottom plate: } K_{eq} (m = 0.5, \phi_0 = 0.9) = 0.79$$

$$\text{Sidewall: } K_{eqsw} (m = 0.44, \phi_0 = 0.9) = 0.81$$

The PMOS transistor displays a reverse behavior, as its substrate is connected to 2.5 V. Hence, for the high-to-low transition ( $V_{low} = 0$ ,  $V_{high} = -1.25$  V), we have

$$\text{Bottom plate: } K_{eq} (m = 0.48, \phi_0 = 0.9) = 0.79$$

$$\text{Sidewall: } K_{eqsw} (m = 0.32, \phi_0 = 0.9) = 0.86$$

Finally, for the low-to-high transition ( $V_{low} = -1.25$  V,  $V_{high} = -2.5$  V), we have

$$\text{Bottom plate: } K_{eq} (m = 0.48, \phi_0 = 0.9) = 0.59$$

$$\text{Sidewall: } K_{eqsw} (m = 0.32, \phi_0 = 0.9) = 0.7$$

By using this approach, the junction capacitance can be replaced by a linear component and treated as any other device capacitance. The result of the linearization is a minor error in the voltage and current waveforms. The logic delays are not significantly influenced by this simplification.

#### Wiring Capacitance $C_w$

The capacitance due to the wiring depends on the length and width of the connecting wires, and is a function of the distance of the fan-out from the driving gate and the number of fan-out gates. As argued in Chapter 4, this component is growing in importance with the scaling of the technology.

#### Gate Capacitance of Fan-Out $C_{g3}$ and $C_{g4}$

We assume that the fan-out capacitance equals the total gate capacitance of the loading gates  $M_3$  and  $M_4$ . Hence,

$$\begin{aligned} C_{fan-out} &= C_{gate}(NMOS) + C_{gate}(PMOS) \\ &= (C_{GSON} + C_{GDON} + W_n L_n C_{ox}) + (C_{GSOp} + C_{GDOp} + W_p L_p C_{ox}) \end{aligned} \quad (5.15)$$

This expression simplifies the actual situation in two ways:


- It assumes that all components of the gate capacitance are connected between  $V_{out}$  and  $GND$  (or  $V_{DD}$ ), and it ignores the Miller effect on the gate–drain capacitances. This has a relatively minor effect on the accuracy, since we can safely assume that the connecting gate does not switch before the 50% point is reached, and  $V_{out2}$  thus remains constant in the interval of interest.
- A second approximation is that the channel capacitance of the connecting gate is constant over the interval of interest. This is not exactly the case as we discovered in Chapter 3. The total channel capacitance is a function of the operation mode of the device, and varies from approximately  $(2/3) WLC_{ox}$  (saturation) to the full  $WLC_{ox}$  (linear and cutoff). A drop in overall gate capacitance also occurs just before the transistor turns on, as in Figure 3-31. During the first half of the transient, it may be assumed that one of the load devices is always in linear mode, while the other transistor evolves from the off mode to saturation. Ignoring the capacitance variation results in a pessimistic estimation with an error of approximately 10%, which is acceptable for a first-order analysis.

#### Example 5.4 Capacitances of a 0.25- $\mu\text{m}$ CMOS Inverter

A minimum-size, symmetrical CMOS inverter has been designed in the 0.25- $\mu\text{m}$  CMOS technology. The layout is shown in Figure 5-15. The supply voltage  $V_{DD}$  is set to 2.5 V. From the layout, we derive the transistor sizes, diffusion areas, and perimeters. This data is summarized in Table 5-1. As an example, we will derive the drain area and perimeter for the NMOS transistor. The drain area is formed by the metal-diffusion contact, which has an area of  $4 \times 4 \lambda^2$ , and the rectangle between contact and gate, which has an area of  $3 \times 1 \lambda^2$ . This results in a total area of  $19 \lambda^2$ , or  $0.30 \mu\text{m}^2$  (as  $\lambda = 0.125 \mu\text{m}$ ). The perimeter of the drain area is rather involved and consists of the following components (going counterclockwise):  $5 + 4 + 4 + 1 + 1 = 15 \lambda$  or  $PD = 15 \times 0.125 = 1.875 \mu\text{m}$ . Notice that the gate side of the drain perimeter is not included, as this is not considered a part of the sidewall. The drain area and perimeter of the PMOS transistor are derived similarly (the rectangular shape makes the exercise considerably simpler):  $AD = 5 \times 9 \lambda^2 = 45 \lambda^2$ , or  $0.7 \mu\text{m}^2$ ;  $PD = 5 + 9 + 5 = 19 \lambda$ , or  $2.375 \mu\text{m}$ .

Table 5-1 Inverter transistor data.

	W/L	AD ( $\mu\text{m}^2$ )	PD ( $\mu\text{m}$ )	AS ( $\mu\text{m}^2$ )	PS ( $\mu\text{m}$ )
NMOS	0.375/0.25	0.3 ( $19 \lambda^2$ )	1.875 ( $15\lambda$ )	0.3 ( $19 \lambda^2$ )	1.875 ( $15\lambda$ )
PMOS	1.125/0.25	0.7 ( $45 \lambda^2$ )	2.375 ( $19\lambda$ )	0.7 ( $45 \lambda^2$ )	2.375 ( $19\lambda$ )

 

**Figure 5-15** Layout of two chained, minimum-size inverters using SCMOS Design Rules (see also Color-plate 6).

This physical information can be combined with the approximations derived earlier to come up with an estimation of  $C_L$ . The capacitor parameters for our generic process were summarized in Table 3-5 and are repeated here for convenience:

Overlap capacitance:  $CGD0(\text{NMOS}) = 0.31 \text{ fF}/\mu\text{m}$ ;  $CGD0(\text{PMOS}) = 0.27 \text{ fF}/\mu\text{m}$

Bottom junction capacitance:  $CJ(\text{NMOS}) = 2 \text{ fF}/\mu\text{m}^2$ ;  $CJ(\text{PMOS}) = 1.9 \text{ fF}/\mu\text{m}^2$

Sidewall junction capacitance:  $CJSW(\text{NMOS}) = 0.28 \text{ fF}/\mu\text{m}$ ;  $CJSW(\text{PMOS}) = 0.22 \text{ fF}/\mu\text{m}$

Gate capacitance:  $C_{ox}(\text{NMOS}) = C_{ox}(\text{PMOS}) = 6 \text{ fF}/\mu\text{m}^2$

Finally, we should also consider the capacitance contributed by the wire connecting the gates and implemented in metal 1 and polysilicon. A layout extraction program typically delivers precise values for this parasitic capacitance. Inspection of the layout helps us form a first-order estimate. It yields that the metal-1 and polysilicon areas of the wire, which are not over active diffusion, equal  $42 \lambda^2$  and  $72 \lambda^2$ , respectively. With the aid of the interconnect parameters of Table 4-2, we find the wire capacitance (observe that we ignore the fringing

Table 5-2 Components of  $C_L$  (for high-to-low and low-to-high transitions).

Capacitor	Expression	Value (fF) (H → L)	Value (fF) (L → H)
$C_{gd1}$	$2 CGD0_n W_n$	0.23	0.23
$C_{gd2}$	$2 CGD0_p W_p$	0.61	0.61
$C_{db1}$	$K_{eqn} AD_n CJ + K_{eqswp} PD_n CJSW$	0.66	0.90
$C_{db2}$	$K_{eqp} AD_p CJ + K_{eqswp} PD_p CJSW$	1.5	1.15
$C_{g3}$	$(CGD0_n + CGSO_n) W_n + C_{ox} W_n L_n$	0.76	0.76
$C_{g4}$	$(CGD0_p + CGSO_p) W_p + C_{ox} W_p L_p$	2.28	2.28
$C_w$	From Extraction	0.12	0.12
$C_L$	$\Sigma$	6.1	6.0

capacitance in this simple exercise; due to the short length of the wire, this contribution can be ignored compared with the other entries):

$$C_{wire} = 42/8^2 \mu\text{m}^2 \times 30 \text{ aF}/\mu\text{m}^2 + 72/8^2 \mu\text{m}^2 \times 88 \text{ aF}/\mu\text{m}^2 = 0.12 \text{ fF}$$

The results of bringing all the components together are summarized in Table 5-2. We use the values of  $K_{eq}$  derived in Example 5.3 for the computation of the diffusion capacitances. Notice that the load capacitance is almost evenly split between its two major components: the *intrinsic capacitance*, composed of diffusion and overlap capacitances, and the *extrinsic load capacitance*, contributed by wire and connecting gate.

#### 5.4.2 Propagation Delay: First-Order Analysis

One way to compute the propagation delay of the inverter is to integrate the capacitor (dis)charge current. This results in the expression

$$t_p = \int_{v_1}^{v_2} \frac{C_L(v)}{i(v)} dv \quad (5.16)$$

with  $i$  the (dis)charging current,  $v$  the voltage over the capacitor, and  $v_1$  and  $v_2$  the initial and final voltage, respectively. An exact computation of this equation is intractable, as both  $C_L(v)$  and  $i(v)$  are nonlinear functions of  $v$ . Instead, we fall back to the simplified switch model of the inverter introduced in Figure 5-6 to derive a reasonable approximation of the propagation delay adequate for manual analysis. The voltage dependencies of the “on” resistance and the load



capacitor are addressed by replacing both by a constant linear element with a value averaged over the interval of interest. The preceding section derived precisely this value for the load capacitance. An expression for the average “on” resistance of the MOS transistor was already derived in Example 3.8 and is repeated here for convenience:

$$R_{eq} = \frac{1}{V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left( 1 - \frac{7}{9} \lambda V_{DD} \right) \quad (5.17)$$

$$\text{with } I_{DSAT} = k' \frac{W}{L} \left( (V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Deriving the propagation delay of the resulting circuit is now straightforward—it is nothing more than the analysis of a first-order linear  $RC$  network, identical to the exercise of Example 4.5. We learned there that the propagation delay of such a network, excited by a voltage step, is proportional to the time constant of the network, formed by pull-down resistor and load capacitance. Hence,

$$t_{pHL} = \ln(2) R_{eqn} C_L = 0.69 R_{eqn} C_L \quad (5.18)$$

Similarly, we can obtain the propagation delay for the low-to-high transition. We write

$$t_{pLH} = 0.69 R_{eqp} C_L \quad (5.19)$$

with  $R_{eqp}$  the equivalent on resistance of the PMOS transistor over the interval of interest. This analysis assumes that the equivalent load-capacitance is identical for both the high-to-low and low-to-high transitions. This was shown to be approximately the case in the example of the previous section. The overall propagation delay of the inverter is defined as the average of the two values:

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left( \frac{R_{eqn} + R_{eqp}}{2} \right) \quad (5.20)$$

Very often, it is desirable for a gate to have identical propagation delays for both rising and falling inputs. This condition can be achieved by making the “on” resistance of the NMOS and PMOS approximately equal. Remember that this condition is identical to the requirement for a symmetrical VTC.

### Example 5.5 Propagation Delay of a 0.25 $\mu\text{m}$ CMOS Inverter

To derive the propagation delays of the CMOS inverter of Figure 5-15, we make use of Eq. (5.18) and Eq. (5.19). The load capacitance  $C_L$  was already computed in Example 5.4, while the equivalent “on” resistances of the transistors for the generic 0.25- $\mu\text{m}$  CMOS process were derived in Table 3-3. For a supply voltage of 2.5 V, the normalized “on” resistances of NMOS and PMOS transistors equal 13 k $\Omega$  and 31 k $\Omega$ , respectively. From the layout, we determine the ( $W$ -to- $L$ ) ratios of the transistors to be 1.5 for the NMOS, and

4.5 for the PMOS. We assume that the difference between drawn and effective dimensions is small enough to be ignorable. This leads to the following values for the delays:

$$t_{pHL} = 0.69 \times \left( \frac{13 \text{ k}\Omega}{1.5} \right) \times 6.1 \text{ fF} = 36 \text{ ps}$$

$$t_{pLH} = 0.69 \times \left( \frac{31 \text{ k}\Omega}{4.5} \right) \times 6.0 \text{ fF} = 29 \text{ ps}$$

and

$$t_p = \left( \frac{36 + 29}{2} \right) = 32.5 \text{ ps}$$

The accuracy of this analysis is checked by performing a SPICE transient simulation on the circuit schematic, extracted from the layout of Figure 5-15. The computed transient response of the circuit is plotted in Figure 5-16, and determines the propagation delays to be 39.9 ps and 31.7 ps for the HL and LH transitions, respectively. The manual results are good, considering the many simplifications made during their derivation. Notice in particular the overshoots on the simulated output signals. These are caused by the gate-drain capacitances of the inverter transistors, which couple the steep voltage step at the input node directly to the output before the transistors can even start to react to the changes at the input. These overshoots clearly have a negative impact on the performance of the gate and explain why the simulated delays are larger than the estimations.

 


Figure 5-16 Simulated transient response of the inverter of Figure 5-15.

**WARNING:** This example might give the impression that manual analysis always leads to close approximations of the actual response, which is not necessarily the case. Large deviations often can be observed between first- and higher order models. The purpose of the manual

analysis is to get a basic insight into the behavior of the circuit and to determine the dominant parameters. A detailed simulation is indispensable when quantitative data is required. Consider the preceding example a stroke of good luck.


The obvious question a designer asks at this point is how to manipulate or optimize the delay of a gate. To provide an answer to this question, it is necessary to make the parameters governing the delay explicit by expanding  $R_{eq}$  in the delay equation. Combining Eq. (5.18) and Eq. (5.17), and assuming for the time being that the channel-length modulation factor  $\lambda$  is ignorable, yields the following expression for  $t_{pHL}$  (a similar analysis holds for  $t_{pLH}$ ):

$$t_{pHL} = 0.69 \frac{3C_L V_{DD}}{4I_{DSATn}} = 0.52 \frac{C_L V_{DD}}{(W/L)_n k'_n V_{DSATn} (V_{DD} - V_{Tn} - V_{DSATn}/2)} \quad (5.21)$$

In the majority of designs, the supply voltage is chosen high enough so that  $V_{DD} \gg V_{Tn} + V_{DSATn}/2$ . Under these conditions, the delay becomes virtually independent of the supply voltage:

$$t_{pHL} \approx 0.52 \frac{C_L}{(W/L)_n k'_n V_{DSATn}} \quad (5.22)$$

Observe that this is a first-order approximation, and that increasing the supply voltage yields an observable, albeit small, improvement in performance due to a nonzero channel-length modulation factor. This analysis is confirmed in Figure 5-17, which plots the propagation delay of the inverter as a function of the supply voltage. It comes as no surprise that this curve is virtu-

 

**Figure 5-17** Propagation delay of CMOS inverter as a function of supply voltage (normalized with respect to the delay at 2.5 V). The dots indicate the delay values predicted by Eq. (5.21). Observe that this equation is only valid when the devices are velocity saturated. Hence, the deviation at low supply voltages.

ally identical in shape to the one of Figure 3-28, which charts the equivalent “on” resistance of the MOS transistor as a function of  $V_{DD}$ . While the delay is relatively insensitive to supply variations for higher values of  $V_{DD}$ , a sharp increase can be observed starting around  $\approx 2V_T$ . This operation region clearly should be avoided if achieving high performance is a primary design goal.

#### Design Techniques

From the preceding discussion, we deduce that the propagation delay of a gate can be minimized in the following ways:

- *Reduce  $C_L$ .* Remember that three major factors contribute to the load capacitance: the internal diffusion capacitance of the gate itself, the interconnect capacitance, and the fan-out. Careful layout helps to reduce the diffusion and interconnect capacitances. **Good design practice requires keeping the drain diffusion areas as small as possible.**
- *Increase the W/L ratio of the transistors.* This is the most powerful and effective performance optimization tool in the hands of the designer. Proceed with caution, however, when applying this approach. Increasing the transistor size also raises the diffusion capacitance and hence  $C_L$ . In fact, once the intrinsic capacitance (i.e. the diffusion capacitance) starts to dominate the extrinsic load formed by wiring and fan-out, increasing the gate size no longer helps in reducing the delay. It only makes the gate larger in area. This effect is called *self-loading*. In addition, wide transistors have a larger gate capacitance, which increases the fan-out factor of the driving gate and adversely affects its speed as well.
- *Increase  $V_{DD}$ .* As illustrated in Figure 5-17, the delay of a gate can be modulated by modifying the supply voltage. This flexibility allows the designer to trade off energy dissipation for performance, as we will see in a later section. However, increasing the supply voltage above a certain level yields only very minimal improvement and thus should be avoided. Also, reliability concerns (oxide breakdown, hot-electron effects) enforce firm upper bounds on the supply voltage in deep submicron processes. ■

#### Problem 5.4 Propagation Delay as a Function of (dis)charge Current

So far, we have expressed the propagation delay as a function of the equivalent resistance of the transistors. Another approach would be to replace the transistor by a current source with a value equal to the average (dis)charge current over the interval of interest. Derive an expression of the propagation delay using this alternative approach.

#### 5.4.3 Propagation Delay from a Design Perspective

Some interesting design considerations and trade-offs can be derived from the delay expressions we have derived so far. Most importantly, they lead to a general approach toward transistor sizing that will prove to be extremely useful.

##### NMOS-to-PMOS Ratio

So far, we have consistently widened the PMOS transistor so that its resistance matches that of the pull-down NMOS device. This typically requires a ratio of 3 to 3.5 between PMOS and

NMOS width. The motivation behind this approach is to create an inverter with a symmetrical VTC and to equate the high-to-low and low-to-high propagation delays. However, this does not imply that this ratio also yields the minimum overall propagation delay. If symmetry and reduced noise margins are not of prime concern, it is actually possible to speed up the inverter by reducing the width of the PMOS device!

The reasoning behind this statement is that, while widening the PMOS improves the  $t_{pLH}$  of the inverter by increasing the charging current, it also degrades the  $t_{pHL}$  by causing a larger parasitic capacitance. When two contradictory effects are present, a transistor ratio must exist that optimizes the propagation delay of the inverter.

This optimum ratio can be derived using a simple analysis technique. Consider two identical cascaded CMOS inverters. The approximate load capacitance of the first gate is given by

$$C_L = (C_{dp1} + C_{dn1}) + (C_{gp2} + C_{gn2}) + C_W \quad (5.23)$$

where  $C_{dp1}$  and  $C_{dn1}$  are the equivalent drain diffusion capacitances of PMOS and NMOS transistors of the first inverter and  $C_{gp2}$  and  $C_{gn2}$  are the gate capacitances of the second gate.  $C_W$  represents the wiring capacitance.

When the PMOS devices are made  $\beta$  times larger than the NMOS ones ( $\beta = (W/L)_p/(W/L)_n$ ), all transistor capacitances scale in approximately the same way, or  $C_{dp1} \approx \beta C_{dn1}$ , and  $C_{gp2} \approx \beta C_{gn2}$ . Equation (5.23) can then be rewritten as

$$C_L = (1 + \beta)(C_{dn1} + C_{gn2}) + C_W \quad (5.24)$$

Based on Eq. (5.20), the following expression for the propagation delay can be derived,

$$\begin{aligned} t_p &= \frac{0.69}{2}((1 + \beta)(C_{dn1} + C_{gn2}) + C_W) \left( R_{eqn} + \frac{R_{eqp}}{\beta} \right) \\ &= 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_W) R_{eqn} \left( 1 + \frac{r}{\beta} \right) \end{aligned} \quad (5.25)$$


Here,  $r (= R_{eqp}/R_{eqn})$  represents the resistance ratio of identically sized PMOS and NMOS transistors. The optimal value of  $\beta$  can be found by setting  $\frac{\partial t_p}{\partial \beta}$  to 0, which yields

$$\beta_{opt} = \sqrt{r \left( 1 + \frac{C_W}{C_{dn1} + C_{gn2}} \right)} \quad (5.26)$$

This means that when the wiring capacitance is negligible ( $C_{dn1} + C_{gn2} \gg C_W$ ),  $\beta_{opt}$  equals  $\sqrt{r}$ , in contrast to the factor  $r$  normally used in the noncascaded case. If the wiring capacitance dominates, larger values of  $\beta$  should be used. The surprising result of this analysis is that smaller device sizes (and thus a smaller design area) yield a faster design at the expense of symmetry and noise margin.

**Example 5.6 Sizing of CMOS Inverter Loaded by an Identical Gate**

Consider again our standard design example. From the values of the equivalent resistances (Table 3-3), we find that a ratio  $\beta$  of 2.4 ( $= 31 \text{ k}\Omega / 13 \text{ k}\Omega$ ) would yield a symmetrical transient response. Eq. (5.26) now predicts that the device ratio for an optimal performance should equal 1.6. These results are verified in Figure 5-18, which plots the simulated propagation delay as a function of the transistor ratio  $\beta$ . The graph clearly illustrates how a changing  $\beta$  trades off between  $t_{pLH}$  and  $t_{pHL}$ . The optimum point occurs around  $\beta = 1.9$ , which is somewhat higher than predicted. Observe also that the rising and falling delays are identical at the predicted point of  $\beta$  equal to 2.4. This is the preferred operation point when the worst case delay is the prime concern.<sup>3</sup>

 

**Figure 5-18** Propagation delay of CMOS inverter as a function of the PMOS-to-NMOS transistor ratio  $\beta$ .

**Sizing Inverters for Performance**

In this analysis, we assume a symmetrical inverter, which is an inverter where PMOS and NMOS are sized such that the rise and fall delays are identical. The load capacitance of the inverter can be divided into an intrinsic and an extrinsic component, or  $C_L = C_{int} + C_{ext}$ .  $C_{int}$  represents the self-loading or intrinsic output capacitance of the inverter, and is associated with the diffusion capacitances of the NMOS and PMOS transistors as well as the gate-drain overlap (Miller) capacitances.  $C_{ext}$  is the extrinsic load capacitance, attributable to fan-out and wiring

<sup>3</sup>You probably wonder why we do not always consider the worst of the rising and falling delays as the prime performance measure of a gate. When cascading inverting gates to form a more complex logic network, you quickly realize that the average of the two is a more meaningful measure. A rising transition on one gate is followed by a falling transition on the next.

capacitance. Assuming that  $R_{eq}$  stands for the equivalent resistance of the gate, we can express the propagation delay as

$$\begin{aligned} t_p &= 0.69R_{eq}(C_{int} + C_{ext}) \\ &= 0.69R_{eq}C_{int}(1 + C_{ext}/C_{int}) = t_{p0}(1 + C_{ext}/C_{int}) \end{aligned} \quad (5.27)$$

where  $t_{p0} = 0.69 R_{eq} C_{int}$  represents the delay of the inverter only loaded by its own intrinsic capacitance ( $C_{ext} = 0$ ), and is called the *intrinsic or unloaded delay*.

The next question is how transistor sizing impacts the performance of the gate. To answer this question, we must establish the relationship between the various parameters in Eq. (5.27) and a sizing factor  $S$ , which relates the transistor sizes of our inverter to a reference gate—typically a minimum-sized inverter. The intrinsic capacitance  $C_{int}$  consists of the diffusion and Miller capacitances, both of which are proportional to the width of the transistors. Hence,  $C_{int} = SC_{iref}$ . The resistance of the gate relates to the reference gate as  $R_{eq} = R_{ref}/S$ . We can now rewrite Eq. (5.27) as

$$\begin{aligned} t_p &= 0.69(R_{ref}/S)(SC_{iref})(1 + C_{ext}/(SC_{iref})) \\ &= 0.69R_{ref}C_{iref}\left(1 + \frac{C_{ext}}{SC_{iref}}\right) = t_{p0}\left(1 + \frac{C_{ext}}{SC_{iref}}\right) \end{aligned} \quad (5.28)$$


From this analysis, we draw two important conclusions:

- The intrinsic delay of the inverter  $t_{p0}$  is independent of the sizing of the gate, and is determined purely by technology and inverter layout. When no load is present, an increase in the drive of the gate is totally offset by the increased capacitance.
- Making  $S$  infinitely large yields the maximum obtainable performance gain, eliminating the impact of any external load, and reducing the delay to the intrinsic one. Yet, any sizing factor  $S$  that is sufficiently larger than  $(C_{ext}/C_{int})$  produces similar results at a substantial gain in silicon area.

### Example 5.7 Device Sizing for Performance

Let us explore the performance improvement that can be obtained by device sizing in the design of Example 5.5. We find from Table 5-2 that  $C_{int}/C_{ext} \approx 1.05$  ( $C_{int} = 3.0$  fF,  $C_{ext} = 3.15$  fF). This would predict a maximum performance gain of 2.05. A scaling factor of 10 allows us to get within 10% of this optimal performance, while larger device sizes only yield ignorable performance gains.

This is confirmed by simulation results, which predict a maximum obtainable performance improvement of 1.9 ( $t_{p0} = 19.3$  ps). In Figure 5-19, we observe that the majority of the improvement is already obtained for  $S = 5$ , and that sizing factors larger than 10 barely yield any extra gain.

 

**Figure 5-19** Increasing inverter performance by sizing the NMOS and PMOS transistor with an identical factor  $S$  for a fixed fan-out (inverter of Figure 5-15).

### Sizing a Chain of Inverters

While sizing up an inverter reduces its delay, it also increases its input capacitance. Gate sizing in an isolated fashion without taking into account its impact on the delay of the preceding gates is a purely academic enterprise. Therefore, a more relevant problem is determining the optimum sizing of a gate when **embedded in a real environment**. A simple chain of inverters is a good first case to study. To determine the input loading effect, the relationship between the input gate capacitance  $C_g$  and the intrinsic output capacitance of the inverter has to be established. Both are proportional to the gate sizing. Hence, the following relationship holds, independently of gate sizing:

$$C_{int} = \gamma C_g \quad (5.29)$$

In Eq. (5.29),  $\gamma$  is a proportionality factor that is only a function of technology and is close to 1 for most submicron processes, as we observed in the preceding examples. Rewriting Eq. (5.28), we obtain

$$t_p = t_{p0} \left( 1 + \frac{C_{ext}}{\gamma C_g} \right) = t_{p0} (1 + f/\gamma) \quad (5.30)$$

which establishes that the delay of an inverter is **only a function of the ratio between its external load capacitance and its input capacitance**. This ratio is called the *effective fan-out*  $f$ .

Let us consider the circuit of Figure 5.20. The goal is to minimize the delay through the inverter chain, with the input capacitance  $C_{g1}$  of the first inverter—typically a minimally-sized gate—and the load capacitance  $C_L$  at the end of the chain fixed.



 


Figure 5-20 Chain of  $N$  inverters with fixed input and output capacitance.

Given the delay expression for the  $j$ -th inverter stage,<sup>4</sup>

$$t_{p,j} = t_{p0} \left( 1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right) = t_{p0} (1 + f_j / \gamma) \quad (5.31)$$

we can derive the total delay of the chain:

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{j=1}^N \left( 1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right), \text{ with } C_{g,N+1} = C_L \quad (5.32)$$

This equation has  $N - 1$  unknowns, being  $C_{g,2}, C_{g,3}, \dots, C_{g,N}$ . The minimum delay can be found by taking  $N - 1$  partial derivatives, and equating them to 0, or  $\partial t_p / \partial C_{g,j} = 0$ . The result is a set of constraints,

$$C_{g,j+1} / C_{g,j} = C_{g,j} / C_{g,j-1} \quad \text{with } (j = 2 \dots N) \quad (5.33)$$

In other words, the optimum size of each inverter is the geometric mean of its neighbors sizes:

$$C_{g,j} = \sqrt{C_{g,j-1} C_{g,j+1}} \quad (5.34)$$

This means that each inverter is sized up by the same factor  $f$  with respect to the preceding gate, has the same effective fan-out ( $f_j = f$ ), and thus the same delay. With  $C_{g,1}$  and  $C_L$  given, we can derive the sizing factor as

$$f = \sqrt[N]{C_L / C_{g,1}} = \sqrt[N]{F} \quad (5.35)$$

and the minimum delay through the chain as

$$t_p = N t_{p0} (1 + \sqrt[N]{F} / \gamma) \quad (5.36)$$

$F$  represents the *overall effective fan-out* of the circuit and equals  $C_L / C_{g,1}$ . Observe how the relationship between  $t_p$  and  $F$  is a strong function of the number of stages. As expected, the relationship is linear when only 1 stage is present. Introducing a second stage turns it into a square root function, and so on. The obvious question now is how to choose the number of stages so that the delay is minimized for a given value of  $F$ .

<sup>4</sup>This expression ignores the wiring capacitance, which is a fair assumption for the time being.

### Choosing the Right Number of Stages in an Inverter Chain

Evaluation of Eq. (5.36) reveals the trade-offs in choosing the number of stages for a given  $F$  ( $= f^N$ ). When the number of stages is too large, the first component of the equation, which represents the intrinsic delay of the stages, becomes dominant. If the number of stages is too small, the effective fan-out of each stage becomes large, and the second component is dominant. The optimum value can be found by differentiating the minimum delay expression by the number of stages and setting the result to 0. We obtain

$$\gamma + \frac{N\sqrt{F}}{N} - \frac{N\sqrt{F} \ln F}{N} = 0$$

or equivalently

$$(5.37)$$

$$f = e^{(1+\gamma/f)}$$

Equation (5.35) has only a closed-form solution for  $\gamma = 0$ —that is when the self-loading is ignored and the load capacitance only consists of the fan-out. Under these simplified conditions, it is found that the optimal number of stages equals  $N = \ln(F)$ , and the effective fan-out of each stage is set to  $f = e = 2.71828$ . This optimal buffer design scales consecutive stages in an exponential fashion, and is thus called an exponential horn [Mead80]. When self-loading is included, Eq. can only be solved numerically. The results are plotted in Figure 5-21a. For the typical case of  $\gamma \approx 1$ , the optimum tapering factor turns out to be close to 3.6. Figure 5-21b plots the (normalized) propagation delay of the inverter chain as a function of the effective fan-out for  $\gamma = 1$ . Choosing values of the fan-out that are higher than the optimum does not effect the delay very much and reduces the required number of buffer stages and the implementation area. A common practice is to **select an optimum fan-out of 4**. The use of too many stages ( $f < f_{opt}$ ), on the other hand, has a substantial negative impact on the delay, and should be avoided.

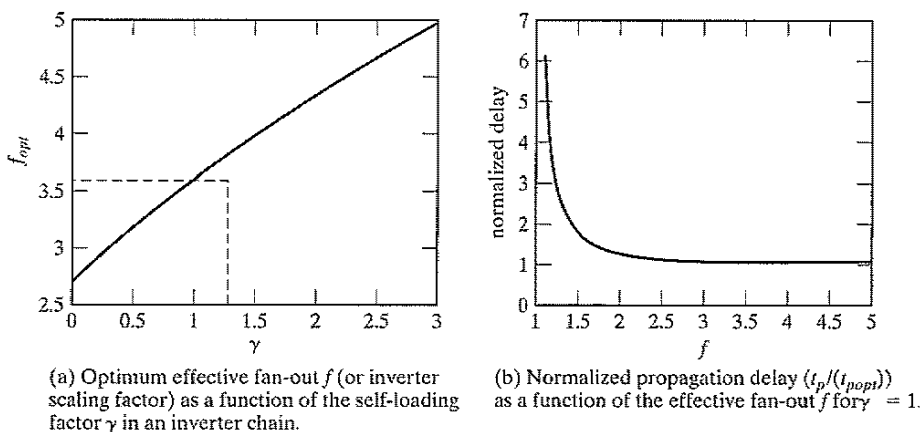


Figure 5-21 Optimizing the number of stages in an inverter chain.

**Example 5.8 The Impact of Introducing Buffer Stages**

Table 5-3 enumerates the values of  $t_{p,opt}/t_{p0}$  for the unbuffered design, the dual stage, and optimized inverter chain for a variety of values of  $F$  (for  $\gamma = 1$ ). Observe the impressive speedup obtained with cascaded inverters when driving very large capacitive loads.

**Table 5-3**  $t_{p,opt}/t_{p0}$  versus  $x$  for various driver configurations.

F	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1


The preceding analysis can be extended to not only cover chains of inverters, but also networks of inverters that contain actual fan-out, an example of which is shown in Figure 5-22. We merely have to adjust the expression for  $C_{ext}$  to incorporate the additional fan-out factors.

**Problem 5.5 Sizing an Inverter Network**

Determine the sizes of the inverters in the circuit of Figure 5-22, such that the delay between nodes *Out* and *In* is minimized. You may assume that  $C_L = 64 C_{g,1}$ .

Hints: Determine first the ratios between the devices that minimize the delay. You should find that the following relationship must hold:

$$\frac{4C_{g,2}}{C_{g,1}} = \frac{4C_{g,3}}{C_{g,2}} = \frac{C_L}{C_{g,3}}$$

 

**Figure 5-22** Inverter network, in which each gate has a fan-out of 4 gates, distributing a single input to 16 output signals in a treelike fashion.


Finding the actual gate sizes ( $C_{g,3} = 2.52C_{g,2} = 6.35C_{g,1}$ ) is a relatively straightforward task (with  $2.52 = 16^{1/3}$ ). Straightforward sizing of the inverter chain, without taking the extra fan-out into account, would have led to a sizing factor of 4 instead of 2.52.

**The Rise-Fall Time of the Input Signal**

All of the preceding expressions were derived under the assumption that the input signal to the inverter abruptly changed from 0 to  $V_{DD}$  or vice versa. Only one of the devices is assumed to be on during the (dis)charging process. In reality, the input signal changes gradually and, temporarily, PMOS and NMOS transistors conduct simultaneously. This affects the total current available for (dis)charging and impacts the propagation delay. Figure 5-23 plots the propagation delay of a minimum-size inverter as a function of the input signal slope—as obtained from SPICE. It can be observed that  $t_p$  increases (approximately) linearly with increasing input slope, once  $t_s > t_p$  ( $t_s = 0$ ).

While it is possible to derive an analytical expression describing the relationship between input signal slope and propagation delay, the result tends to be complex and of limited value. From a design perspective, it is more valuable to relate the impact of the finite slope on the performance directly to its cause, which is the limited driving capability of the preceding gate. If the latter would be infinitely strong, its output slope would be zero, and the performance of the gate under examination would be unaffected. The strength of this approach is that it realizes that a gate is never designed in isolation, and that its performance is affected by both the fan-out and the driving strength of the gate(s) feeding into its inputs. This leads to a revised expression for the propagation delay of an inverter  $i$  in a chain of inverters [Hedenstierna87]:

$$t_p^i = t_{step}^i + \eta t_{step}^{i-1} \tag{5.38}$$

 

**Figure 5-23**  $t_p$  as a function of the input signal slope (10–90% rise or fall time) for minimum-size inverter with fan-out of a single gate.

Eq. (5.38) states that the propagation delay of inverter  $i$  equals the sum of the delay of the same gate for a step input ( $t_{step}^i$ ) (i.e. zero input slope) augmented with a fraction of the step-input delay of the preceding gate ( $i - 1$ ). The fraction  $\eta$  is an empirical constant, which typically has values around 0.25. This expression has the advantage of being very simple, while exposing all relationships necessary for the delay computations of complex circuits.

### Example 5.9 Delay of Inverter Embedded in Network

Consider, for example, the circuit of Figure 5-22. With the aid of Eq. (5.31) and Eq. (5.38), we can derive an expression for the delay of the stage-2 inverter, marked by the gray box:

$$t_{p,2} = t_{p0} \left( 1 + \frac{4C_{g,3}}{\gamma C_{g,2}} \right) + \eta t_{p0} \left( 1 + \frac{4C_{g,2}}{\gamma C_{g,1}} \right)$$

An analysis of the overall propagation delay in the style of Problem 5.5, leads to the following revised sizing requirements for minimum delay:

$$\frac{4(1 + \eta)C_{g,2}}{C_{g,1}} = \frac{4(1 + \eta)C_{g,3}}{C_{g,2}} = \frac{C_L}{C_{g,3}}$$

If we assume  $\eta = 0.25$ ,  $f_2$  and  $f_1$  evaluate to 2.47.

### Design Challenge

It is advantageous to keep the signal rise times smaller than or equal to the gate propagation delays. This proves to be true not only for performance, but also for power consumption considerations, as will be discussed later. Keeping the rise and fall times of the signals small and of approximately equal values is one of the major challenges in high-performance design; it is often called *slope engineering*. ■

### Problem 5.6 Impact of Input Slope

Determine if reducing the supply voltage increases or decreases the influence of the input signal slope on the propagation delay. Explain your answer.

### Delay in the Presence of (Long) Interconnect Wires

The interconnect wire has played a minimal role in our analysis thus far. When gates get farther apart, the wire capacitance and resistance can no longer be ignored, and may even dominate the transient response. Earlier delay expressions can be adjusted to accommodate these extra contributions by employing the wire modeling techniques introduced in the previous chapter. The analysis detailed in Example 4.9 is directly applicable to the problem at hand. Consider the circuit of Figure 5-24, where an inverter drives a single fan-out through a wire of length  $L$ . The driver is represented by a single resistance  $R_{dr}$ , which is the average between  $R_{eqn}$  and  $R_{eqp}$ .  $C_{int}$  and  $C_{fan}$  account for the intrinsic capacitance of the driver, and the input capacitance of the fan-out gate, respectively.

 


Figure 5-24 Inverter driving single gate through wire of length  $L$ .

The propagation delay of the circuit can be obtained by applying the Elmore delay expression:

$$\begin{aligned} t_p &= 0.69R_{dr}C_{int} + (0.69R_{dr} + 0.38R_w)C_w + 0.69(R_{dr} + R_w)C_{fan} \\ &= 0.69R_{dr}(C_{int} + C_{fan}) + 0.69(R_{dr}c_w + r_wC_{fan})L + 0.38r_wc_wL^2 \end{aligned} \quad (5.39)$$

The 0.38 factor accounts for the fact that the wire represents a distributed delay.  $C_w$  and  $R_w$  stand for the total capacitance and resistance of the wire, respectively. The delay expression contains a component that is linear with the wire length, as well as a quadratic one. It is the latter that causes the wire delay to rapidly become the dominant factor in the delay budget for longer wires.

#### Example 5.10 Inverter Delay in Presence of Interconnect

Consider the circuit of Figure 5-24, and assume the device parameters of Example 5.5:  $C_{int} = 3$  fF,  $C_{fan} = 3$  fF, and  $R_{dr} = 0.5(13/1.5 + 31/4.5) = 7.8$  k $\Omega$ . The wire is implemented in metal and has a width of  $0.4$   $\mu\text{m}$ —the minimum allowed. This yields the following parameters:  $c_w = 92$  aF/ $\mu\text{m}$ , and  $r_w = 0.19$   $\Omega/\mu\text{m}$  (Example 4.4). With the aid of Eq. (5.39), we can compute at what wire length the delay of the interconnect becomes equal to the intrinsic delay caused purely by device parasitics. Solving the following quadratic equation yields a single (meaningful) solution:

$$\begin{aligned} 6.6 \times 10^{-18}L^2 + 0.5 \times 10^{-12}L &= 32.29 \times 10^{-12} \\ \text{or, } L &= 65 \mu\text{m} \end{aligned}$$

Observe that the extra delay is due solely to the linear factor in the equation—more specifically, to the extra capacitance introduced by the wire. The quadratic factor (the distributed wire delay) becomes dominant only at much larger wire lengths ( $> 7$  cm). This can be attributed to the high resistance of the (minimum-size) driver transistors. A different balance emerges when wider transistors are used. Analyze, for instance, the same problem with the driver transistors 100 times wider.

## 5.5 Power, Energy, and Energy Delay

So far, we have seen that the static CMOS inverter with its almost ideal VTC—symmetrical shape, full logic swing, and high noise margins—offers a superior robustness, which simplifies the design process considerably and opens the door for design automation. Another major

attractor for static CMOS is the almost complete absence of power consumption in steady-state operation mode. It is this combination of robustness and low static power that has made static CMOS the technology of choice of most contemporary digital designs. The power dissipation of a CMOS circuit is instead dominated by the dynamic dissipation resulting from charging and discharging capacitances.

### 5.5.1 Dynamic Power Consumption

#### Dynamic Dissipation due to Charging and Discharging Capacitances

Each time the capacitor  $C_L$  gets charged through the PMOS transistor, its voltage rises from 0 to  $V_{DD}$ , and a certain amount of energy is drawn from the power supply. Part of this energy is dissipated in the PMOS device, while the remainder is stored on the load capacitor. During the high-to-low transition, this capacitor is discharged, and the stored energy is dissipated in the NMOS transistor.<sup>5</sup>

A precise measure for this energy consumption can be derived. Let us first consider the low-to-high transition. We assume, initially, that the input waveform has zero rise and fall times—in other words, the NMOS and PMOS devices are never on simultaneously. Therefore, the equivalent circuit of Figure 5-25 is valid. The values of the energy  $E_{VDD}$ , taken from the supply during the transition, as well as the energy  $E_C$ , stored on the capacitor at the end of the transition, can be derived by integrating the instantaneous power over the period of interest:

$$E_{VDD} = \int_0^{\infty} i_{VDD}(t) V_{DD} dt = V_{DD} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt = C_L V_{DD} \int_0^{V_{DD}} dv_{out} = C_L V_{DD}^2 \quad (5.40)$$

 


Figure 5-25 Equivalent circuit during the low-to-high transition.

<sup>5</sup>Observe that this model is a simplification of the actual circuit. In reality, the load capacitance consists of multiple components, some of which are located between the output node and GND, others between output node and  $V_{DD}$ . The latter experience a charge–discharge cycle that is out of phase with the capacitances to GND (i.e., they get charged when  $V_{out}$  goes low and discharged when  $V_{out}$  rises.) While this distributes the energy delivery by the supply over the two phases, it does not affect the overall dissipation, and the results presented in this section are still valid.